

21415

3 Hours / 100 Marks

Seat No.

| | | | | | | | |
|--|--|--|--|--|--|--|--|
| | | | | | | | |
|--|--|--|--|--|--|--|--|

- Instructions* –
- (1) All Questions are *Compulsory*.
 - (2) Answer each next main Question on a new page.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Assume suitable data, if necessary.
 - (6) Mobile Phone, Pager and any other Electronics Communication devices are not permissible in Examination Hall.

Marks

1. a) Attempt any THREE of the following: 12

- (i) Draw symbols and VI characteristics of following devices:
 - 1) GTO
 - 2) IGBT
 - 3) LASCR
 - 4) TRIAC
- (ii) Following figure shows circuit diagram of a six-pulse converter. With supply phase sequence A-B-C, indicate the firing sequence of six thyristors. (Refer Fig. No. 1)

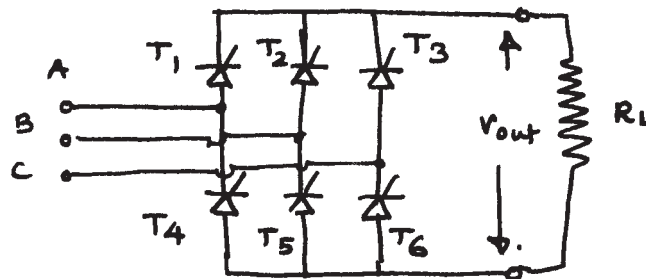


Fig. No. 1

P.T.O.

- (iii) Draw circuit diagram of single phase full bridge inverter.
Draw waveforms of load voltage and load current for R-L load.
- (iv) Explain the technique for speed control of DC series motor using thyristor converter.

b) Attempt any ONE of the following:

6

- (i) Draw waveforms of the following power electronic circuit for gate pulses pattern as shown in Figure No. 2. Indicate load voltage, current, capacitor voltage.

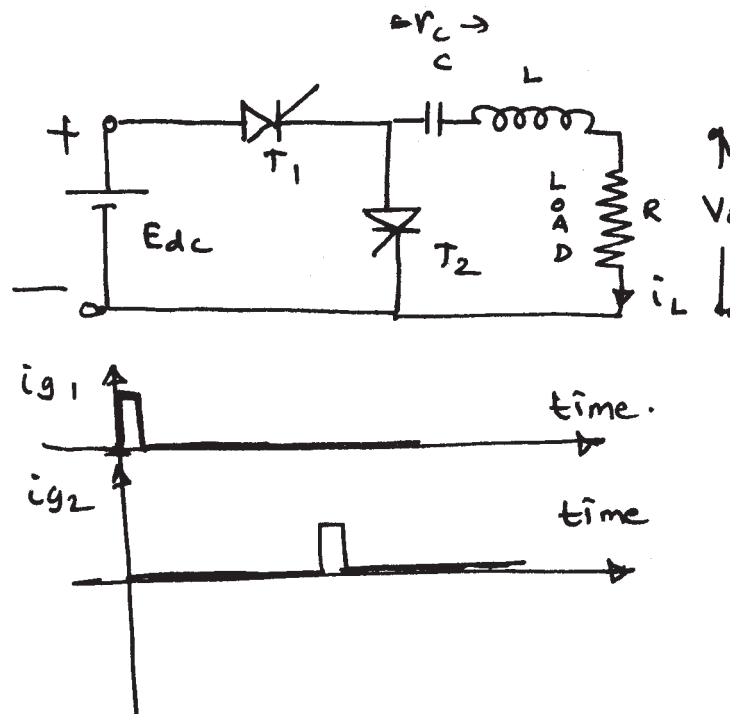


Fig. No. 2

- (ii) Draw circuit diagram of single phase mid-point converter.
Draw output voltage, current waveforms with R-L load.

- 2. Attempt any FOUR of the following:** **16**
- a) State any four voltage and current rating of thyristor.
 - b) Draw circuit diagram and waveforms of single phase cycloconverter.
 - c) Indicate firing angle and conduction angle for half wave controlled converter connected to
 - (i) R Load
 - (ii) R-L load
 - d) Explain turn-OFF methods of a thyristor.
 - e) Describe how control of firing angle can control speed of DC shunt motor controlled by thyristor converter.
 - f) Classify choppers based on quadrants.
- 3. Attempt any FOUR of the following:** **16**
- a) Draw two transistor equivalent circuit of a thyristor and explain turn-ON process.
 - b) What is effect of connecting freewheeling diode on controlled converter performance?
 - c) Draw equivalent circuit of thyristor mounted on heat sink. Indicate thermal resistances.
 - d) Draw schematic circuit diagram of Class-B chopper and necessary waveforms.
 - e) Draw schematic circuit diagram of thyristorized battery charger.

4. a) Attempt any THREE of the following: 12
- (i) Describe control techniques for control of chopper.
 - (ii) Draw circuit diagram of UJT triggering of SCR and draw waveforms to show firing angle control.
 - (iii) Describe use of thyristor in static VAR compensation.
 - (iv) Draw circuit diagram of JONES chopper. Draw waveforms of load voltage and capacitor voltage.
- b) Attempt any ONE of the following: 6
- (i) What is meaning of “Harmonics”? Draw circuit diagram of any one type of harmonic filter used at inverter output.
 - (ii) Describe speed control of 3 ϕ Induction motor using Voltage Source Inverter. What is the need of controlling v/f ratio?
5. Attempt any FOUR of the following: 16
- a) Describe effect of supply inductance on output voltage of converter.
 - b) Describe working principle of dielectric heating using thyristor.
 - c) Describe working of basic Current Source Inverter (CSI) based induction motor control.
 - d) Describe Sinusoidal PWM for control of inverter. Define modulation index.
 - e) Describe working of electric welding using thyristor.
 - f) Identify the mistakes in the circuit shown in Figure No. 3 and correct the same and draw voltage output and current waveforms for R-L Load.

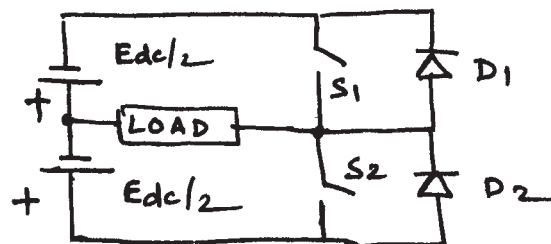


Fig. No. 3

6. Attempt any FOUR of the following:**16**

- a) Draw waveforms to indicate turn-ON process of a thyristor. Indicate rise time, delay and spread time.
 - b) Describe thyristorised induction heating.
 - c) State differences between MOSFET and thyristor inverter.
 - d) Describe working of load commutated chopper.
 - e) Describe street light control using thyristor.
-