

17323

14115

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions* – (1) All Questions are *Compulsory*.
(2) Illustrate your answers with neat sketches wherever necessary.
(3) Figures to the right indicate full marks.
(4) Assume suitable data, if necessary.
(5) Use of Non-programmable Electronic Pocket Calculator is permissible.

Marks

1. Attempt any TEN of the following: 20
- a) Define cycle and time period related to a.c. waveform.
- b) Find frequency and amplitude of the following waveform.
Refer Figure No. 1

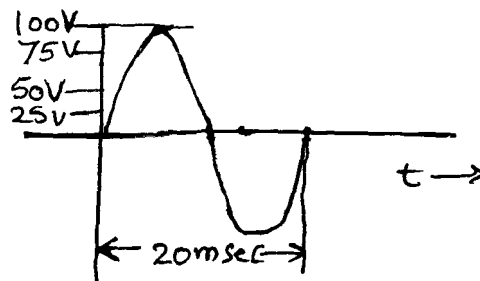


Fig. No. 1

P.T.O.

- c) Define active power and reactive power for R-L-C series circuit.
- d) Draw impedance triangle and voltage phasor diagram for R-L series circuit.
- e) Define susceptance and admittances for a parallel circuit.
- f) Define quality factor for parallel resonance and write its mathematical expression.
- g) Draw sinusoidal waveform of 3-phase emf and indicate the phase sequence.
- h) Draw circuit diagrams showing additive polarity and subtractive polarity.
- i) Write the procedure of converting a current source into voltage source.
- j) State superposition theorem applied to D.C. circuits.
- k) State maximum power transfer theorem for D.C. circuits.
- l) State the behavior of following elements at the time of switching i.e. transient period.
 - (i) Pure L
 - (ii) Pure C.

2. Attempt any FOUR of the following:

16

- a) An e.m.f. source represented by $e = 20 \sin 314t$ is connected to a pure inductance having value 10 mH. Find:
 - (i) The equation of current flowing through it
 - (ii) Draw the waveforms of voltage and current.
- b) Derive the expression for current in pure capacitive circuit when connected to sinusoidal a.c. source. Draw the phasor diagram.

- c) For given waveform. Refer Figure No. 2:
- Identify type of circuit
 - State nature of p.f.
 - Draw phasor diagram
 - Write expressions for voltage and current.

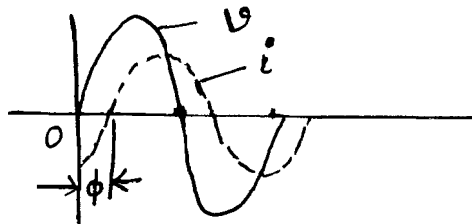


Fig. No. 2

- d) Draw graphical representation of resistance, inductive reactance, capacitive reactance and impedance related to frequency for series resonance circuit.
- e) An alternating voltage of 250 V, 50 Hz is applied to a coil which takes 5 A of current. The power absorbed by the circuit is 1 KW. Find the resistance and inductance of the coil.
- f) A R-L-C series circuit with a resistance of 20Ω , inductance of 0.25 H and capacitance of $100 \mu\text{F}$ is supplied with 240 V variable a.c. supply calculate:
- Resonance frequency
 - Current at this condition
 - Power factor
 - Quality factor.


3. Attempt any FOUR of the following:**16**

- a) Compare series resonance to parallel resonance on the basis of:
- (i) Resonant frequency
 - (ii) Impedance
 - (iii) Current and
 - (iv) Magnification.
- b) Derive the expression for resonance frequency for a R-L-L parallel circuit.
- c) A choke coil has a resistance of $2\ \Omega$ and an inductance of $0.035\ \text{H}$ is connected in parallel with a $350\ \mu\text{F}$ capacitor which is in series with a resistance of $20\ \Omega$. When the combination is connected across a $200\ \text{V}$, $50\ \text{Hz}$ supply. Calculate:
- (i) The total current taken and
 - (ii) Power factor of whole circuit.
- d) A coil of resistance $4\ \Omega$ and inductance $0.07\ \text{H}$ is connected in parallel with another coil of resistance $10\ \Omega$ and inductance $0.12\ \text{H}$. The combination is connected across $230\ \text{V}$, $50\ \text{Hz}$ supply. Determine total current and current through each branch.
- e) Define the following terms:
- (i) Lagging quantity
 - (ii) Leading quantity
- Also represent the above terms for voltage and current in pure inductance and pure capacitance circuit.
- f) A $200\ \text{W}$, $100\ \text{V}$ lamp is connected in series with a capacitor to a $120\ \text{V}$, $50\ \text{Hz}$ a.c. supply calculate:
- (i) The capacitance required
 - (ii) The phase angle between voltage and current.


4. Attempt any **FOUR** of the following:

16

- a) Draw the waveforms of a 3-phase emf. with following phase sequence.
- (i) R-B-Y
- (ii) B-R-Y
- b) Three coils each with a resistance of $10\ \Omega$ and inductance of $0.35\ \text{mH}$ are connected in star to a 3-phase, $440\ \text{V}$, $50\ \text{Hz}$ supply. Calculate the line current and total power taken per phase.
- c) A delta connected induction motor is supplied by 3-phase, $400\ \text{V}$, $50\ \text{Hz}$ supply. The line current is $43.3\ \text{A}$ and the total power taken from the supply is $24\ \text{KW}$. Find the resistance and reactance per phase of motor winding.
- d) Derive the formulae for star to delta transformation.
- e) Using mesh analysis calculate voltage drop across $10\ \Omega$ resistance in following circuit. Refer Figure No. 3

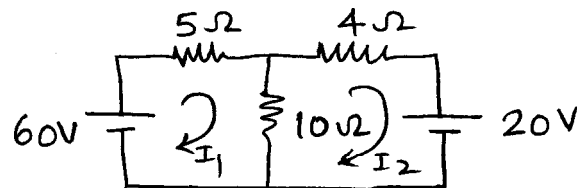**Fig. No. 3**


- f) For following circuit calculate resistance R . using Node analysis. Refer Figure No. 4.

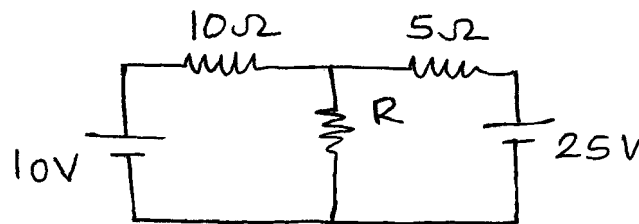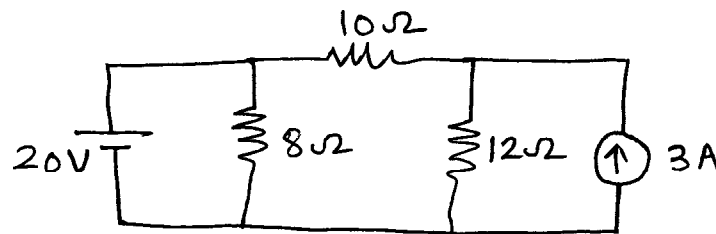**Fig. No. 4**

5. Attempt any ONE of the following:


16

- With the help of phasor diagram, derive the relationship between line and phase values in a balanced star connected 3-phase supply.
- State the Norton's theorem. Also write stepwise procedure for applying Norton's theorem to simple circuit.
- Calculate current through each branch using superposition theorem. Refer Figure No. 5

Fig. No. 56. Attempt any FOUR of the following:

16

- Convert following circuit into Thevenin's circuit across A and B. Refer Figure No. 6

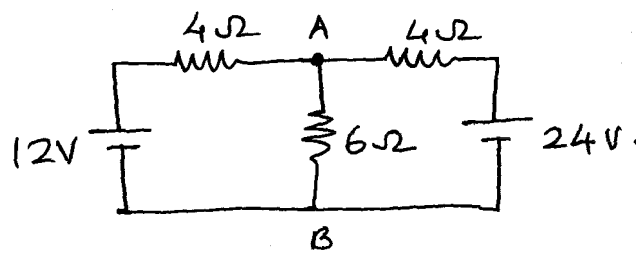Fig. No. 6

- b) Calculate the value of R_L in following circuit using maximum power transfer theorem for the transfer of maximum power to the load. Refer Figure No. 7

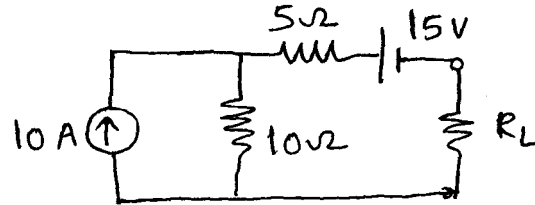


Fig. No. 7

- c) Determine current through $10\ \Omega$ resistance using mesh analysis. Refer Figure No. 8

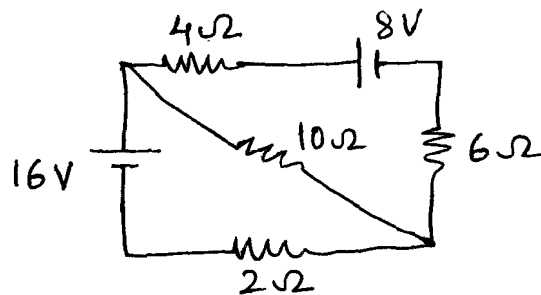


Fig. No. 8

- d) Derive the expression for resonance frequency in a R-L-C series circuit.
- e) Explain the concept of initial and final conditions in switch circuits for R, L and C.
- f) Draw the phasor diagram and waveforms of voltage, current and power in a pure inductance circuit supplied by a 1-phase a.c. source.
