



# 17302

15162

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All questions are **compulsory**.
  - (2) Illustrate your answers with neat sketches **wherever** necessary.
  - (3) Figures to the **right** indicate **full** marks.
  - (4) Assume suitable data, if **necessary**.
  - (5) Use of Non-programmable Electronic Pocket Calculator is **permissible**.
  - (6) Mobile Phone, Pager and any other Electronic Communication devices are **not** permissible in Examination Hall.

**Marks**

1. A) Attempt **any six** :

**12**

- a) What is rectifier ? List types of rectifier.
- b) Sketch symbol and label the terminals of zener diode and LED.
- c) Sketch and label input and output terminals of CB configuration.
- d) Sketch pin diagram of IC 555 and label all pins.
- e) Draw logical symbol of 2 : 1 multiplexer and write its truth table.
- f) State types of real time mechatronics system.
- g) Draw V-I characteristics of P-N junction diode.
- h) List types of Bijunction transistor and draw symbols of the same with neat labels.

B) Attempt **any two** :

**8**

- i) What is filter ? List types of filter. Draw circuit diagram of any one type.
- ii) Sketch circuit diagram of non-inverting op-amp. Calculate gain if  $R_f = 15 \text{ k}\Omega$   $R_i = 5 \text{ k}\Omega$ .
- iii) What is PLC ? Sketch architecture of PLC and label all blocks.

2. Attempt **any four** :

**16**

- a) Compare Bijunction transistor and Field effect transistor.
- b) Sketch pin out diagram of IC 741. label all pins and state function of each pin.
- c) What is thermal runaway ? What is the use of heat sink ?
- d) What is oscillator ? State Barkhausen criteria for oscillations. List types of oscillator.
- e) Sketch logical circuit of differentiator and write its output voltage equation.
- f) Write truth table and sketch symbol of AND and NAND gate.

**P.T.O.**



- 3. Attempt any four :** **16**
- a) Draw instrumentation amplifier and write its output voltage equation.
  - b) Compare microprocessor and microcontroller (any 4 points).
  - c) Draw two stage RC coupled amplifier and its frequency response.
  - d) Sketch circuit diagram, input and output waveform of full wave bridge rectifier.
  - e) What is mechatronics ? State its any four applications.
  - f) Draw block diagram of ADC and write function of each block.
- 4. Attempt any four :** **16**
- a) Sketch block diagram of CNC system from mechatronics view and state function of each block.
  - b) What is data logger ? State its applications.
  - c) What is transducer ? What are the selection criteria of transducers ? Give classification of transducer.
  - d) Write features of 8085 microprocessor.
  - e) Draw ladder diagram for start-stop logic with one input push button for start and one push button for stop and one output for motor to activate solenoid valve.
  - f) Draw logical diagram of D Flip-Flop and write its truth table.
- 5. Attempt any four :** **16**
- a) Define load and line regulation.
  - b) Compare HWR and FWR with respect to ripple factor and efficiency.
  - c) How BJT works as a switch ? (Explain with diagram).
  - d) Draw circuit diagram and waveform of Astable multivibrator using IC 555.
  - e) Draw Decade counter using T. Flip-Flop and write its truth table.
  - f) State two reason that mechatronics system is getting popular. Give basic elements of mechatronics.
- 6. Attempt any four :** **16**
- a) Draw block diagram of regulated power supply and give function of each block.
  - b) List four criteria to select PLC for any particular application.
  - c) How optocoupler act as an isolator ?
  - d) Draw single channel DAS (Data Acquisition System). Give function of each block.
  - e) What is the need of signal conditioning ? Draw AC signal conditioning system.
  - f) What is triggering mechanism ? Give types of triggering with waveform.
-