



17302

15116

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) *All questions are compulsory.*
 - (2) *Illustrate your answers with neat sketches wherever necessary.*
 - (3) *Figures to the right indicate full marks.*
 - (4) *Use of Non-programmable Electronic Pocket Calculator is permissible.*
 - (5) *Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.*

Marks

1. a) Attempt **any six** : **12**
- i) State types of filters.
 - ii) Draw symbols of LDR and Diode.
 - iii) State types of oscillators.
 - iv) Define thermal runaway.
 - v) Draw logical symbol of NOT and AND gate.
 - vi) Draw symbol and label terminals of NPN and PNP transistors.
 - vii) Define intrinsic and extrinsic semiconductors.
 - viii) Draw VI characteristics of PN junction diode.
- b) Attempt **any two** : **8**
- i) What is PLC ? Sketch architecture of PLC and label all blocks.
 - ii) Differentiate microprocessor and microcontroller.
 - iii) Sketch circuit diagram of non-inverting op-amp. Calculate gain if $R_f = 25 \text{ k}\Omega$, $R_1 = 5 \text{ k}\Omega$.
2. Attempt **any four** : **16**
- a) Differentiate Bifunction transistor and field effect transistor.
 - b) Draw instrumentation amplifier and write its output voltage equation.
 - c) Explain load and line regulation.
 - d) Illustrate working of BJT as a switch with diagram.
 - e) Draw ladder diagram for start-stop logic with one input push button for start and one push button for one output for motor to activate solenoid valve.
 - f) Write truth table and sketch symbol of AND and NAND Gate.

P.T.O.

**3. Attempt any four :****16**

- a) Sketch pin out diagram of IC 741. Label all pins and state function of each pin.
- b) Differentiate RC, LC and crystal oscillator on the basis of
 - i) Component used
 - ii) Frequency range
 - iii) Frequency stability
 - iv) Applications.
- c) Sketch circuit diagram, input and output waveform of half wave rectifier.
- d) What is mechatronics ? State its any four applications.
- e) Draw circuit diagram and waveform of astable multivibrator using IC 555.
- f) Illustrate function of D flip-flop with truth table and logical diagram.

4. Attempt any four :**16**

- a) State the principle of R-2R type DAC and write two applications of DAC.
- b) Draw two stage RC coupled amplifier and its frequency response.
- c) What is data logger ? State its applications.
- d) Write features of 8085 microprocessor.
- e) Draw and explain the circuit of op-amp as adder.
- f) Draw block diagram of regulated power supply and write function of each block.

5. Attempt any four :**16**

- a) What is transducer ? Write selection criteria for transducer.
- b) State need of signal conditioning. Draw AC signal conditioning system.
- c) Draw single channel data acquisition system and write function of each block.
- d) Draw CB and CE configuration for BJT.
- e) Draw transformer coupled amplifier and its frequency response.
- f) Draw logical diagram of 4 : 1 multiplexer and write its truth table.

6. Attempt any four :**16**

- a) What is decoder ? Draw logical diagram of 3 : 8 decoder and its truth table.
 - b) State the factors on which selection of PLC is based.
 - c) Explain the concept of CIM briefly.
 - d) What is advance vehicle condition system ? Explain briefly.
 - e) State function and applications of robotics.
 - f) Draw J-K flip-flop using NAND gate and what is the race around condition ?
-