



17320

21314

3 Hours/100 Marks

Seat No.

--	--	--	--	--	--	--	--

- 
- Instructions:**
- (1) **All** questions are **compulsory**.
  - (2) Illustrate your answers with **neat** sketches **wherever** necessary.
  - (3) Figures to the **right** indicate **full** marks.
  - (4) Use of Non-programmable Electronic Pocket Calculator is **permissible**.
  - (5) Mobile Phone, Pager and any other Electronic Communication devices are **not permissible** in Examination Hall.
- 

**MARKS**

1. Attempt **any ten** of the following :

**20**

- a) Convert given numbers :
  - i)  $(110100)_2 = (\dots)_{\text{Gray}}$
  - ii)  $(1111)_{\text{Gray}} = \dots_B$
- b) Draw the logic circuit diagram of 1 bit memory cell using NAND gate.
- c) State the necessity of multiplexers.
- d) Differentiate between RAM and ROM (any 2 points).
- e) Subtract  $(32)_{10}$  from  $(85)_{10}$  using 2's complement binary arithmetic.
- f) Give two applications of A/D converter.
- g) Draw OR and AND gate using NAND gate only.
- h) Classify memories on the basis of principle of operation.
  - i) Write truth table and the expressions of half subtractor.
  - j) Perform  $(52)_{10} - (89)_{10}$  using 9's and 10's complement method.
- k) Draw the truth table of following IC's
  - i) IC – 7432
  - ii) IC – 7486
- l) Draw circuit diagram of 4 : 1 multiplexer.
- m) Give various methods of D/A converter.
- n) State the applications of Flip-Flops.

**P.T.O.**



2. Attempt **any four** of the following :

- a) Perform the following operations :
  - i)  $(11100)_2 \div (100)_2$
  - ii)  $(1010.11)_2 \times (11)_2$
- b) Design 32 : 1 multiplexer using 16 : 1 multiplexer and 2 : 1 multiplexer.
- c) Draw the circuit diagram of S – R Flip-Flop using NAND gate and describe its working.
- d) Simplify the following expression using Boolean laws.
  - i)  $y = (A + B) (A + C)$
  - ii)  $y = ABC + \bar{A}\bar{B}C + A\bar{B}\bar{C}$
- e) How many bits are required for a resolution of 5 mV and full scale voltage in 15V ?
- f) Identify the following circuit as combinational circuit or sequential circuit.
  - i) 3 – bit ring counter
  - ii) Full adder
  - iii) Clocked J-K F/F
  - iv) 4 : 1 MUX

3. Attempt **any four** of the following :

- a) State and prove De-Morgan’s 1<sup>st</sup> and 2<sup>nd</sup> theorem.
- b) Describe the operation of single digit BCD adder using IC – 7483 with circuit diagram.
- c) State the working principle of J–K Flip-Flop with neat diagram.
- d) Minimize the following expression using K-map.
  - i)  $f(w, x, y) = \sum m (0, 1, 2, 4, 6, 7)$
  - ii)  $f(A, B, C, D) = \prod M (0, 2, 7, 8, 9, 10, 13)$
- e) Describe with circuit diagram the working operation of static RAM cell.
- f) Study the given circuit as shown in fig. no. 1 initial o/p condition is  $Q_A Q_B Q_C = 010$ , write truth table of output  $Q_A Q_B Q_C$ .

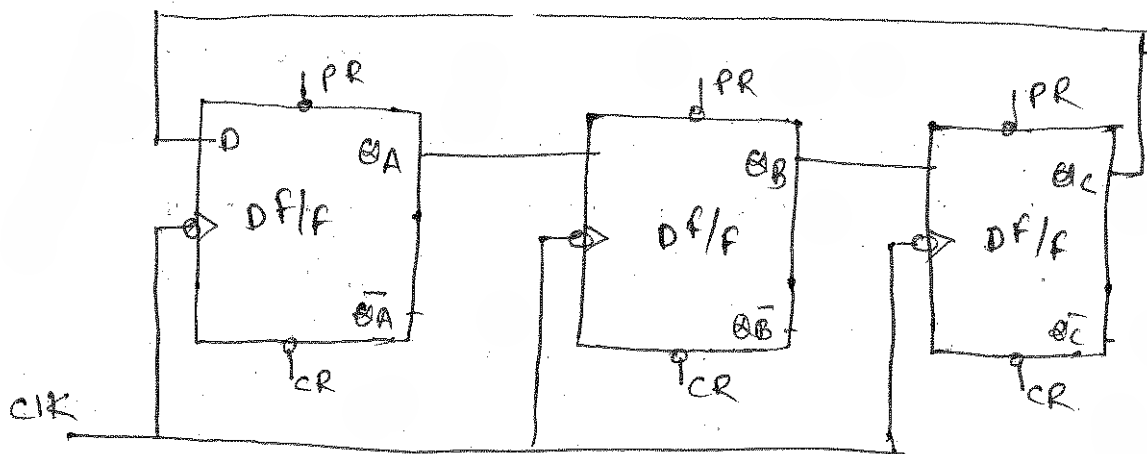


Fig No. 1




4. Attempt **any four** of the following :

- a) Encode the following decimal number in BCD code and excess-3 code.
  - i)  $(48)_{10}$
  - ii)  $(228)_{10}$
- b) Describe R-2R ladder network method of D/A conversion with neat circuit diagram.
- c) Explain the operation of TTL logic using NAND gate.
- d) Design a full subtractor circuit using K-map with truth tables.
- e) For 3 bit synchronous up-counter.
  - i) Draw circuit diagram (use T-Flip Flop)
  - ii) Write truth table
- f) Draw block diagram of decimal to BCD encoder with its truth table.

5. Attempt **any four** of the following :

 - a) Compare combinational and sequential logic circuits. (any four points)
- b) Draw pinout diag. of 2716 EPROM and state its operation.
- c) Explain race around condition in J-K Flip-Flop.
- d) Describe the working of dual slope A/D converter.
- e) Compare TTL and CMOS logic families.
- f) In the given fig. 2, the control signal  $S_2S_3$  of 1 : 4 demux changes from 00 through 11. Write its truth table.



( +5V = 1, Ground = 0 )

Fig. No. 2



6. Attempt **any four** of the following :

- Add  $(147)_{10}$  and  $(284)_{10}$  in BCD code.
- Explain the operation of 1 : 4 de-multiplexer using logic gate.
- Describe operation of SIPO shift register with circuit diagram.
- A RAM IC has 12 address lines and 8 data lines. If its first location has address 9000H what will be the address of the last location ?
- Describe the working principle of successive approximation method ADC with block diagram.
- For a given logical diagram, derive Boolean expression for output Y by simplifying it as much as possible.

 


Fig. No. 3