

17424

15162

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions* – (1) All Questions are *Compulsory*.
(2) Answer each Section on separate answer sheet.
(3) Illustrate your answers with neat sketches wherever necessary.
(4) Figures to the right indicate full marks.
(5) Use of Non-programmable Electronic Pocket Calculator is permissible.
(6) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

SECTION - I

1. Attempt any NINE of the following:

18

- State any two advantages of three phase system over single phase system.
- State Ohm's law.
- Define power and energy.
- State the necessity of starter.
- List the various parts of dc machine.
- Write working principle of dc motor.
- What is ideal transformer? How it differs form practical transformer?
- State the need of earthing.
- Give classifications of transformer according to their construction.

P.T.O.

- j) List the different types of wire used in electrical wiring.
- k) A transformer does not operate on a d.c supply. State reason.
- l) Write two safety precautions to be taken while handling an electrical equipments.

2. Attempt any FOUR of the following: 16

- a) State working principle of MCCB. State its two applications.
- b) For 12 kVA, 440 V/220 V, 50 Hz, 1 ϕ transformer, find:
 - (i) Primary current
 - (ii) Secondary current
 - (iii) Turns ratio and
 - (iv) No. of turns on primary side
- c) With neat construction explain working of R-split type of induction motor.
- d) Compare squirrel cage and slip ring type three phase induction motor (any four points).
- e) State any four parts and their materials used for three phase induction motor.
- f) What is the importance of improvement in power factor? State any two methods for power factor improvement.

3. Attempt any FOUR of the following: 16

- a) A furnace takes a current of 10 Amp from a 220 V, dc supply for eight hours. Calculate the energy consumed in kWh.
- b) State the function of no volt coil and overload coil in case of DC shunt motor starter.
- c) Describe the operation of mercury vapour lamp with neat connection diagram.
- d) Draw neat diagrams explain plate earthing.
- e) Differentiate between two winding transformer with auto transformer (any four points).
- f) Describe with a circuit diagram, the operation of capacitor start induction run single phase induction motor.

SECTION - II

- 4. Attempt any NINE of the following: 18**
- a) Define doping.
 - b) Draw symbol of P-N junction diode and give one application of the same.
 - c) What is breakdown in diodes? State its types.
 - d) Draw symbol of following with all indications:
 - (i) PNP transistor
 - (ii) NPN transistor
 - e) Enlist the applications of transistor.
 - f) Define filter.
 - g) Enlist the types of filter.
 - h) Define voltage regulator.
 - i) State truth table of two input Ex-OR gate.
 - j) Draw symbol of light emitting diode. State any two applications of LED's.
 - k) What is mean by positive logic.
 - l) Give important applications of SCR.
- 5. Attempt any FOUR of the following: 16**
- a) Describe the operation of zener diode and draw its V-I characteristics.
 - b) Enlist the applications of following:
 - (i) Resistor
 - (ii) Inductor
 - c) State De-morgan's second theorem and prove it with the help of truth table.
 - d) Draw and describe input and output characteristics of transistor in common emitter mode.
 - e) Compare half wave and full wave centre tapped type rectifier.
 - f) Explain bridge rectifier with the help of diagram.

6. Attempt any FOUR of the following:

16

- a) Explain with the help of diagram:
 - (i) conductors
 - (ii) semiconductors
- b) Describe the working of TRIAC with the help of a neat sketch. Also state its two applications.
- c) Compare intrinsic and extrinsic semiconductors.
- d) Draw the symbol, logical expression and truth table of AND and NAND gate.
- e) Explain block diagram of power supply in detail.
- f) Identify the circuit and explain it in detail. (Refer Fig. No. 1)

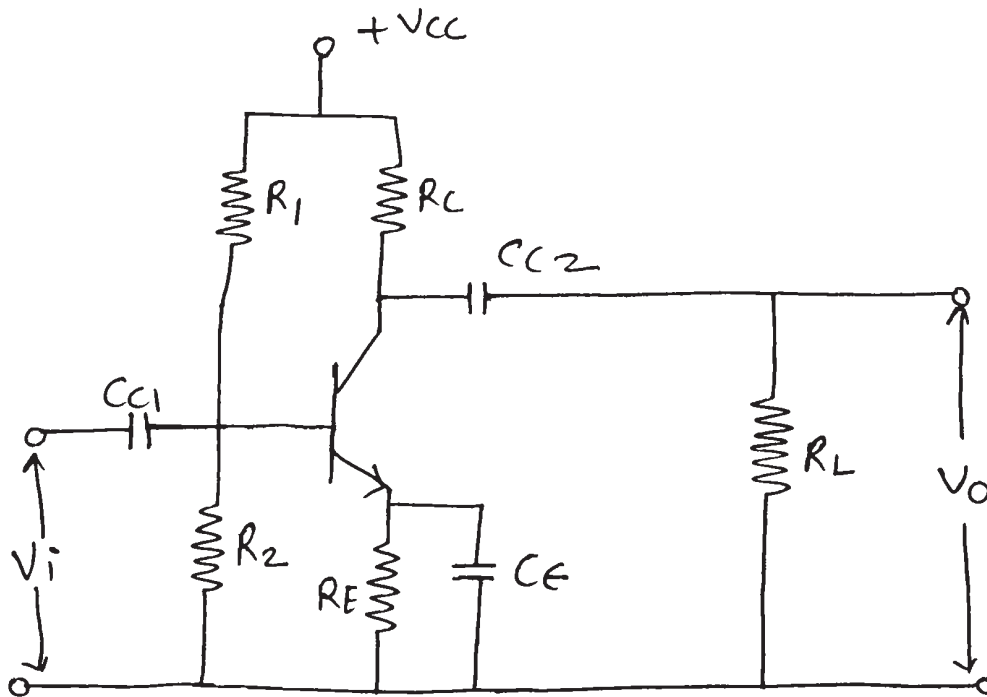


Fig. No. 1
