

# 17215

14115

3 Hours / 100 Marks


Seat No.

--	--	--	--	--	--	--	--

- Instructions* – (1) All Questions are *Compulsory*.  
(2) Illustrate your answers with neat sketches wherever necessary.  
(3) Figures to the right indicates full marks.  
(4) Assume suitable data, if necessary.

**Marks**

1. **Attempt any TEN of the following :** **20**
- State the Faraday's law of Electromagnetic induction along with formula.
  - Draw a label diagram of ferrite core inductor.
  - State the specifications of capacitor.
  - Draw the circuit diagram of bridge rectifier and label it.
  - List the types of filters.
  - Draw the ideal and practical voltage source.
  - State the Kirchoff's voltage law.
  - Calculate the current through  $10\ \Omega$  resistor –

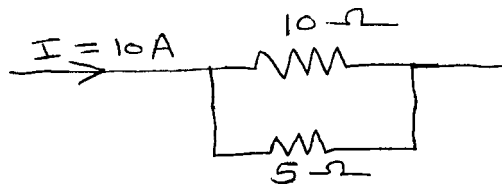

**Fig. No. 1**

P.T.O.

- i) Draw the symbol of schottky diode and tunnel diode.
- j) State four application of PIN diode.
- k) Draw RC integrator and differentiator.
- l) Draw the circuit diagram of clipper.

**2. Attempt any FOUR of the following : 16**

- a) Explain the working of TDR along with its symbol and characteristics.
- b) List the specifications of linear and nonlinear potentiometers. State its applications (Four points)
- c) Draw the constructional diagram of electrolytic capacitor. Explain the working.
- d) List the classification of capacitor. Which type of dielectric materials used in capacitor.
- e) Draw the construction diagram of air core inductor. List two applications.
- f) Draw the V-I characteristics of P-N junction diode.  
What is static and dynamic resistance of it ?

**3. Attempt any FOUR of the following : 16**

- a) Explain with neat sketch construction of PIN diode. Draw its characteristics in reverse bias mode.
- b) Describe the working of tunnel diode. Draw its characteristics.
- c) Describe the working principle of laser diode.
- d) Explain the working of schottky diode.
- e) Compare L, C, LC and  $\pi$  filter on the basis of – usefulness in reducing ripple or suitability for heavy / light load.

- f) State the values of following parameters with reference to full wave rectifier.
- (i) Ripple factor
  - (ii) Efficiency
  - (iii) TUF
  - (iv) PIV

**4. Attempt any FOUR of the following :**

**16**

- a) Draw the circuit diagram of full wave rectifier with filter. State any four advantages.
- b) Using colour code, write the colour codes for the following resistors –
  - (i) 680 K  $\Omega$ ,  $\pm 5\%$
  - (ii) 3.3  $\Omega$ ,  $\pm 10\%$
- c) State the advantages of L and C. filter. (Four points)
- d) An AC supply of 230V is applied to HWR through a transformer with turns ratio 10 : 1. Find DC output voltage and PIV of diode.
- e) Compare PN junction diode and zener diode. (Four points)
- f) Compare zener breakdown and avalanche breakdown. (Four points)

5. Attempt any **FOUR** of the following :


16

- a) What is linear and nonlinear waveshaping circuit ?
- b) Draw the circuit diagram of negative clamper.  
Write one application of negative and positive clamper.
- c) Explain the following terms –
  - (i) Bilateral Network
  - (ii) Linear Network
- d) Draw the output waveforms of RC Integrator for square wave and triangular wave as input signal.
- e) State the superposition theorem.
- f) Draw the star and delta connection. State any one conversion formula.
- g) Explain the working principle of slug tuned inductor.

6. Attempt any **FOUR** of the following :

16

- a) Draw the output waveform, when a sinewave is applied to following circuits –
  - (i)
  - (ii)

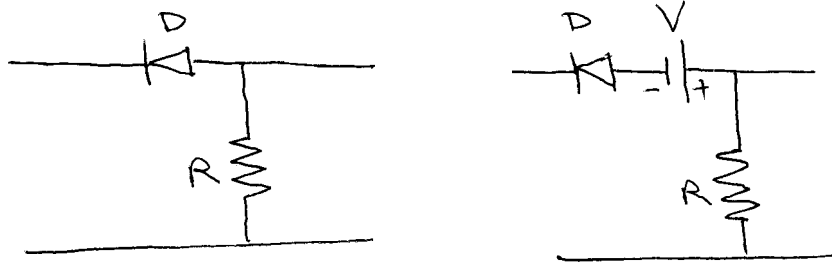

**Fig. No. 2**


- b) Compare clipper and clamper.
- c) Define following terms –
  - (i) Active networks
  - (ii) Unilateral networks

17215

[ 5 ]


**Marks**

- d) Calculate  $I_L$  for the network shown in Figure No.3.

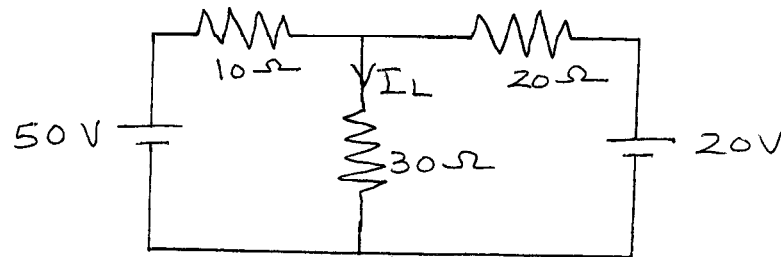

**Fig. No. 3**

- e) Find the value of load resistance  $R_L$  to get maximum power transferred to it. Refer Figure No.4.

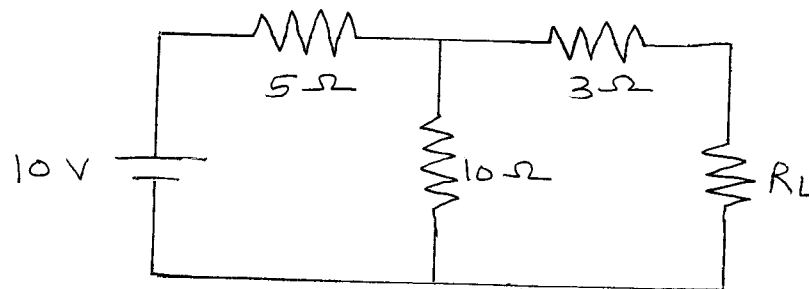

**Fig. No. 4**

- f) State Norton's theorem with suitable example.

\_\_\_\_\_