



17319

16117

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) *All questions are compulsory.*
 - (2) *Illustrate your answers with neat sketches wherever necessary.*
 - (3) *Figures to the right indicate full marks.*
 - (4) *Assume suitable data, if necessary.*
 - (5) *Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.*

Marks

1. A) Attempt **any six** of the following : **12**
- a) Draw symbol of NPN and PNP transistor.
 - b) What are different types of amplifier coupling ?
 - c) Define intrinsic stand off ratio for UJT.
 - d) List various transistor biasing methods.
 - e) State the effect of VGS on channel conductivity on N-channel JFET.
 - f) What is thermal runaway ? How it can be avoided ?
 - g) State the need of regulator.
 - h) State the conditions for sustained oscillations.
- B) Attempt **any two** : **8**
- a) Draw the output characteristics of common emitter configuration. What is the effect of base current I_B on collector current I_C with reference to characteristics ?
 - b) Draw the circuit diagram of voltage divider biasing method of BJT. How stability in operating point is obtained ?
 - c) Draw circuit diagram of transistorized series voltage regulator and explain its working.
2. Attempt **any four** : **16**
- a) With the help of neat circuit diagram, explain the working of fixed bias method for BJT.
 - b) Describe the working principle of N-channel JFET with diagram.
 - c) Draw transistor as switch. What is voltage across transistor (V_{CE}) and current through transistor (I_C) when transistor is ON and OFF ?
 - d) Draw block diagram of voltage shunt and voltage series feedback.
 - e) Draw the block diagram of regulated power supply. Write the function of each block.

P.T.O.

**3. Attempt any four :****16**

- a) Compare CB, CE, CC configuration of BJT with reference to following points.
 - i) Input impedance
 - ii) Output impedance
 - iii) Current gain
 - iv) Voltage gain.
- b) With the help of neat circuit diagram, explain the working of self bias method for FET.
- c) Draw circuit diagram of UJT Relaxation Oscillator and describe its working principle.
- d) Draw circuit diagram of two stage RC coupled amplifier. State the need of multistage amplifier.
- e) Draw and describe working of Zener diode as voltage regulator.
- f) Sketch pin diagram of IC 723. Give any four advantages of IC voltage regulator over discrete voltage regulator.

4. Attempt any four :**16**

- a) Draw transfer and drain characteristics of JFET. Give relation between μ , r , d .
- b) Draw the circuit diagram of double tuned amplifier and describe its working.
- c) Explain the working of N-channel E-MOSFET.
- d) Explain class B push-pull amplifier with neat diagram.
- e) Differentiate between class A and class B amplifier on the following basis.
 - i) Position of Q points on load line
 - ii) Distortion in output voltage
 - iii) Collector current waveform
 - iv) Efficiency.
- f) Describe working of bootstrap time base generator with circuit diagram.

5. Attempt any four :**16**

- a) Define α , β with respect to transistor configuration. State the relation between α and β .
- b) For RC phase shift oscillator the components values are as follows : $R = 8.2 \text{ k}\Omega$, $C = 0.01 \mu\text{f}$, $R_1 = 1.2 \text{ k}\Omega$, $R_F = 39 \text{ k}\Omega$. What will be the frequency of oscillation ?
- c) Draw the circuit diagram of single stage class A power amplifier and describe its working.
- d) How FET can be used as an amplifier ? Explain with neat sketch.
- e) Draw the circuit diagram of crystal oscillator, and give the basic principle of Piezoelectric crystal.
- f) Draw Miller sweep generator and give any two applications.



[3]

17319

Marks

6. Attempt **any four** :

16

- a) In CE configuration if $\beta = 98$, leakage current $I_{CEO} = 50 \mu\text{A}$. If base current is 0.5 mA. Determine I_C and I_E .
 - b) Distinguish between series and shunt voltage regulator (any four points)
 - c) State the effect of negative feedback on following parameter
 - i) Bandwidth
 - ii) Noise
 - iii) Gain
 - iv) Distortion
 - d) Draw circuit diagram of two stage transformer coupled amplifier. Draw its frequency response.
 - e) Sketch neat labelled VI characteristics of unijunction transistor.
 - f) Draw circuit diagram of single stage CE amplifier and state function of each component.
-