

EXPERIMENT NO.9

TITLE: OP-AMP AS SCHMITT TRIGGER.**OBJECTIVES:**

1. To assemble the circuit of SCHMITT TRIGGER using op-amp IC 741 in inverting configuration.
2. To observe and plot the output voltage waveform of SCHMITT TRIGGER.

LAB REQUIREMENTS:

Breadboard, Op-amp IC 741, Resistor (R1 & R2), DC regulated Dual power supply (0-30V), Function Generator, CRO/DSO and connecting wires/Probes.

CIRCUIT DIAGRAM:**THEORY:**

SCHMITT TRIGGER is a circuit which converts irregular shaped waveform into square or pulse. This circuit is also called as squaring circuit. Above circuit shows an inverting comparator with positive feedback. The input v_{in} triggers (change of state) output v_o every time it exceeds certain voltage levels called as upper threshold voltage v_{ut} and lower threshold voltage v_{lt} .

These voltage levels are obtained by voltage divider R1-R2 where voltage across R1 is fed back to the (+) input. The voltage across R1 is the variable reference voltage that depends upon the value and polarity of output voltage v_o . When $v_o = +V_{sat}$, voltage across R1 is called as upper threshold voltage v_{ut} . The input voltage v_{in} must be slightly

more positive than v_{ut} in order to cause the output v_o to switch from $+V_{sat}$ to $-V_{sat}$. As long as $v_{in} < V_{ut}$, $v_o = +V_{sat}$. Using voltage divider rule,

$$V_{ut} = \frac{R_1}{R_1 + R_2} \cdot (+V_{sat})$$

On the other hand, When $v_o = -V_{sat}$, voltage across R1 is called as lower threshold voltage v_{lt} . The input voltage v_{in} must be slightly more negative than v_{lt} in order to cause the output v_o to switch from $-V_{sat}$ to $+V_{sat}$. As long as $v_{in} > V_{lt}$, $v_o = -V_{sat}$. Using voltage divider rule,

$$V_{lt} = \frac{R_1}{R_1 + R_2} \cdot (-V_{sat})$$

Output of Schmitt trigger is square wave when input is sine wave. This circuit is said to exhibit the phenomenon known as hysteresis. Hysteresis is the property of the system where output value incorporates some lag, delay or history dependence.

EXPERIMENTAL PROCEDURE:

1. Refer the Pin Diagram of op-amp IC741 & assemble the SCHMITT TRIGGER circuit in inverting configuration of op-amp as per circuit diagram on the breadboard.
2. Set the DC power supply to provide $+V_{CC}$ & $-V_{EE}$ by making necessary adjustment & Apply V_{CC} & $V_{EE} = \pm 15V$ at respective pins of op-amp IC 741.
3. Set the function generator to provide 2V (p-p) sine wave at 500HZ & Apply this AC input at pin 2 (INV) of op-amp IC741.
4. Observe the output of this circuit on CRO/DSO.
5. Measure the output voltage swing, V_{ut} & V_{lt} . Note the readings in the observation table.
6. Plot the output voltage waveforms for v_{in} , V_{ut} & V_{lt} .

OBSERVATION TABLE:

Sr. No.	Input Signal Voltage (V_{in}) p-p	Input Signal Frequency (Hz)	R1 $K\Omega$	R2 $K\Omega$	V_{ut} (Volts)	V_{It} (Volts)	Output Voltage Swing (p-p)
1							

CALCULATIONS:(Calculations for V_{ut} & V_{It})**RESULT:**

1. Circuit of SCHMITT TRIGGER using op-amp IC 741 has been assembled in _____ configuration of op-amp with input _____ wave signal set at _____ amplitude & _____ frequency.
2. It has been observed from the output waveform that output is _____ wave for _____ wave input.
3. The input v_{in} triggers output v_o every time it exceeds certain voltage levels called as _____ and _____.

EVALUATION (BY TEACHER):

Excellent/Good/Average/Poor