



LAB MANUAL

Electronic Circuit Simulation

(EC-516-F)

V SEMESTER ECS

*Department of Electronics & Communication Engg.
Dronacharya College of Engineering
Khentawas, Gurgaon – 123506*


LIST OF EXPERIMENTS

1. Simulate and study V-I characteristics of a Diode using PSPICE windows.
2. Simulate and study Half-wave and Full-wave Rectifier using PSPICE windows
3. Simulate and study Diode Clipper and Clamper circuit using PSPICE windows.
4. Simulate and study V-I characteristics of a NPN-BJT using PSPICE windows.
5. Simulate and study Darlington pair amplifier circuit using PSPICE windows and determine quiescent condition.
6. Simulate and study transient & frequency response of a BJT amplifier in common-emitter configuration using PSPICE windows.
7. Simulate and study active low-pass, high-pass & band-pass filter using PSPICE windows.
8. Simulate and study Integrator using PSPICE windows.
9. Simulate and study Differentiator using PSPICE windows.
10. Simulate and study basic AND, OR, NOT, NOR, NAND, EX-OR gates using PSPICE windows.

EXPERIMENT NO 1

AIM: Simulate and study V-I characteristics of a Diode using PSPICE windows.


CIRCUIT DIAGRAM:

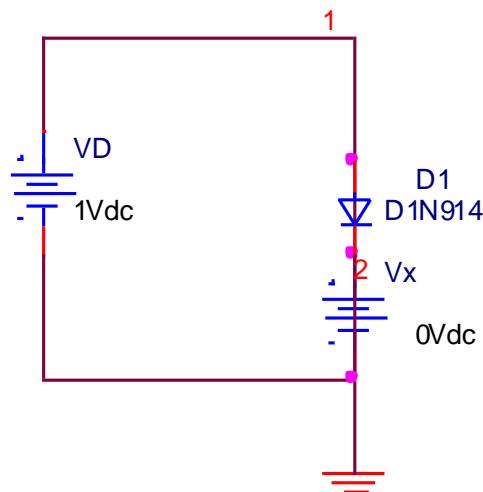

PROGRAM:

```
vd 1 0 dc 1v  
d1 1 2 d1n914;  
vx 2 0 dc 0v;  
.model D1N914  D(Is=168.1E-21 N=1 Rs=.1 Ikf=0 Xti=3 Eg=1.11 Cjo=4p M=.3333  
+      Vj=.75 Fc=.5 Isr=100p Nr=2 Bv=100 Ibv=100u Tt=11.54n)  
.dc vd 0 1v 0.01v;  
  
.plot dc I(vx);  
.probe;  
.tran 0us 100us;  
.end;
```

RESULT:


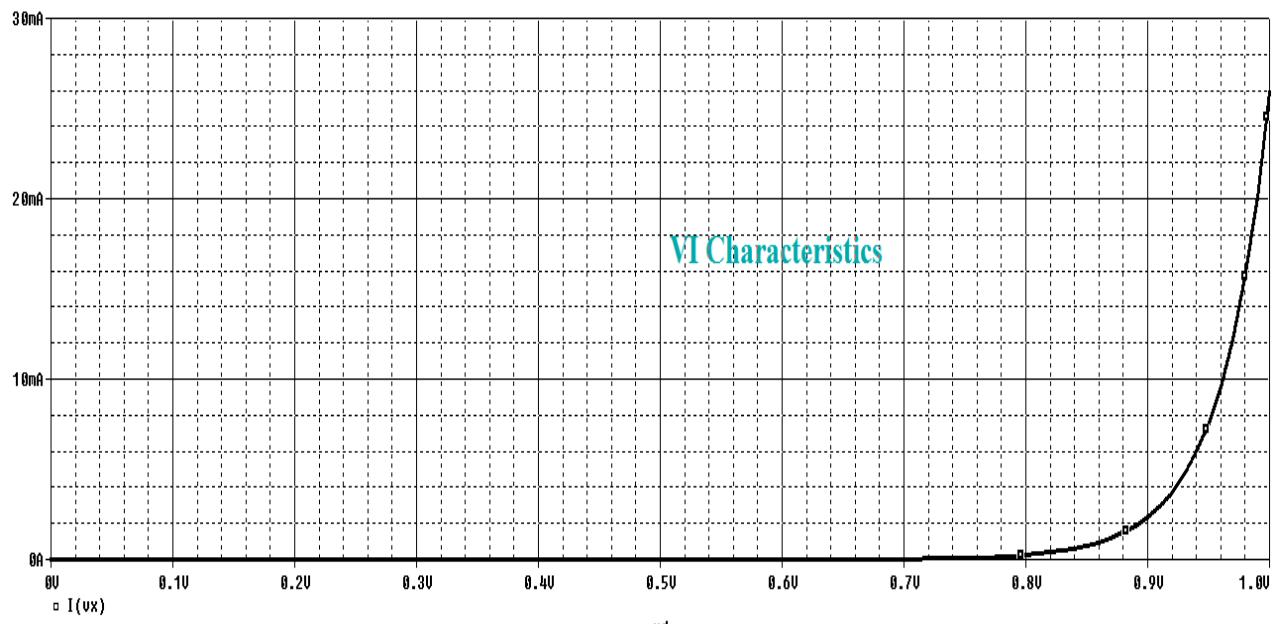


CONCLUSION: The forward biased silicon diode in an electronic system under dc condition has a drop of 0.7v across it in conduction state at any value of diode current.

EXPERIMENT NO 2

AIM: Simulate and study Half-wave and Full-wave Rectifier using PSPICE windows.

CIRCUIT DIAGRAM:

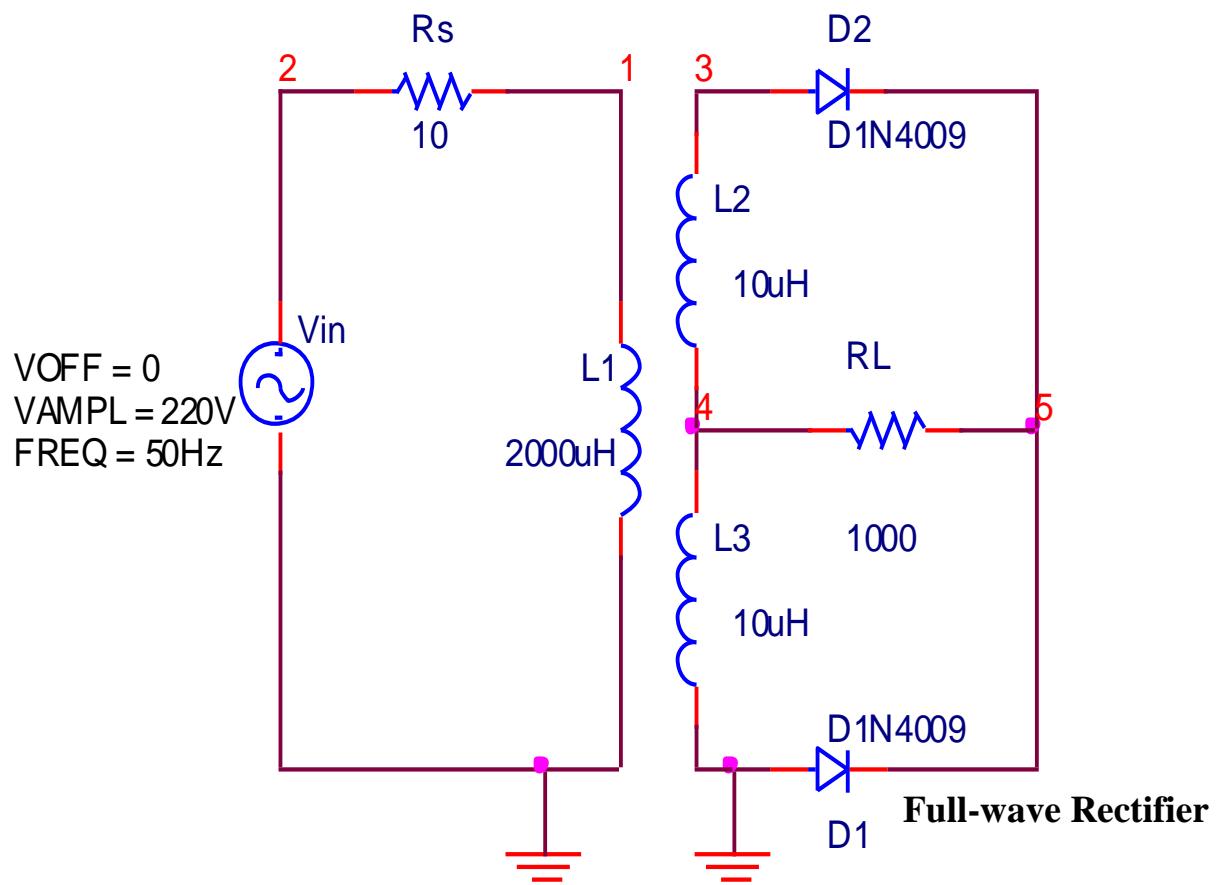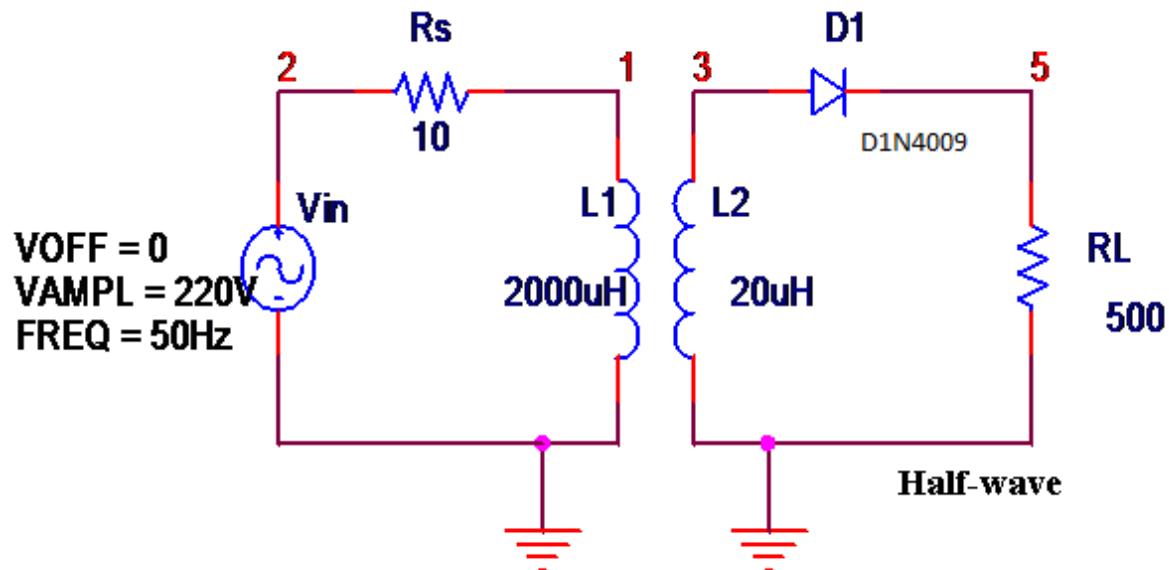

PROGRAM:

*HALF WAVE rectifier

VIN 2 0 sin(0 220V 50HZ)

RL 5 0 500

RS 2 1 10

L1 1 0 2000uH

L2 3 0 20uH

K1 L1 L2 0.99999

D1 3 5 D1N4009

```
.model D1N4009 D(Is=544.7E-21 N=1 Rs=.1 Ikf=0 Xti=3 Eg=1.11 Cjo=4p M=.3333
+ Vj=.75 Fc=.5 Isr=30.77n Nr=2 Bv=25 Ibv=100u Tt=2.885n)
```

.tran 0.2m 200m

.plot tran v(3), v(5)

.probe

.end

***FULL WAVE rectifier**

Vin 2 0 sin(0 230V 50HZ)

RL 5 4 1000

RS 2 1 10

L1 1 0 2000

L2 3 4 10

L3 4 0 10


K1 L1 L2 L3 0.99

D1 0 5 D1N4009


D2 3 5 D1N4009

```
.model D1N4009
D(Is=544.7E-21 N=1 Rs=.1 Ikf=0 Xti=3 Eg=1.11 Cjo=4p M=.3333
+      Vj=.75 Fc=.5 Isr=30.77n Nr=2 Bv=25 Ibv=100u Tt=2.885n)
.tran 0.2ms 200ms
.probe
.end
```

RESULT:

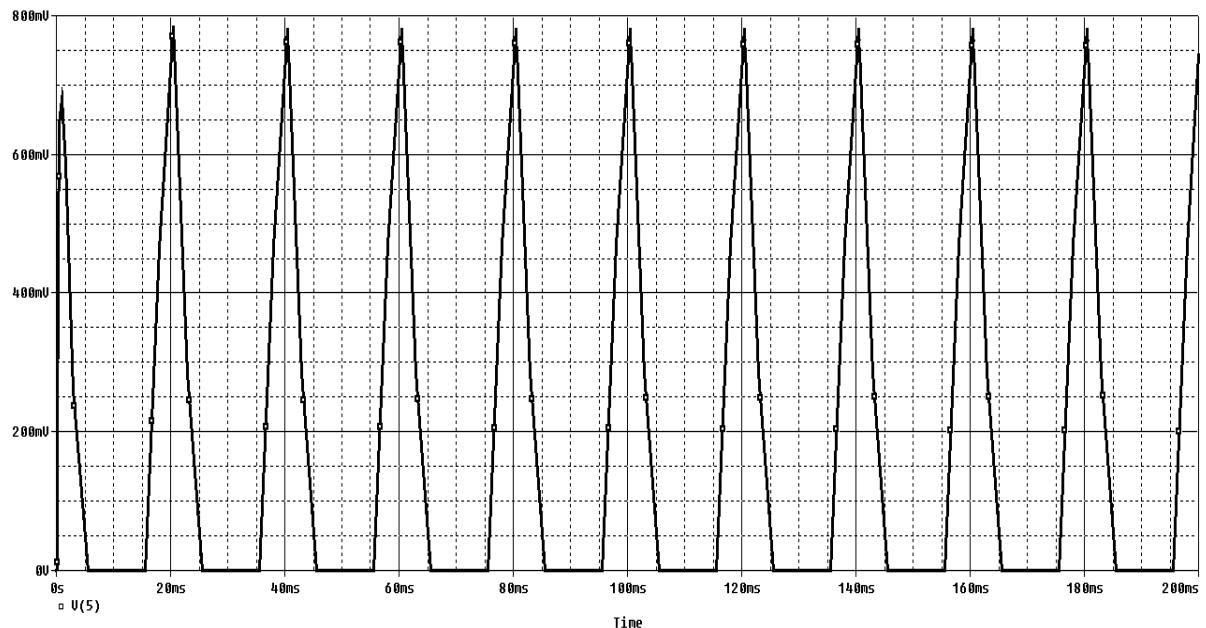

HALF-WAVE RECTIFIER

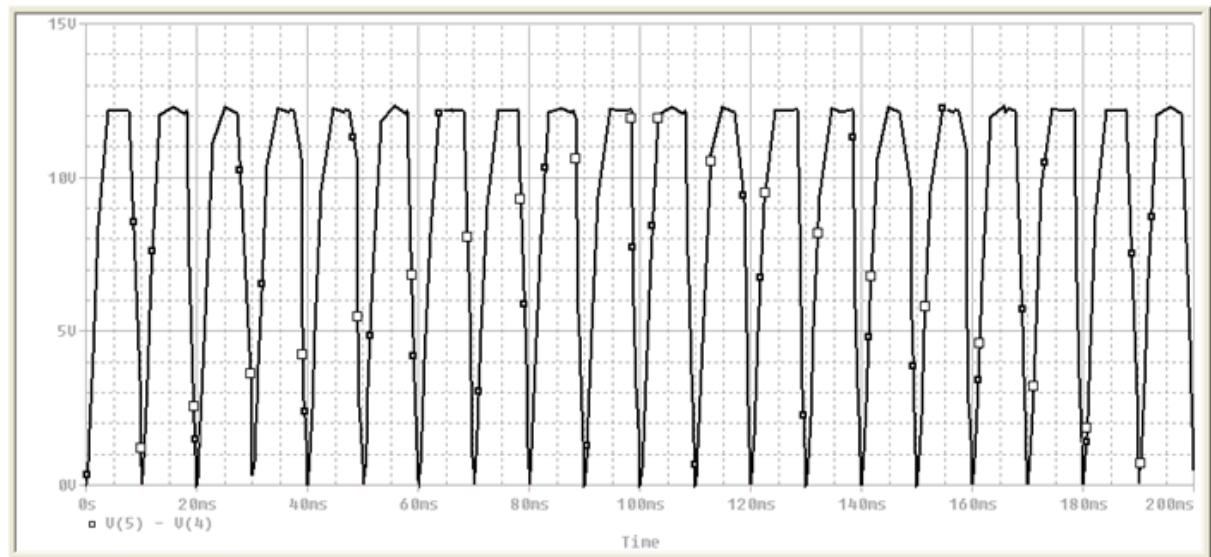

FULL WAVE RECTIFIER


CONCLUSION: We are able to visualise the expected output of Half-wave and Full-wave Rectifier circuit as given in theory.

EXPERIMENT NO 3


AIM: Simulate and study Diode Clipper and Clamper circuit using PSPICE windows.

CIRCUIT DIAGRAM:

Clipper Circuit-

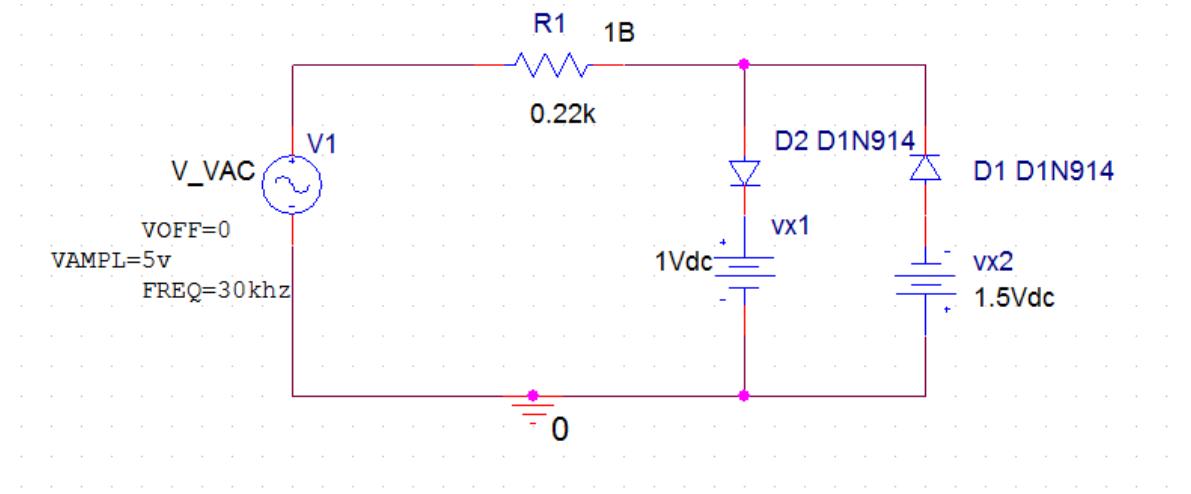

Clamper Circuit-

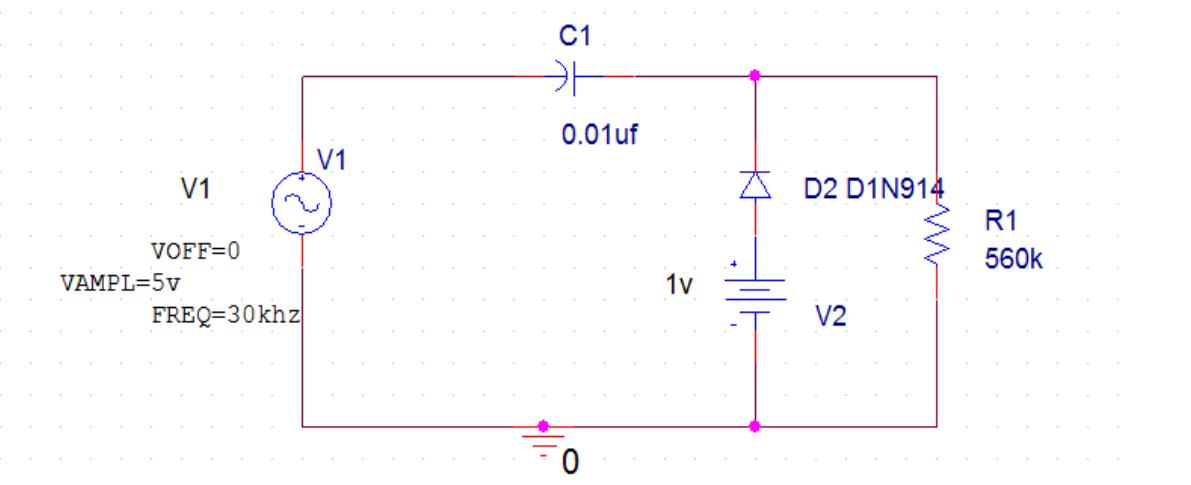

PROGRAM:

```
*CLIPPER CIRCUIT

V_VAC 1 0 sin(0 5v 30khz);

r1 1 2 0.22k;

d1 2 3 D1N914;

d2 4 2 D1N914;

vx1 3 0 dc 1v;

vx2 0 4 dc 1.5v;

.model D1N914 D(Is=168.1E-21 N=1 Rs=.1 Ikf=0 Xti=3 Eg=1.11 Cjo=4p M=.3333
+      Vj=.75 Fc=.5 Isr=100p Nr=2 Bv=100 Ibv=100u Tt=11.54n)

.probe;

.tran 0us 100us;

.end;
```

***CLAMPER CIRCUIT**

```
V1 1 0 sin(0 5v 30khz);

c1 1 2 0.01u;

d1 3 2 D1N914;

r1 2 0 560k;



v2 3 0 1v;

.model D1N914 D(Is=168.1E-21 N=1 Rs=.1 Ikf=0 Xti=3 Eg=1.11 Cjo=4p M=.3333
+      Vj=.75 Fc=.5 Isr=100p Nr=2 Bv=100 Ibv=100u Tt=11.54n)

.probe;

.tran 0us 100us;

.end;
```

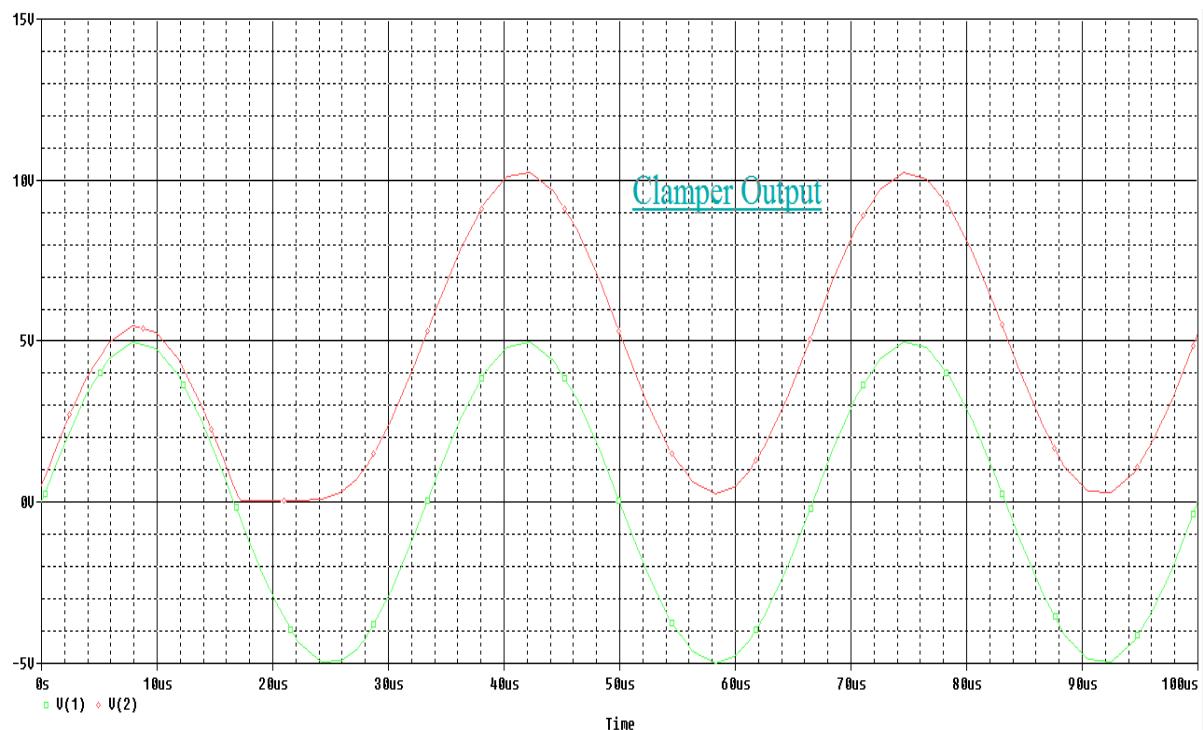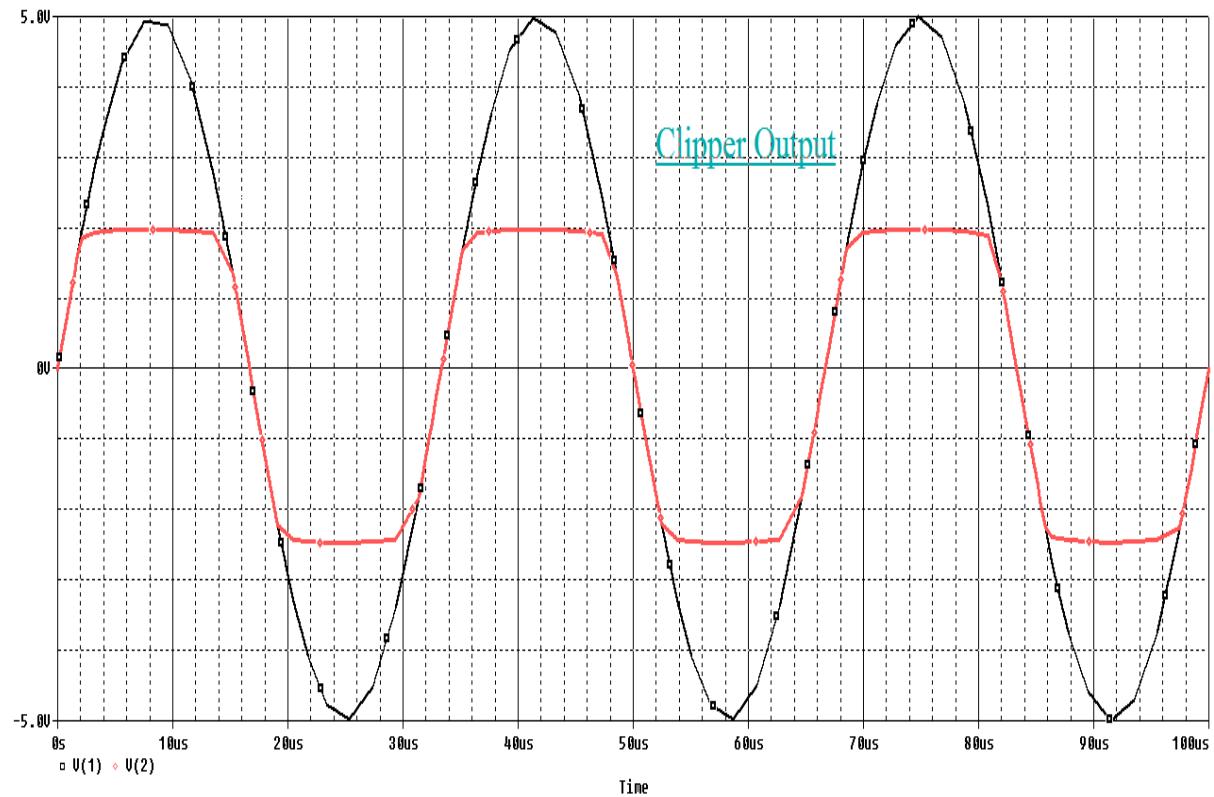
RESULT:

CONCLUSION: We are able to visualise the expected output of Clipper Circuit and Clamper Circuit as given in theory.

EXPERIMENT NO 4

AIM: Simulate and study V-I characteristics of a NPN-BJT using PSPICE windows.

CIRCUIT DIAGRAM:

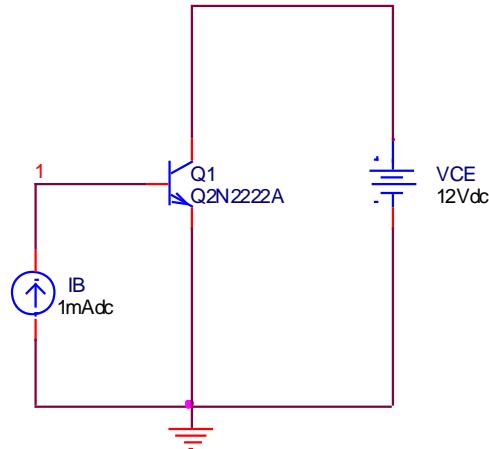

PROGRAM:

* NPN-BJT CHARACTERISTICS

IB 0 1 DC 1MA

VCE 2 0 DC 12V

Q1 2 1 0 Q2N2222A *Tools – Pspice - Library - Bipolar

.MODEL Q2N2222A NPN (IS=2.105E-16 BF=173 VA=83.3V CJE=29.6PF CJC=19.4PF

+ TF=489.88PS TR=4.9NS)


.DC VCE 0 10V 0.02V IB 0 1MA 200UA

.PROBE

.OP

.END

RESULT:

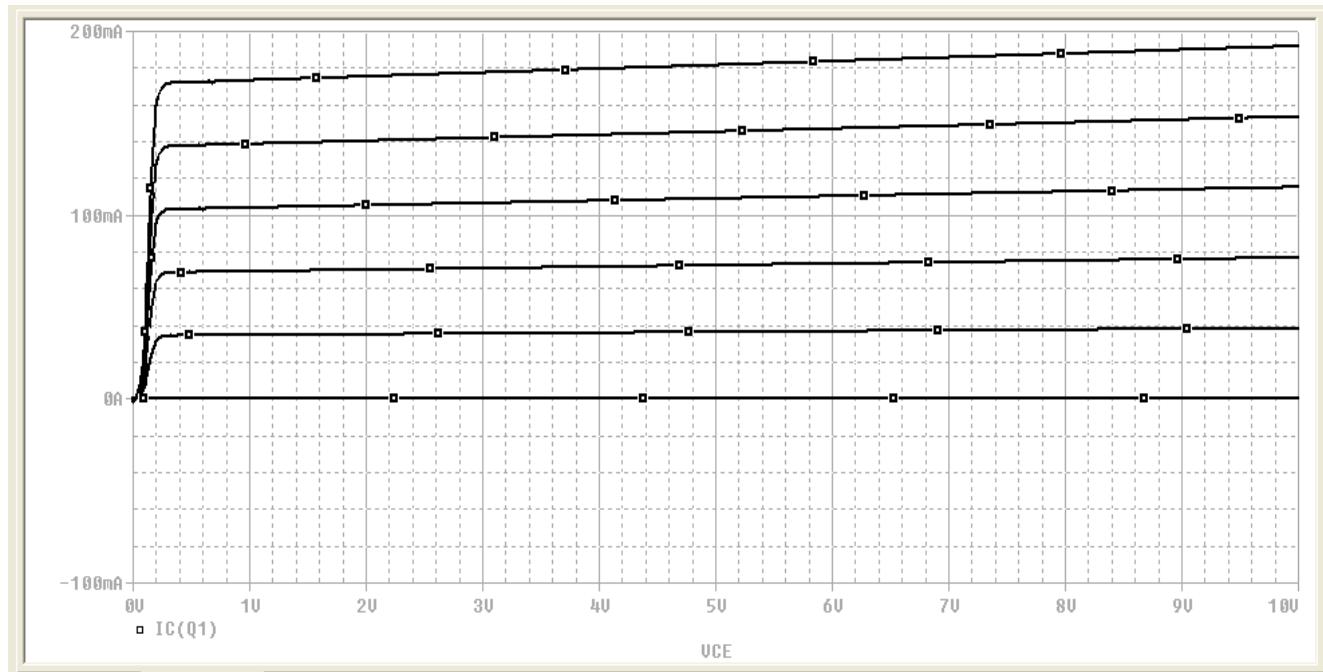


CONCLUSION: We are able to visualise the expected output of NPN-BJT circuit as given in theory.

EXPERIMENT NO 5

AIM: Simulate and study Darlington pair amplifier circuit using PSPICE windows and determine quiescent condition.

CIRCUIT DIAGRAM:

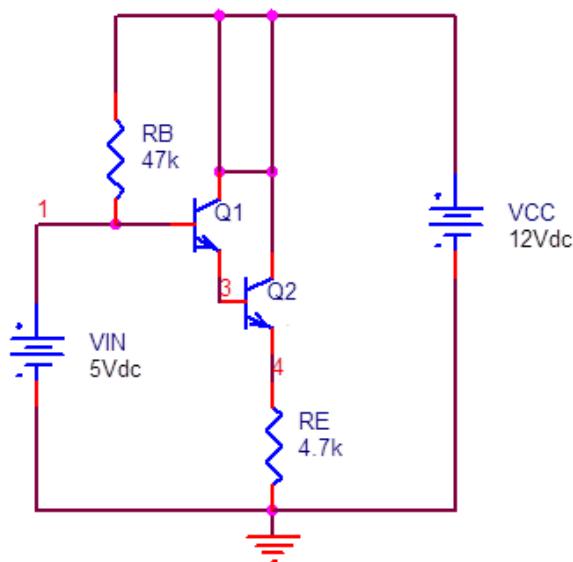

PROGRAM:

VCC 2 0 DC 12V

VIN 1 0 DC 5V

Q1 2 1 3 Q2N2484 * BJTs with model (Q2N2484)

Q2 2 3 4 Q2N2484

RB 2 1 47k

RE 4 0 4.7K

* Model Q2N2484 for NPN BJTs

.model Q2N2484 NPN(Is=5.911f Xti=3 Eg=1.11 Vaf=62.37 Bf=697.1 Ne=1.342
+ Ise=5.911f Ikf=13.93m Xtb=1.5 Br=1.297 Nc=2 Isc=0 Ikr=0 Rc=1.61
+ Cjc=4.017p Mjc=.3174 Vjc=.75 Fc=.5 Cje=4.973p Mje=.4146 Vje=.75
+ Tr=4.687n Tf=820.4p Itf=.35 Vtf=4 Xtf=7 Rb=10)

* Transfer function analysis to calculate dc gain, input resistance and output resistance

.TF V(4) VIN

.END

RESULT:

**** 11/11/13 09:10:06 ***** PSpice Lite (April 2011) ***** ID# 10813 ****

**** Darlington Pair

**** SMALL SIGNAL BIAS SOLUTION TEMPERATURE = 27.000 DEG C

NODE VOLTAGE NODE VOLTAGE NODE VOLTAGE NODE VOLTAGE

(1) 5.0000 (2) 12.0000 (3) 4.3560 (4) 3.5909

VOLTAGE SOURCE CURRENTS

NAME CURRENT

VCC -9.129E-04

VIN 1.489E-04

TOTAL POWER DISSIPATION 1.02E-02 WATTS

**** SMALL-SIGNAL CHARACTERISTICS

V(4)/VIN = 9.851E-01

INPUT RESISTANCE AT VIN = 4.696E+04

OUTPUT RESISTANCE AT V(4) = 6.677E+01

JOB CONCLUDED

**** 11/11/13 09:10:06 ***** PSpice Lite (April 2011) ***** ID# 10813 ****

**** Darlington Pair


**** JOB STATISTICS SUMMARY

Total job time (using Solver 1) = 0.00

EXPERIMENT NO 6

AIM: Simulate and study transient & frequency response of a BJT amplifier in common-emitter configuration using PSPICE windows.

CIRCUIT DIAGRAM:


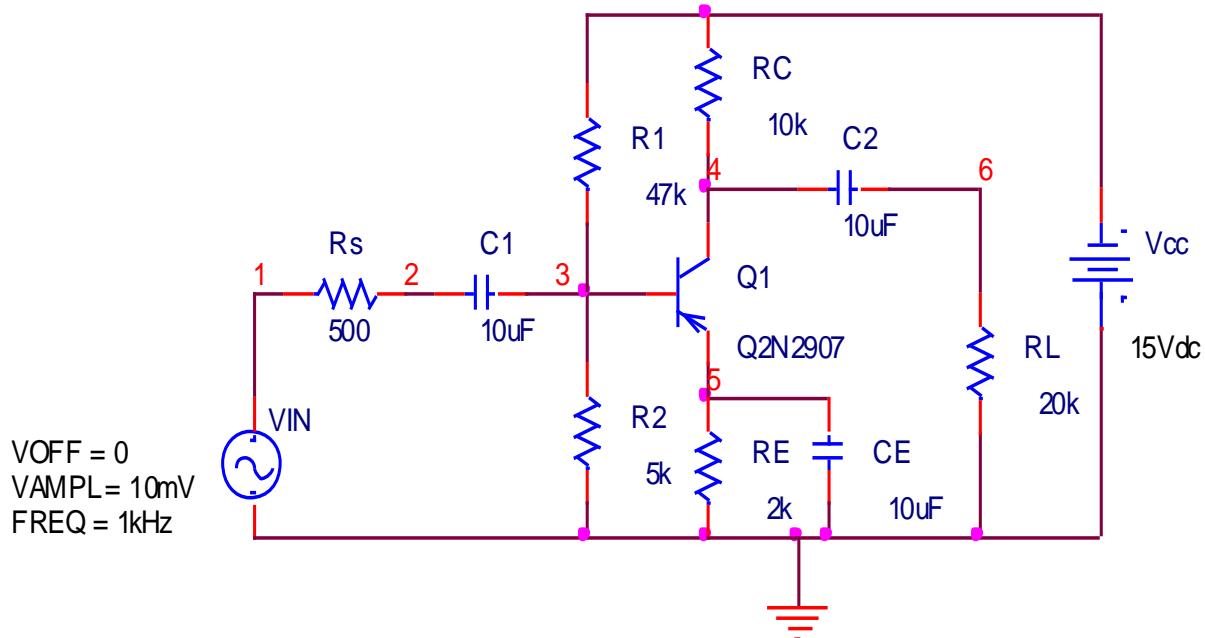


PROGRAM:

```
*  
.AC DEC 10 1hz 10khz;  
VIN 1 0 AC 10mv sin(0 10mv 1khz);  
VCC 0 7 DC 15v;  
RS 1 2 500;  
R1 7 3 47k;  
R2 3 0 5k;  
RC 7 4 10k;  
RE 5 0 2k;  
RL 6 0 20k;  
C1 2 3 10uF;
```

```
C2 4 6 10uF;  
CE 5 0 10uF;  
Q1 4 3 5 0 Q2N2907;  
.model Q2N2907      PNP(Is=650.6E-18 Xti=3 Eg=1.11 Vaf=115.7 Bf=231.7 Ne=1.829  
+          Ise=54.81f Ikf=1.079 Xtb=1.5 Br=3.563 Nc=2 Isc=0 Ikr=0 Rc=.715  
+          Cjc=14.76p Mjc=.5383 Vjc=.75 Fc=.5 Cje=19.82p Mje=.3357 Vje=.75  
+          Tr=111.3n Tf=603.7p Itf=.65 Vtf=5 Xtf=1.7 Rb=10)  
*          National      pid=63      case=TO18  
*          88-09-09 bam creation  
.tran 50us 2ms;  
.plot tran V(4) V(6) V(1);  
.plot AC VM(6) VP(6);  
.probe;  
.end;
```

RESULT:

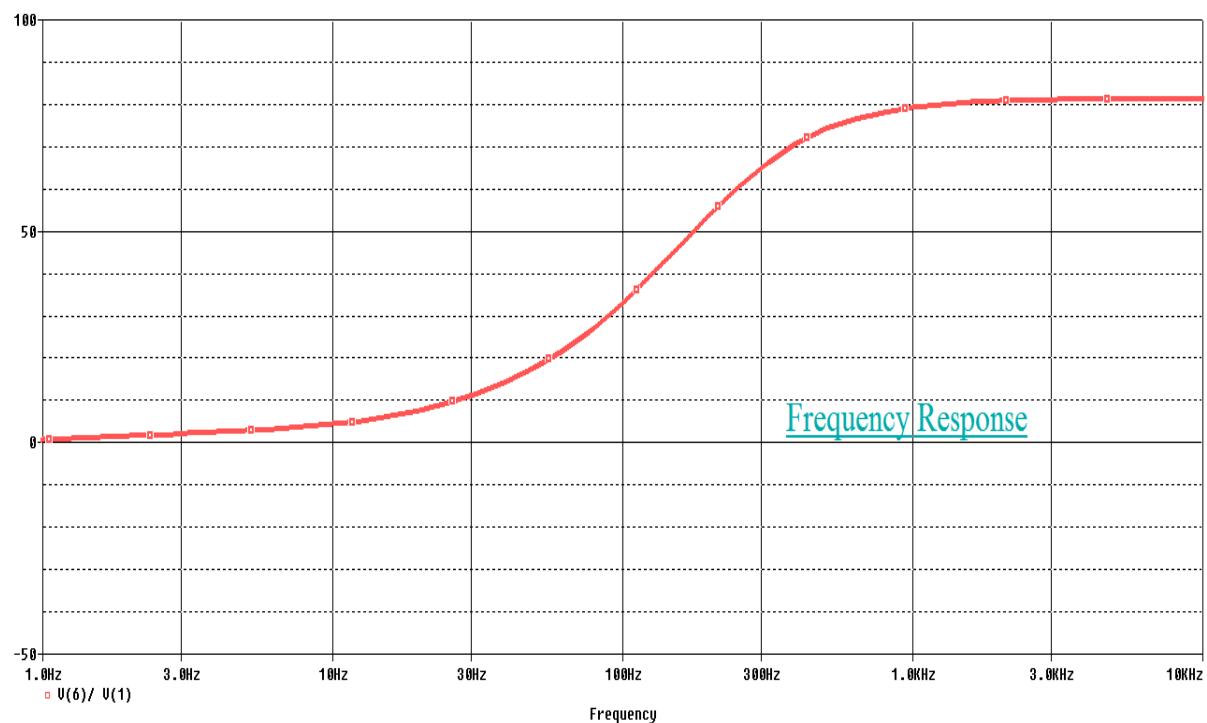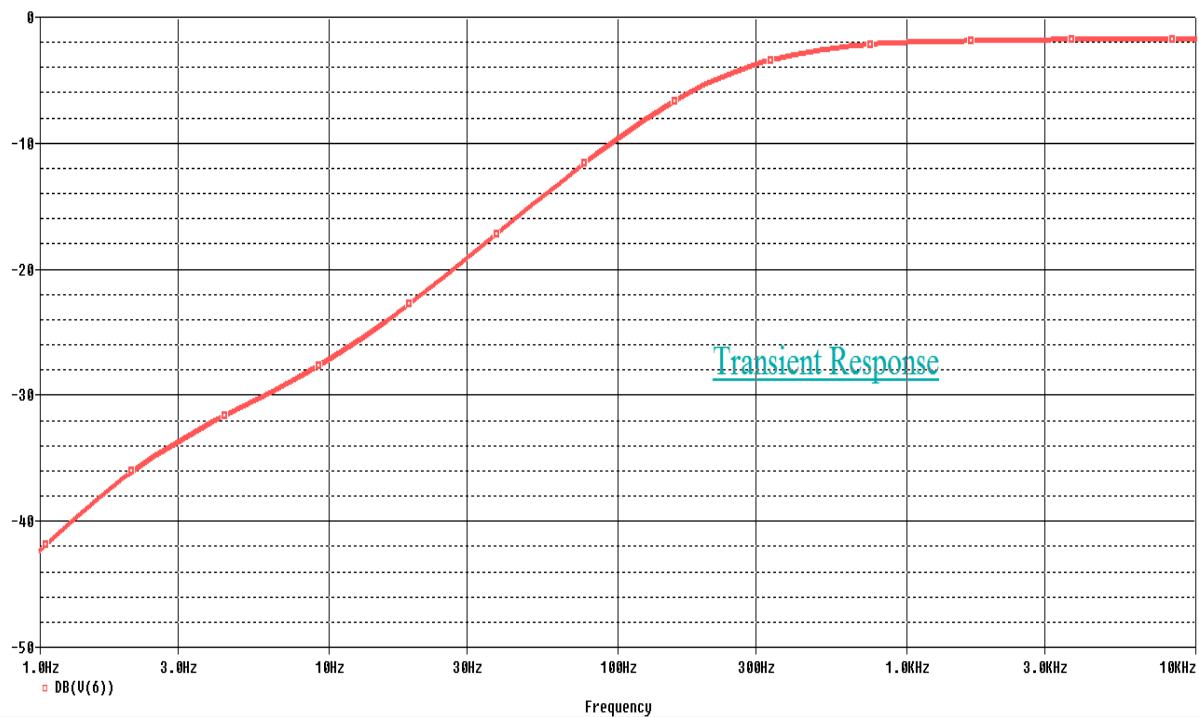


CONCLUSION: We are able to visualise the expected output of transient & frequency response of a BJT amplifier in common-emitter configuration as given in theory.


EXPERIMENT NO 7

AIM: Simulate and study active low-pass, high-pass & band-pass filter using PSPICE windows.


CIRCUIT DIAGRAM:

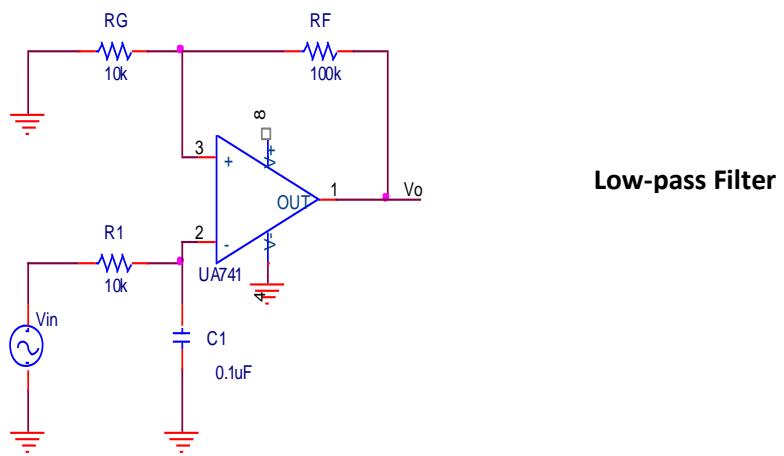

Low-pass Filter

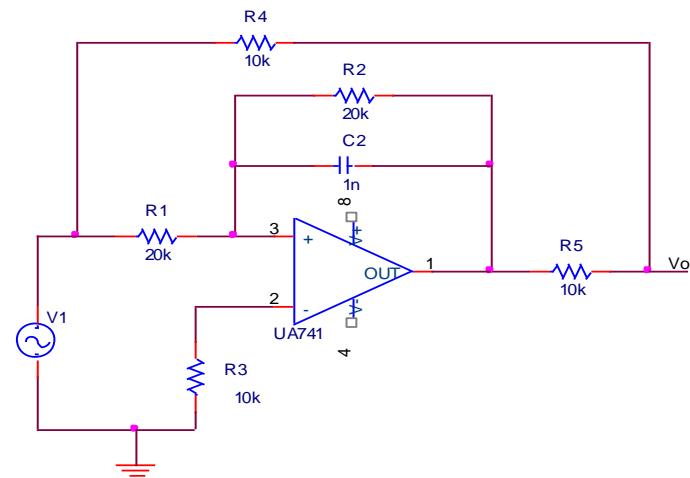

High-pass Filter

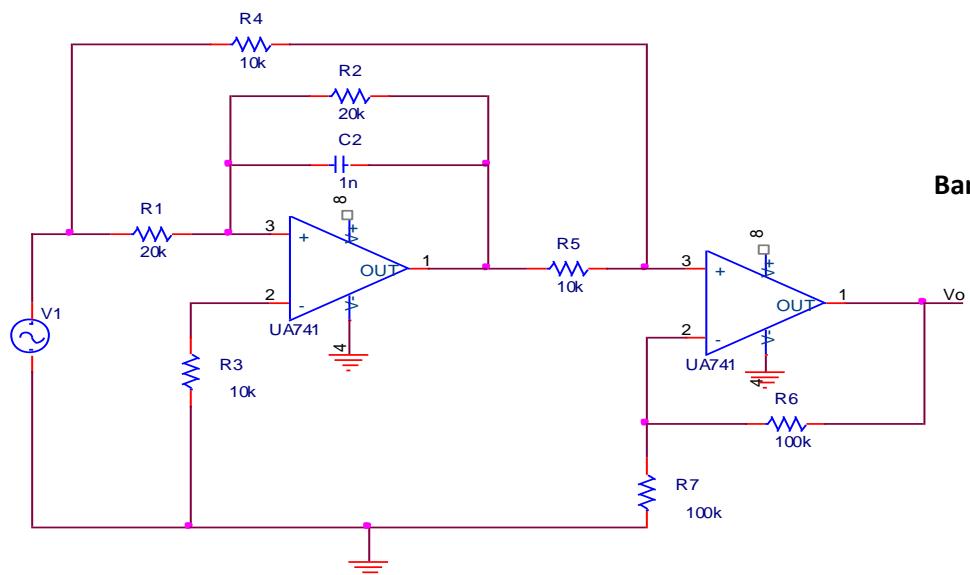

Band-pass Filter

PROGRAM:

*Low Pass Filter (BY UA 741)

VIN 1 0 AC 1

RG 3 0 10K

RF 3 4 100K

R1 1 2 15.9K

C1 2 0 .01UF

XA1 2 3 7 4 6 UA741

*

* connections: non-inverting input

* | inverting input

* || positive power supply

* ||| negative power supply

* |||| output

* |||||

.subckt uA741 1 2 3 4 5

* c1 11 12 8.661E-12

c2 6 7 30.00E-12

dc 5 53 dy

de 54 5 dy

dip 90 91 dx

dIn 92 90 dx

dp 4 3 dx

egnd 99 0 poly(2),(3,0),(4,0) 0 .5 .5

fb 7 99 poly(5) vb vc ve vlp vln 0 10.61E6 -1E3 1E3 10E6 -10E6

ga 6 0 11 12 188.5E-6

gcm 0 6 10 99 5.961E-9

```
iee 10 4 dc 15.16E-6
hlim 90 0 vlim 1K
q1 11 2 13 qx
q2 12 1 14 qx
r2 6 9 100.0E3
rc1 3 11 5.305E3
rc2 3 12 5.305E3
re1 13 10 1.836E3
re2 14 10 1.836E3
ree 10 99 13.19E6
ro1 8 5 50
ro2 7 99 100
rp 3 4 18.16E3
vb 9 0 dc 0
vc 3 53 dc 1
ve 54 4 dc 1
vlim 7 8 dc 0
vlp 91 0 dc 40
vln 0 92 dc 40
.model dx D(Is=800.0E-18 Rs=1)
.model dy D(Is=800.00E-18 Rs=1m Cjo=10p)
.model qx NPN(Is=800.0E-18 Bf=93.75)
.ends
.AC DEC 10 10HZ 100GHZ
.PLOT AC VM(4) VP(4)
.PROBE
.END
```

* HIGH PASS Filter (BY UA741)

VIN 1 0 AC 1

RG 3 0 10K

RF 3 4 10K

C1 1 2 .01UF

R1 2 0 15.9K

XA1 2 3 7 4 6 UA741

*

* connections: non-inverting input

* | inverting input

* || positive power supply

* ||| negative power supply

* |||| output

* |||||

.subckt uA741 1 2 3 4 5

*

c1 11 12 8.661E-12

c2 6 7 30.00E-12

dc 5 53 dy

de 54 5 dy

dip 90 91 dx

dIn 92 90 dx

dp 4 3 dx

egnd 99 0 poly(2),(3,0),(4,0) 0 .5 .5

fb 7 99 poly(5) vb vc ve vlp vln 0 10.61E6 -1E3 1E3 10E6 -10E6

ga 6 0 11 12 188.5E-6

gcm 0 6 10 99 5.961E-9

```
iee 10 4 dc 15.16E-6
hlim 90 0 vlim 1K
q1 11 2 13 qx
q2 12 1 14 qx
r2 6 9 100.0E3
rc1 3 11 5.305E3
rc2 3 12 5.305E3
re1 13 10 1.836E3
re2 14 10 1.836E3
ree 10 99 13.19E6
ro1 8 5 50
ro2 7 99 100
rp 3 4 18.16E3
vb 9 0 dc 0
vc 3 53 dc 1
ve 54 4 dc 1
vlim 7 8 dc 0
vlp 91 0 dc 40
vln 0 92 dc 40
.model dx D(Is=800.0E-18 Rs=1)
.model dy D(Is=800.00E-18 Rs=1m Cjo=10p)
.model qx NPN(Is=800.0E-18 Bf=93.75)
.ends
.AC DEC 10 10HZ 100KHZ
.PLOT AC VM(4) VP(4)
.PROBE
.END
```

*BAND PASS FILTER

VIN 1 0 AC 1V

R1 1 2 5K

R2 3 4 1.5K

R3 2 0 265K

C1 2 4 0.01UF

C2 2 3 0.01UF

RL 4 0 15K

VCC 6 0 DC 12V

VEE 0 7 DC 12V

XA1 0 3 6 7 4 UA741

.subckt uA741 1 2 3 4 5

*

c1 11 12 8.661E-12

c2 6 7 30.00E-12

dc 5 53 dy

de 54 5 dy

dlp 90 91 dx

dln 92 90 dx

dp 4 3 dx

egnd 99 0 poly(2),(3,0),(4,0) 0 .5 .5

fb 7 99 poly(5) vb vc ve vlp vln 0 10.61E6 -1E3 1E3 10E6 -10E6

ga 6 0 11 12 188.5E-6

gcm 0 6 10 99 5.961E-9

iee 10 4 dc 15.16E-6



hlim 90 0 vlim 1K

q1 11 2 13 qx

```
q2 12 1 14 qx
r2 6 9 100.0E3
rc1 3 11 5.305E3
rc2 3 12 5.305E3
re1 13 10 1.836E3
re2 14 10 1.836E3
ree 10 99 13.19E6
ro1 8 5 50
ro2 7 99 100
rp 3 4 18.16E3
vb 9 0 dc 0
vc 3 53 dc 1
ve 54 4 dc 1
vlim 7 8 dc 0
vlp 91 0 dc 40
vln 0 92 dc 40
.model dx D(Is=800.0E-18 Rs=1)
.model dy D(Is=800.00E-18 Rs=1m Cjo=10p)
.model qx NPN(Is=800.0E-18 Bf=93.75)
.ends
.AC DEC 10 100HZ 1MEGHZ
.PLOT AC VM(4) VP(4)
.PROBE
.END
```


RESULT:

*LOW PASS CIRCUIT

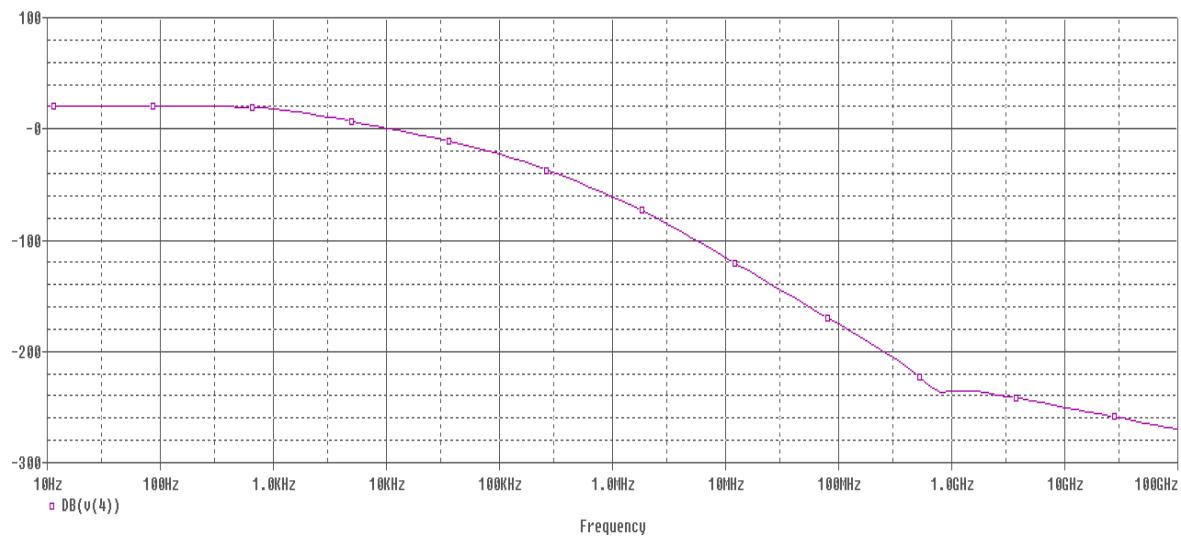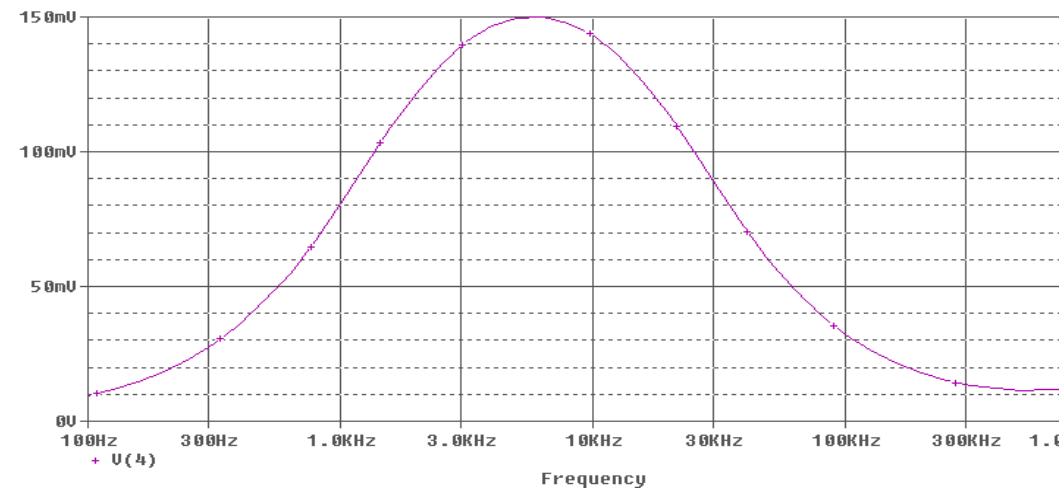



RESULT:

*HIGH PASS CIRCUIT

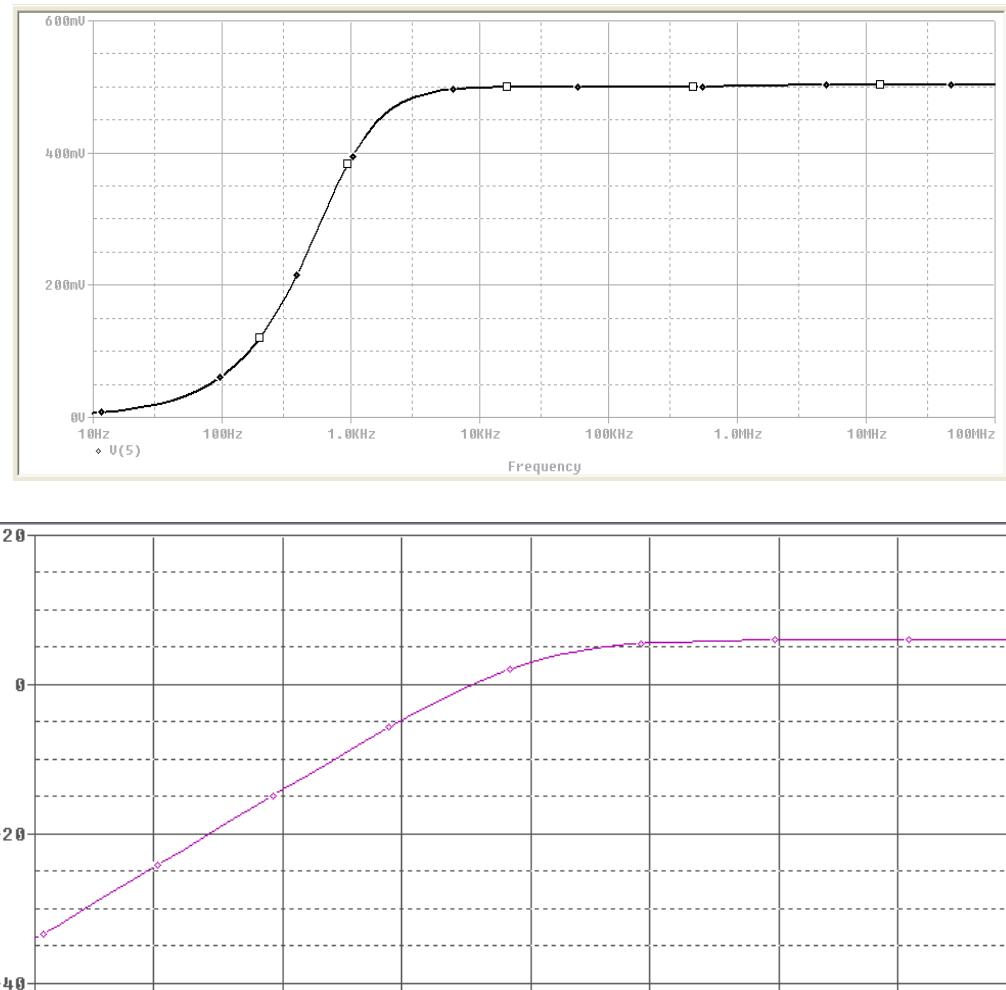

*BAND PASS CIRCUIT

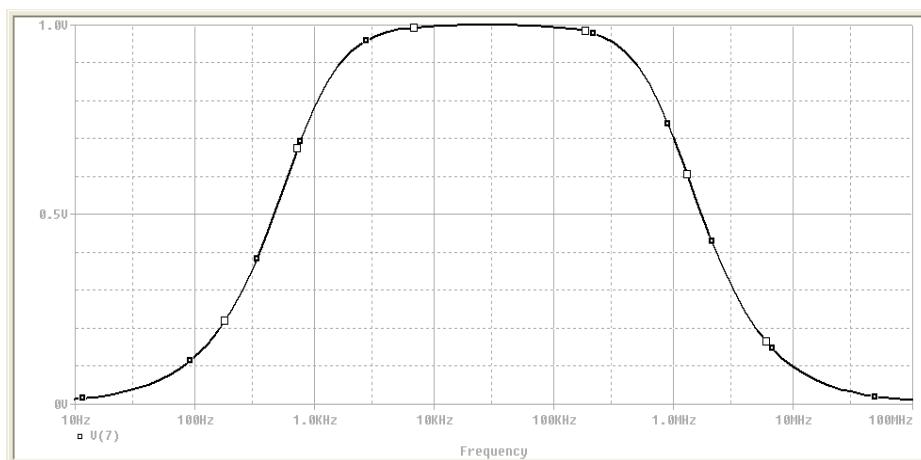

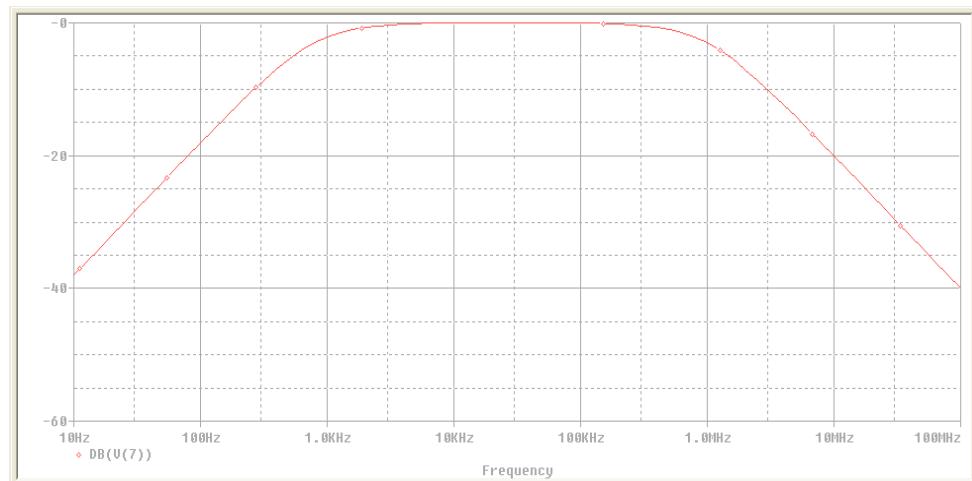


CONCLUSION: We are able to visualise the expected output of active low-pass, high-pass & band-pass filter as given in theory.

EXPERIMENT NO 8

AIM: Simulate and study Integrator using PSPICE windows.

CIRCUIT DIAGRAM:

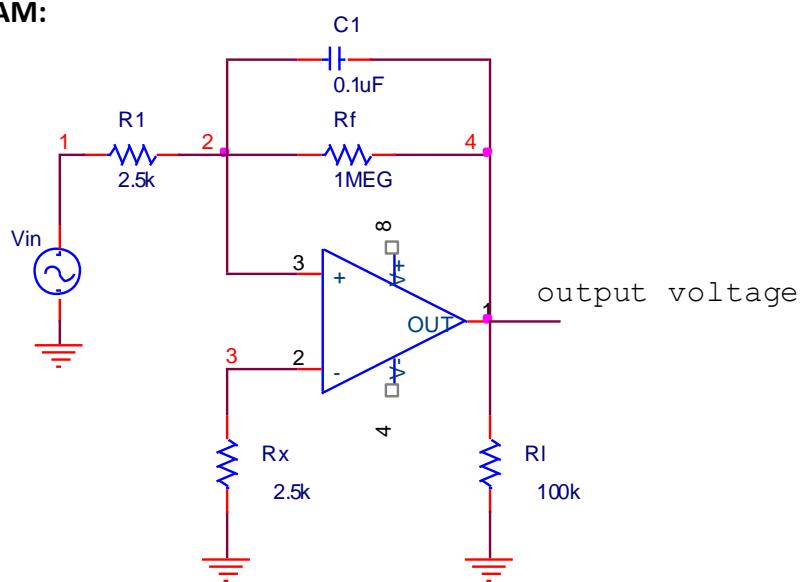

PROGRAM:

* INTEGRATOR

VIN 1 0 PWL(0 0 1NS -1V 1MS -1V 1.0001MS 1v 2ms 1v 2.0001ms -1V 3MS -1V 3.0001MS 1V 4MS 1V)

R1 1 3 2.5K

RF 3 6 1MEG

RX 2 0 2.5K

RL 6 0 100K

C1 3 6 0.1UF

XA1 2 3 7 4 6 UA741


* connections: non-inverting input

* | inverting input

* | | positive power supply

```
*      ||| negative power supply
*
*      ||| | output
*
*      |||| |
.subckt uA741 1 2 3 4 5
*
c1 11 12 8.661E-12
c2 6 7 30.00E-12
dc 5 53 dy
de 54 5 dy
dlp 90 91 dx
dln 92 90 dx
dp 4 3 dx
egnd 99 0 poly(2),(3,0),(4,0) 0 .5 .5
fb 7 99 poly(5) vb vc ve vlp vln 0 10.61E6 -1E3 1E3 10E6 -10E6
ga 6 0 11 12 188.5E-6
gcm 0 6 10 99 5.961E-9
iee 10 4 dc 15.16E-6
hlim 90 0 vlim 1K
q1 11 2 13 qx
q2 12 1 14 qx
r2 6 9 100.0E3
rc1 3 11 5.305E3
rc2 3 12 5.305E3
re1 13 10 1.836E3
re2 14 10 1.836E3
ree 10 99 13.19E6
ro1 8 5 50
```

```
ro2 7 99 100
rp 3 4 18.16E3
vb 9 0 dc 0
vc 3 53 dc 1
ve 54 4 dc 1
vlim 7 8 dc 0
vlp 91 0 dc 40
vln 0 92 dc 40
.model dx D(Is=800.0E-18 Rs=1)
.model dy D(Is=800.00E-18 Rs=1m Cjo=10p)
.model qx NPN(Is=800.0E-18 Bf=93.75)
.ends
.TRAN 50US 4MS
.PROBE
.END
```

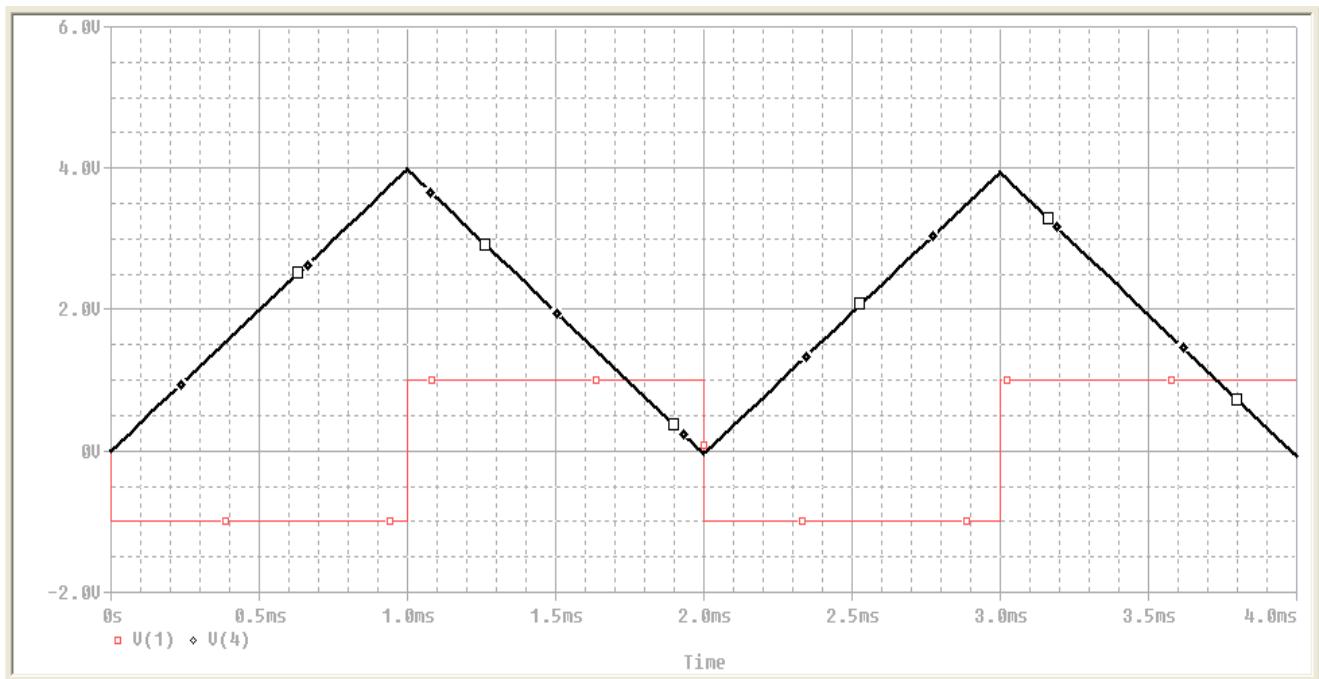
RESULT:

CONCLUSION: We are able to visualise the expected output of Integrator circuit as given in theory.

EXPERIMENT NO 9

AIM: Simulate and study Differentiator using PSPICE windows.

CIRCUIT DIAGRAM:

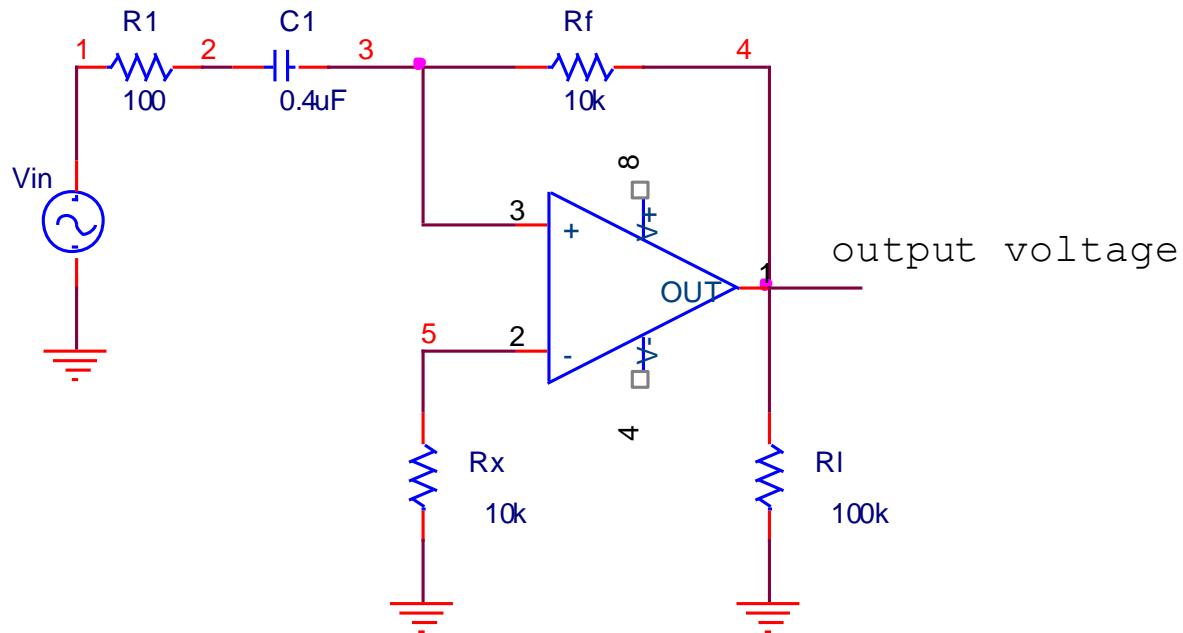

PROGRAM:

*DIFFERENTIATOR CIRCUIT

VIN 1 0 PWL(0 0 1MS 1 2MS 0 3MS 1 4MS 0)

R1 1 8 82

RF 3 6 1.5K

RX 2 0 1.5K

RL 6 0 10K

C1 8 3 0.1UF

CF 3 6 .005UF

XA1 2 3 7 4 6 UA741

*


* connections: non-inverting input

* | inverting input

```
*      | | positive power supply
*
*      | | | negative power supply
*
*      | | | | output
*
*      | | | |
.subckt uA741 1 2 3 4 5
*
c1 11 12 8.661E-12
c2 6 7 30.00E-12
dc 5 53 dy
de 54 5 dy
dlp 90 91 dx
dln 92 90 dx
dp 4 3 dx
egnd 99 0 poly(2),(3,0),(4,0) 0 .5 .5
fb 7 99 poly(5) vb vc ve vlp vln 0 10.61E6 -1E3 1E3 10E6 -10E6
ga 6 0 11 12 188.5E-6
gcm 0 6 10 99 5.961E-9
iee 10 4 dc 15.16E-6
hlim 90 0 vlim 1K
q1 11 2 13 qx
q2 12 1 14 qx
r2 6 9 100.0E3
rc1 3 11 5.305E3
rc2 3 12 5.305E3
re1 13 10 1.836E3
re2 14 10 1.836E3
ree 10 99 13.19E6
```

```
ro1 8 5 50
ro2 7 99 100
rp 3 4 18.16E3
vb 9 0 dc 0
vc 3 53 dc 1
ve 54 4 dc 1
vlim 7 8 dc 0
vlp 91 0 dc 40
vln 0 92 dc 40
.model dx D(Is=800.0E-18 Rs=1)
.model dy D(Is=800.00E-18 Rs=1m Cjo=10p)
.model qx NPN(Is=800.0E-18 Bf=93.75)
.ends
.TRAN 50US 4MS
.PROBE
.END
```

RESULT:

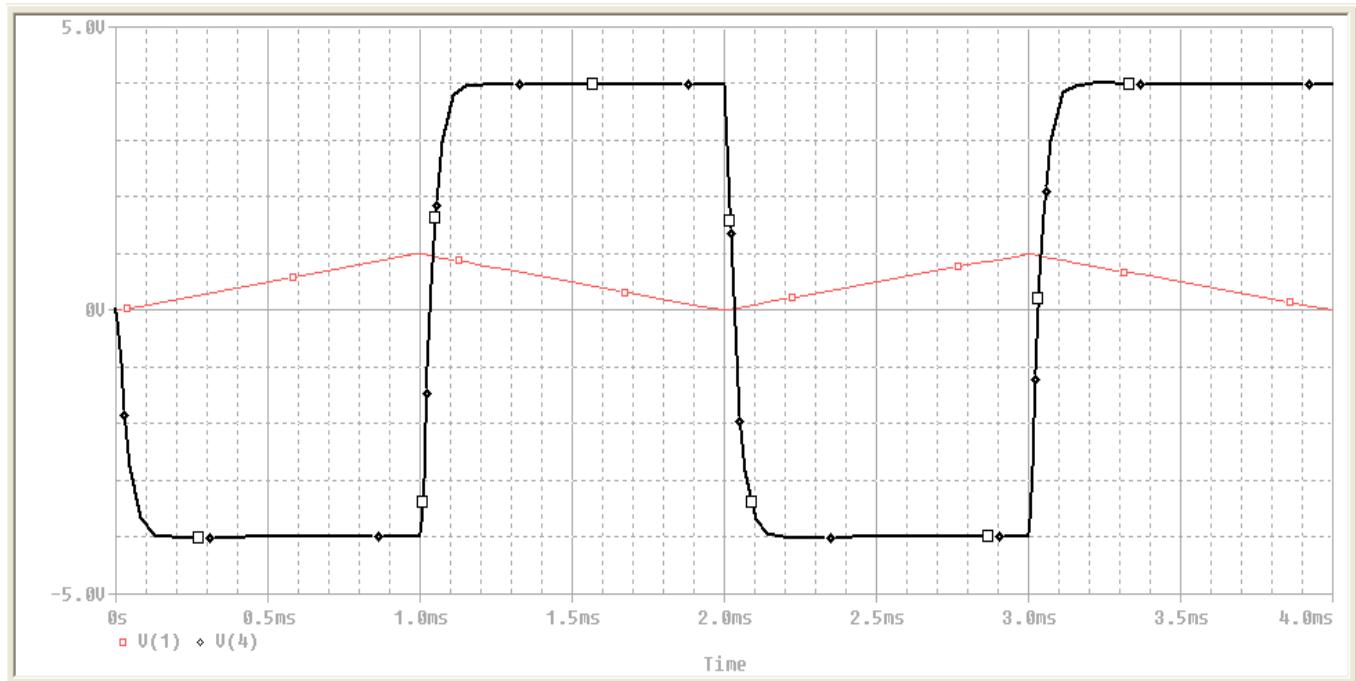


CONCLUSION: We are able to visualise the expected output of Differentiator circuit as given in theory.

EXPERIMENT NO.10


AIM: Simulate and study basic AND, OR, NOT, NOR, NAND, EX-OR gates using PSPICE windows.

CIRCUIT DIAGRAM:


AND GATE

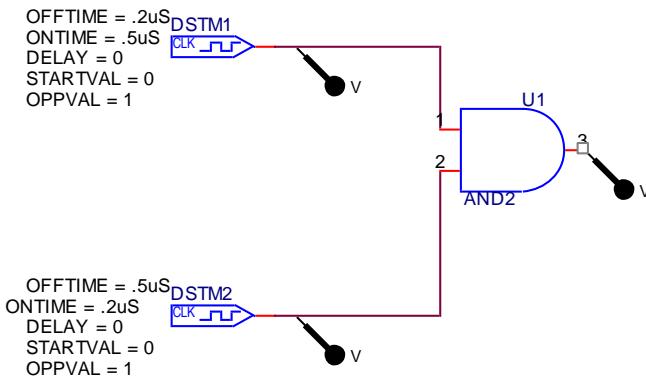


NAND GATE

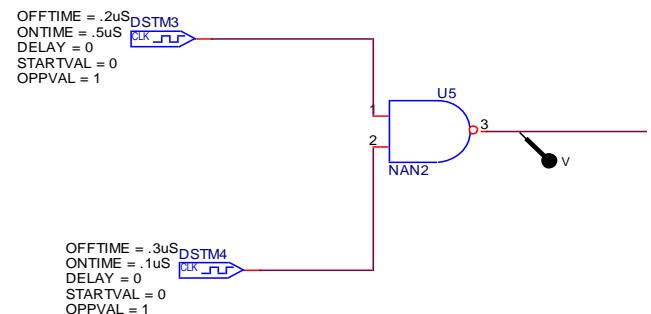


OR GATE

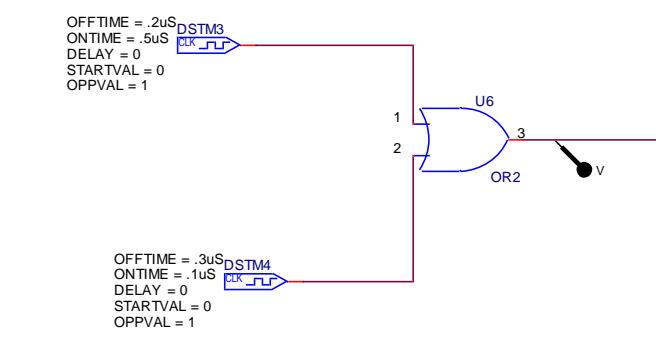


NOR GATE

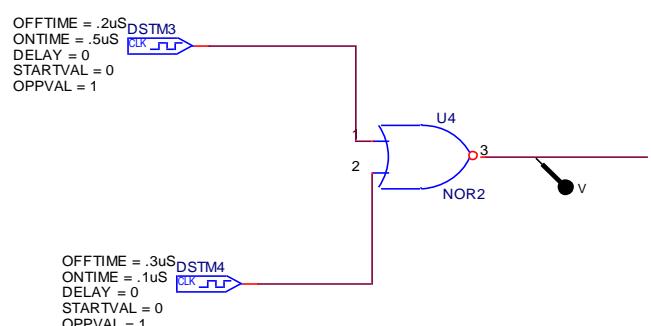

NOT GATE

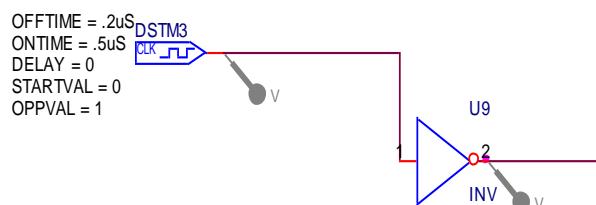


NOR GATE

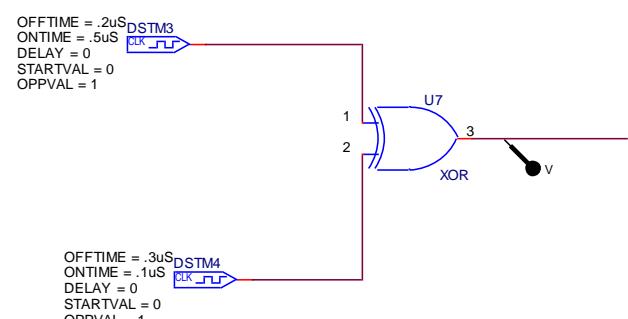


OUTPUT:


(A) AND GATE

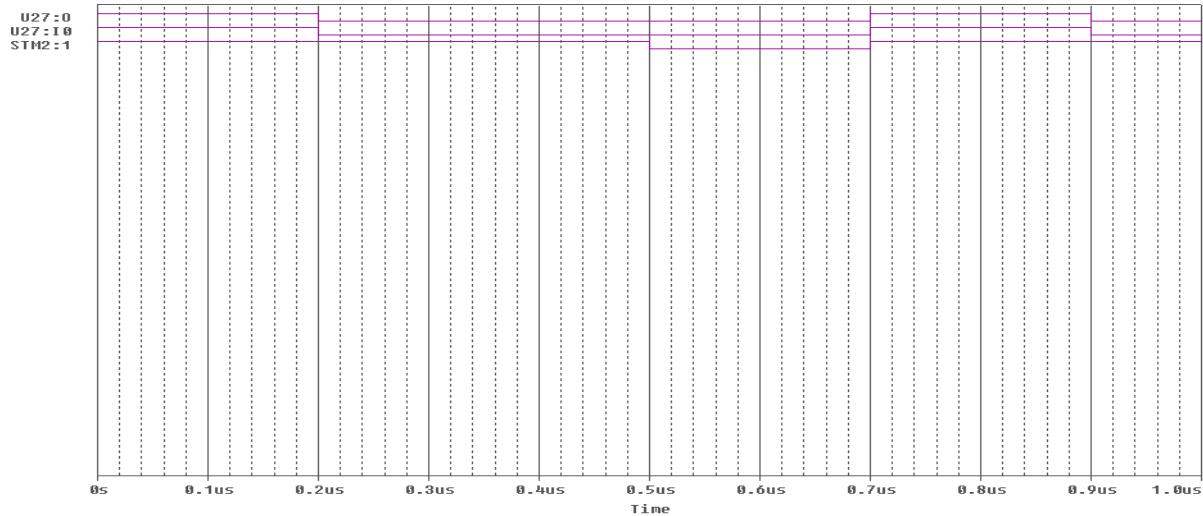


(B) OR GATE

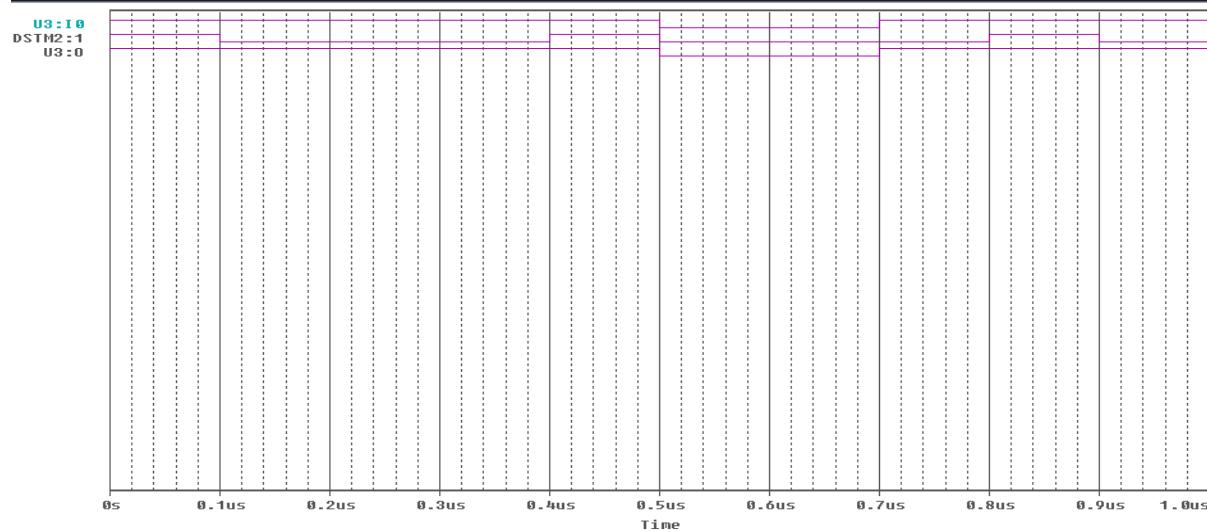


(C) NOT GATE

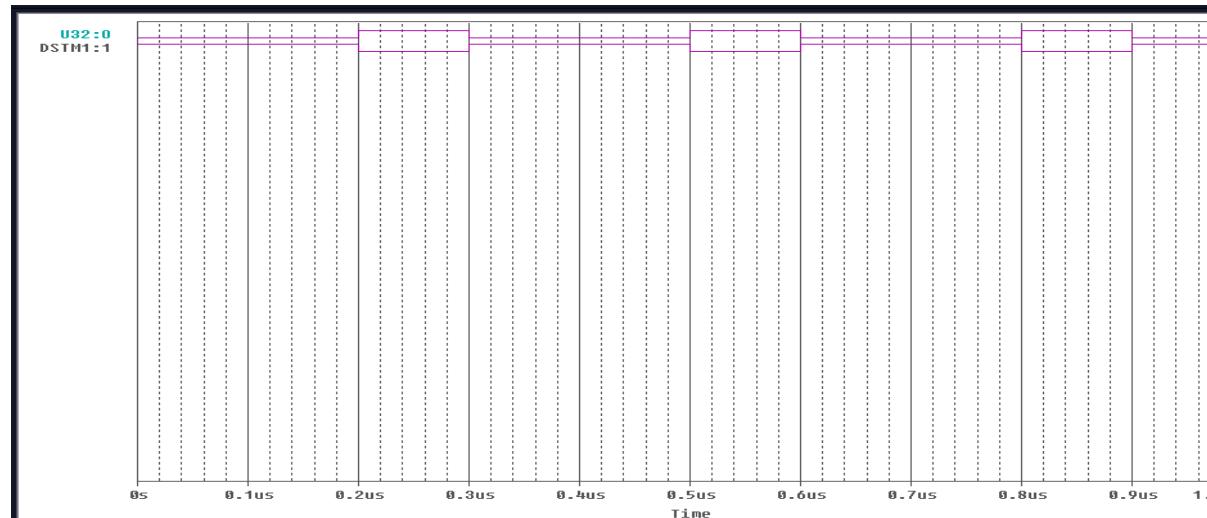

(D) NAND GATE

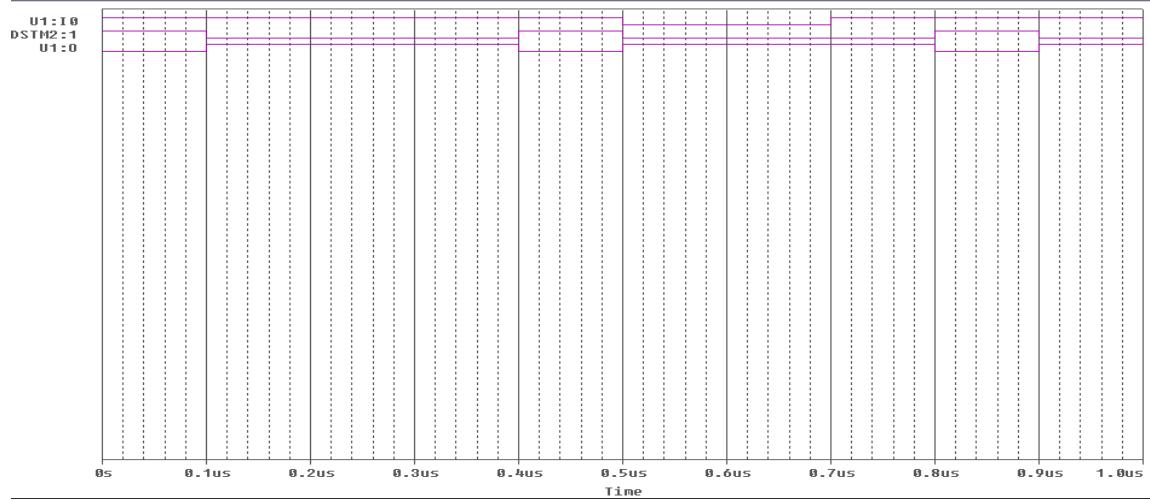

(E) NOR GATE

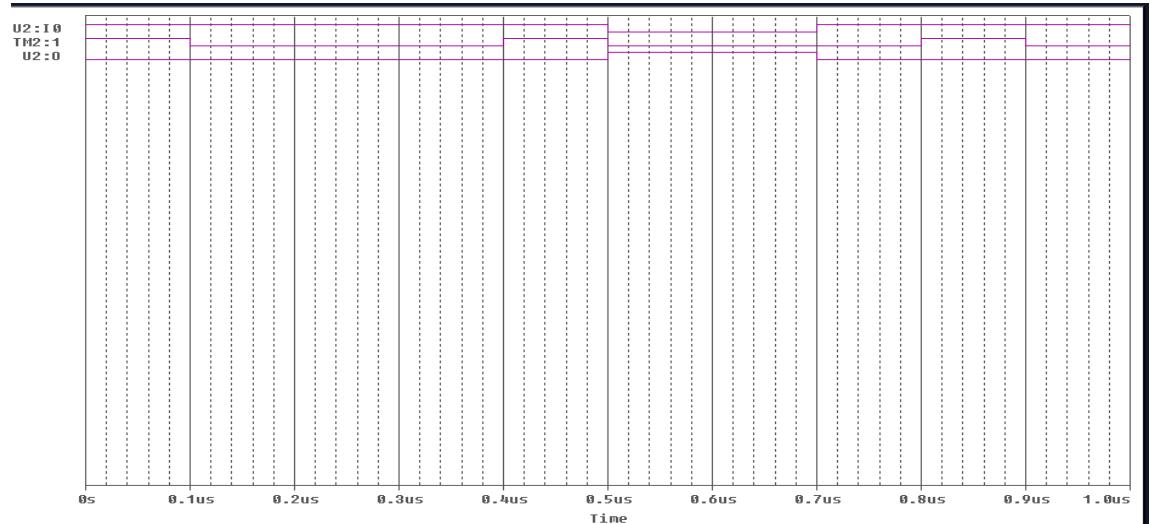

(F) X-OR GATE

