

Unit - II.

PHASE CONTROLLED RECTIFIERS.

CONVERTER:-

It is a circuit which converts the nature of energy namely from ac to dc (or) from dc to ac.

It has two modes:

(i) Rectifier:- It is a circuit which converts ac to dc.

(ii) Inverter:- It is a circuit which converts dc to ac.

Rectifiers are classified as:-

- a) Uncontrolled Rectifier
- b) Fully controlled Rectifier.
- c) Half controlled rectifier

1) Uncontrolled rectifier:-

\* Uses only diodes. Diodes cannot be controlled.

\* amplitude of output voltage cannot be varied and

it is fixed by the amplitude of supply voltage.

2) Fully controlled rectifier:-

\* Uses only SCRs.

\* Output voltage is dependant on supply voltage

and firing angle. SCRs can be controlled easily.

3) Half controlled rectifier.

\* Uses combination of diodes and SCRs.

\* Only limited control over output voltage.


## Phase control:-

The method of controlling the turning "ON" of an SCR by varying its firing angle is called as phase control.


## Firing angle ( $\alpha$ ):-

It is the angle at which the SCR is turned ON.

## classification:-

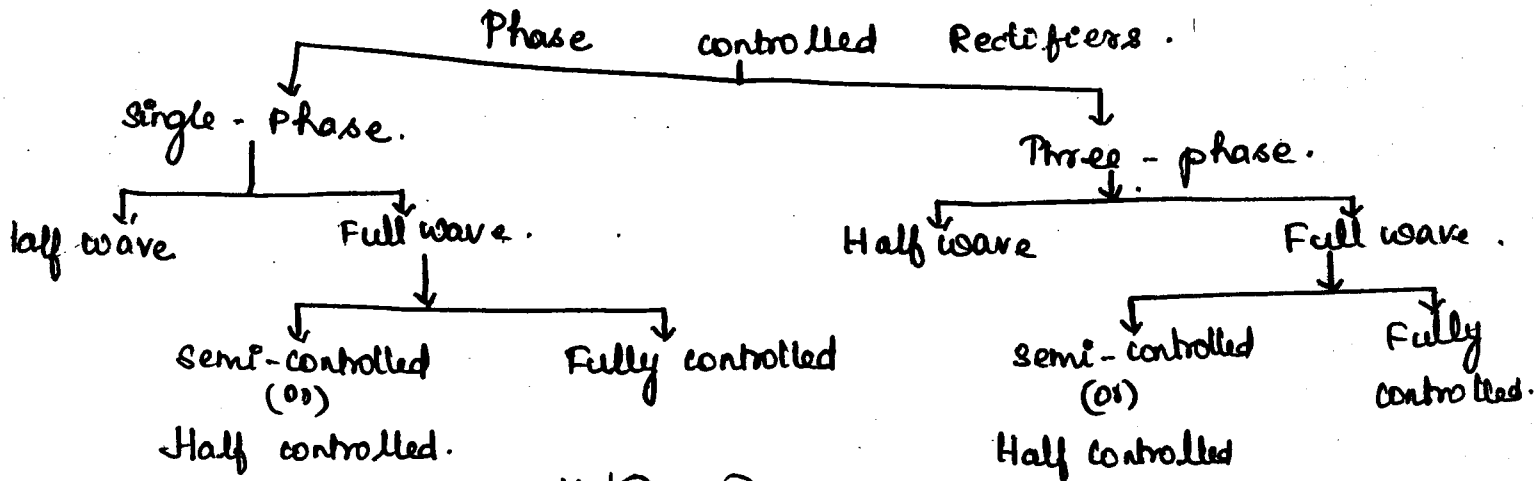


## Half wave rectifier:-

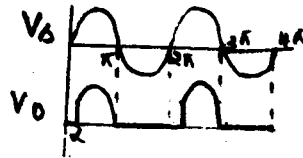

\* when positive half cycle of supply voltage alone is applied to the load, it is called as half-wave converter.
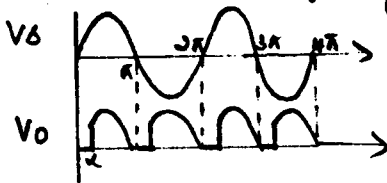
## Full wave rectifier:-

\* when both half cycles are applied to load after rectifying



## Half controlled (or) Semi controlled rectifier:-

\* circuit has combination of SCRs and diodes.

\* due to presence of diode control is effected only for positive o/p vge. o/p vge cannot be negative. Can be operated only in first quadrant.

$$\frac{V}{I}$$

## Fully controlled rectifier:-

\* Uses only SCRS. \* o/p current is always +ve. \* o/p vge can be positive or negative. Operated in I and IV quadrant

## Four quadrant converter (or) Full bridge converter:-

\* operates on all 4 quadrants \* o/p vge and curt can be either +ve or -ve

$$\frac{V}{I}$$

Principle of phase control:-

The principle of phase control can be explained by means of a 1 $\phi$  Half wave rectifier.

In phase control the SCRs are turned OFF by line or natural commutation.  $\therefore$  they do not need external commutation circuits.

NOTE:-


In this discussion, SCRs and diodes are assumed as ideal switches.

\* No  $V_{ge}$  drop across them.

\* No reverse current under reverse bias condition.

\* Holding current is zero.

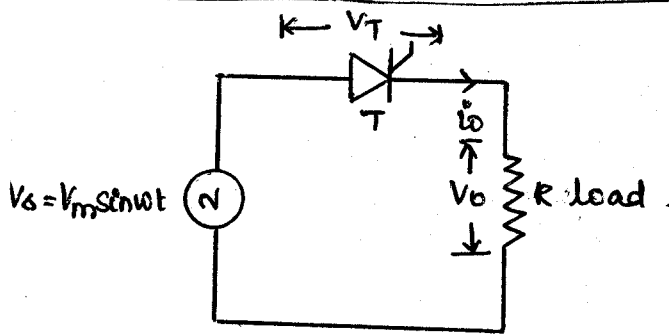1 $\phi$  HALF WAVE RECTIFIER (HWR) WITH RESISTIVE (R) LOAD:-



NOTE:-

\* SCR is forward biased when anode of SCR is +ve w.r.t cathode.

\* SCR can be triggered only when it is in forward biased condition.

\* when SCR is turned ON,  $V_{ge}$  across SCR = 0 and current =  $I_{avg}$ .

\* when SCR is turned OFF,  $V_{ge}$  across SCR = supply  $V_{ge}$  and current = 0.

The SCR T is supplied with an ac voltage given

by  $V_s = V_m \sin \omega t$ .

$i_o =$  load current,  $V_o =$  load  $V_{ge}$ .

$V_T =$   $V_{ge}$  across SCR.

In the positive half cycle:-

\* Anode of SCR is +ve w.r.t. cathode

\* SCR T is forward biased.

\* SCR is triggered or turned ON at  $\omega t = \alpha$ .

∴ from 0 to  $\alpha$

SCR T is OFF

∴  $V_T = V_s$

$i_T = 0$

\* At  $\alpha$  SCR T is ON

∴  $V_T = 0$  [ when SCR is ON  $V_{gc}$  across it is zero ]

$i_o = i_T = \uparrow$

\* In the negative half cycle:


\* At  $\omega t = \pi$ ; anode of SCR is -ve w.r.t. cathode.

\* ∴ SCR T is reverse biased and turned OFF (by line commutation)

∴  $V_o = 0$ ;  $i_o = 0$ ;  $V_T = V_s$ .

In this SCR conducts only in +ve half cycle.

Period	$V_o$	$i_o$	$i_T$	$V_T$
0 to $\alpha$	0	0	0	$V_s$
$\alpha$ to $\pi$	follows $V_s$	+ve current	+ve amt	0
$\pi$ to $\pi + \alpha$	0	0	0	$V_s$
$\pi + \alpha$ to $2\pi$	follows $V_s$	+ve	+ve.	0

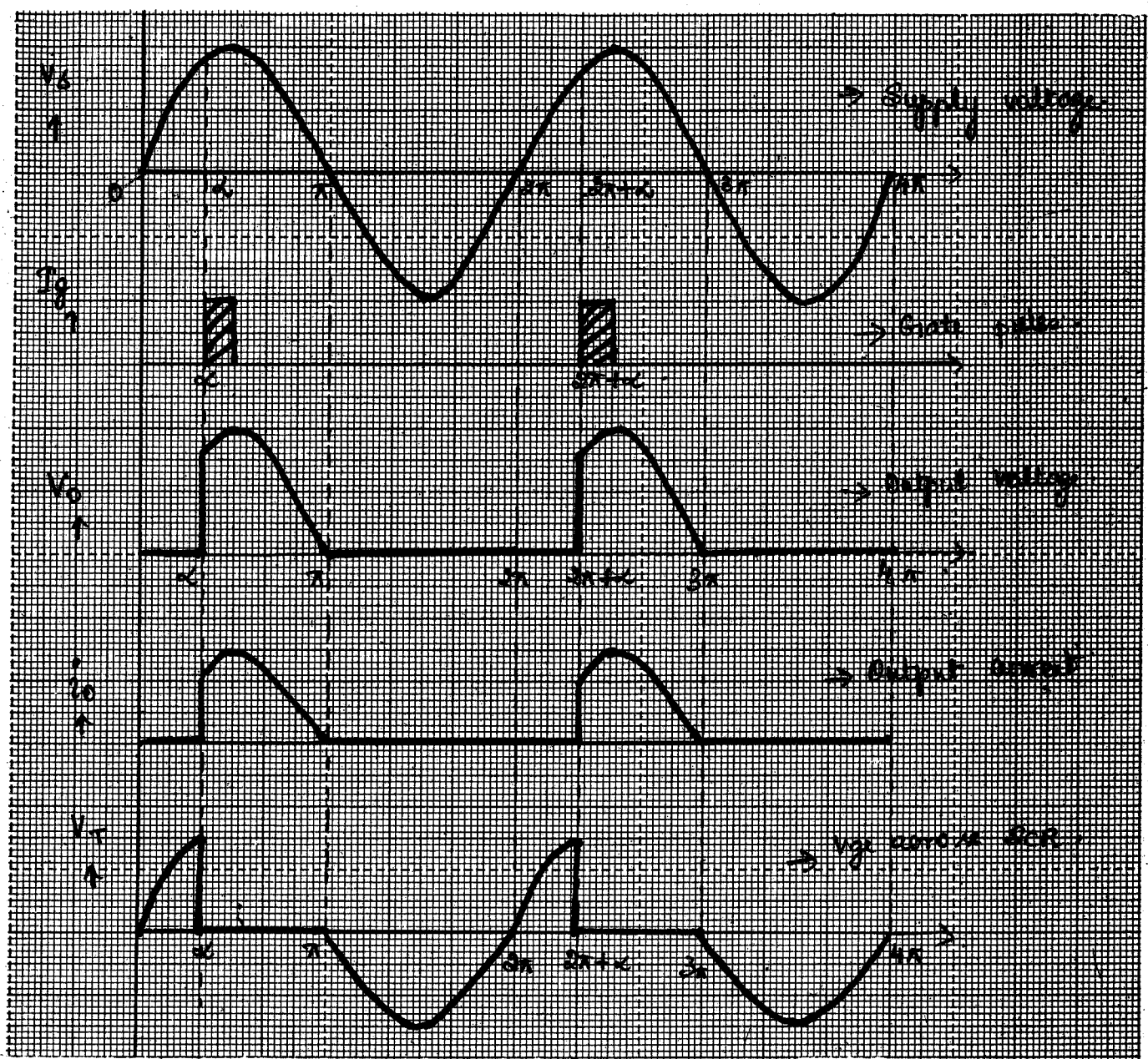

Output voltage  $V_o(\text{avg}) = \frac{1}{2\pi} \int_{\alpha}^{\pi} V_m \sin \omega t \cdot d\omega t$

$$= \frac{V_m}{2\pi} \left[ -\cos \omega t \right]_{\alpha}^{\pi}$$

$$= -\frac{V_m}{2\pi} [\cos \pi - \cos \alpha]$$

$$= -\frac{V_m}{2\pi} [-1 - \cos \alpha]$$

$$V_o(\text{avg}) = \frac{V_m}{2\pi} [1 + \cos \alpha]$$

$$V_o(\text{rms}) = \sqrt{\frac{1}{2\pi} \int_{\alpha}^{\pi} V_m^2 \sin^2 \omega t \cdot d\omega t}$$

$$= \sqrt{\frac{V_m^2}{2\pi} \int_{\alpha}^{\pi} \sin^2 \omega t \cdot d\omega t}$$

$$= \sqrt{\frac{V_m^2}{2\pi} \int_{\alpha}^{\pi} \frac{(1 - \cos 2\omega t)}{2} d\omega t}$$

$$= \sqrt{\frac{V_m^2}{4\pi} \left\{ [\omega t]_{\alpha}^{\pi} - \left[ \frac{\sin 2\omega t}{2} \right]_{\alpha}^{\pi} \right\}}$$

$$= \sqrt{\frac{V_m^2}{4\pi} \left\{ [\pi - \alpha] - \frac{1}{2} [\sin 2\pi - \sin 2\alpha] \right\}}$$

$\sin 2\pi = 0$


$$V_o(\text{rms}) = \frac{V_m}{2\sqrt{\pi}} \sqrt{(\pi - \alpha) + \frac{1}{2} \sin 2\alpha}$$

$$I_o(\text{avg}) = \frac{V_o(\text{avg})}{R} = \frac{V_m}{2\pi R} [1 + \cos \alpha]$$

$$I_o(\text{rms}) = \frac{V_m}{2R\sqrt{\pi}} \sqrt{(\pi - \alpha) + \frac{1}{2} \sin 2\alpha}$$

$$\text{Power} = P = V_{\text{rms}} * I_{\text{rms}}$$
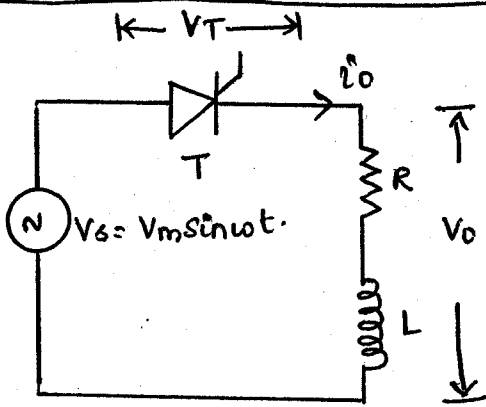
# 1 $\phi$ HALF WAVE CIRCUIT WITH RL load:-



During positive half cycle.

\* The SCR T is forward biased.

\* At  $\omega t = \alpha$ ; triggering pulse is given to SCR T.

\* From 0 to  $\alpha$ ; SCR T is forward biased.

$\therefore$  Vge across SCR  $V_T = V_s$ .

\* current  $i_T = i_o = 0$ .

\* Vge across load  $V_o = 0$ .

At  $\omega t = \alpha$  when SCR T is ON

\*  $V_T = 0$

$V_o = V_s$

$i_o = \uparrow$ ing slowly due to inductance L.

But because the load has an inductance L the current increases very slowly and reaches its maximum at  $\omega t = \pi$ .

$\therefore$  At  $\omega t = \pi$ ;  $V_o = 0$ ;  $i_o = i_{max}$ .

During -ve half cycle:-

\* during -ve half cycle at  $\omega t = \pi$ ; though load voltage is zero and though the SCR T is reverse biased, it will not turn OFF because  $i_o$  is not less than holding current.

\*  $i_o$  takes some time ( $\beta$ ) to reduce to zero.

$\therefore$  at  $\omega t = \beta$ ;  $V_o = 0$ ;  $i_o = 0$ .

\* From  $\pi$  to  $\pi + \beta$  the Vge across SCR will be -ve like the supply Vge ( $\therefore$  it is reverse biased).


\* Again at  $\omega t = 2\pi + \alpha$ , SCR T is turned ON. and the same process as above is repeated.

\*  $\alpha$  is called firing angle.

\*  $\beta$  is called extinction angle.

\*  $(\beta - \alpha) = \theta$  is called conduction angle.

Period	$V_o$	$i_o$	$V_T$
0 to $\alpha$	0	0	$V_s$
$\alpha$ to $\pi$	$V_s$	increases slowly	0
$\pi$ to $\beta$	$-V_s$	decreases to zero	0
$\beta$ to $2\pi$	0	0	$-V_s$

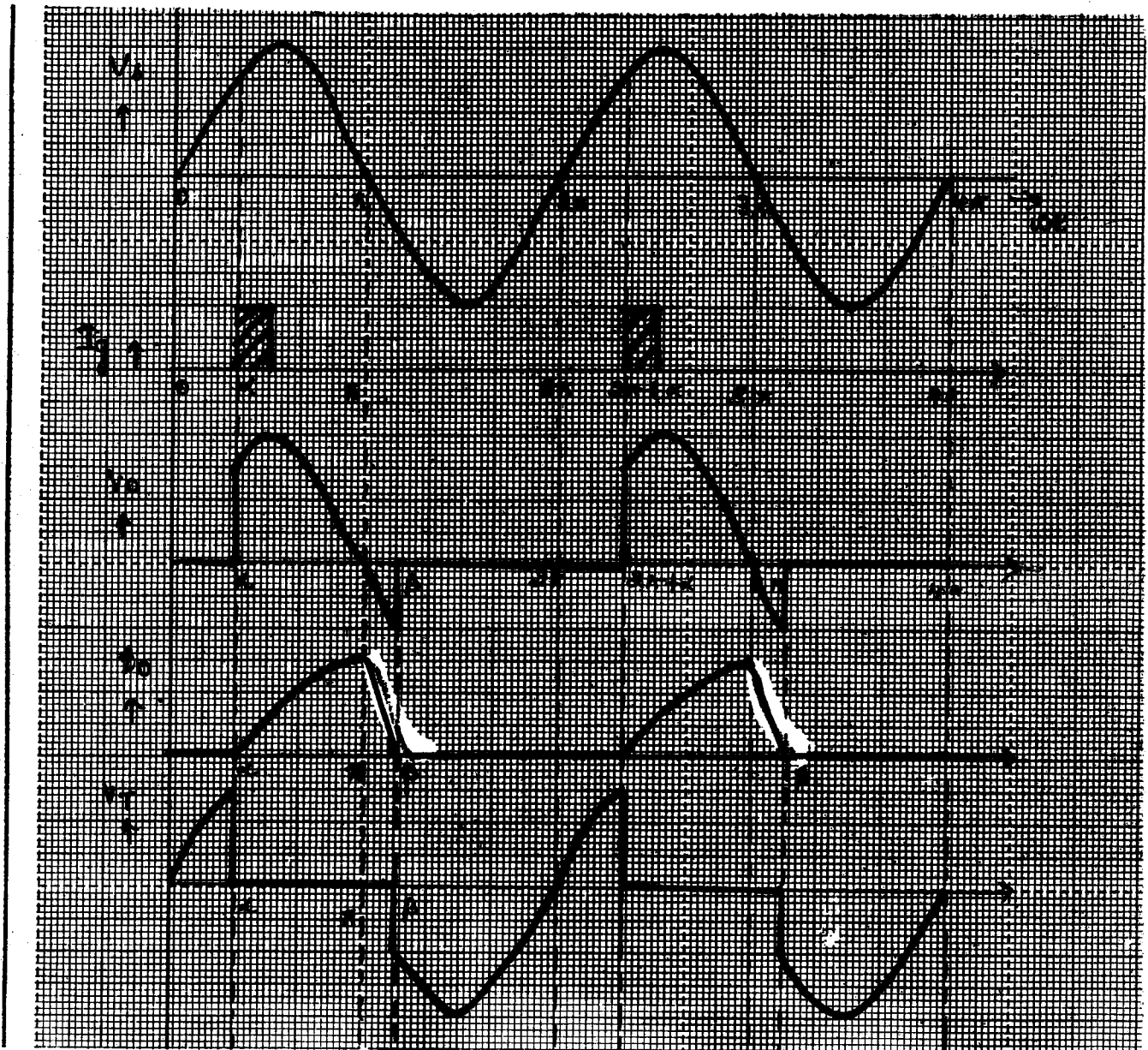



Average value of load voltage  $V_o(\text{avg}) = \frac{1}{2\pi} \int_{\alpha}^{\beta} V_m \sin \omega t \cdot d\omega t$

$$V_o(\text{avg}) = \frac{V_m}{2\pi} \int_{\alpha}^{\beta} \sin \omega t \cdot d\omega t$$

$$= \frac{V_m}{2\pi} \left[ -\cos \omega t \right]_{\alpha}^{\beta} = -\frac{V_m}{2\pi} [\cos \beta - \cos \alpha]$$

$$V_o(\text{avg}) = \frac{V_m}{2\pi} [\cos \alpha - \cos \beta]$$

$$I_o(\text{avg}) = \frac{V_o(\text{avg})}{R} = \frac{V_m}{2\pi R} [\cos \alpha - \cos \beta]$$

Rms value :-  $V_o(\text{rms}) = \sqrt{\frac{1}{2\pi} \int_{\alpha}^{\beta} V_m^2 \sin^2 \omega t \cdot d\omega t}$

$$= \sqrt{\frac{V_m^2}{2\pi} \int_{\alpha}^{\beta} \left[ \frac{1 - \cos 2\omega t}{2} \right] d\omega t}$$

$$= \sqrt{\frac{V_m^2}{4\pi} \left\{ [\omega t]_{\alpha}^{\beta} - \left[ \frac{\sin 2\omega t}{2} \right]_{\alpha}^{\beta} \right\}}$$

$$V_o(\text{rms}) = \frac{V_m}{2\sqrt{\pi}} \left[ \beta - \alpha - \frac{1}{2} [\sin 2\beta - \sin 2\alpha] \right]$$

$$I_o(\text{rms}) = \frac{V_o(\text{rms})}{R} = \frac{V_m}{2R\sqrt{\pi}} \left[ \beta - \alpha - \frac{1}{2} [\sin 2\beta - \sin 2\alpha] \right]$$

$$P = V_o(\text{rms}) * I_o(\text{rms})$$

# 1 $\phi$ HALF WAVE RECTIFIER WITH RL LOAD & FREEWHEELING DIODE.

\* The waveform of load current  $i_o$  is improved by connecting a freewheeling diode (FD) across the load.

\* FD is also called as flywheel diode or commutating diode.


\* It is used to prevent the reversal of load voltage.

## Advantages of freewheeling diode:-

\* Improves input power factor angle.

\* Improves load current waveform.

\* Better load performance.

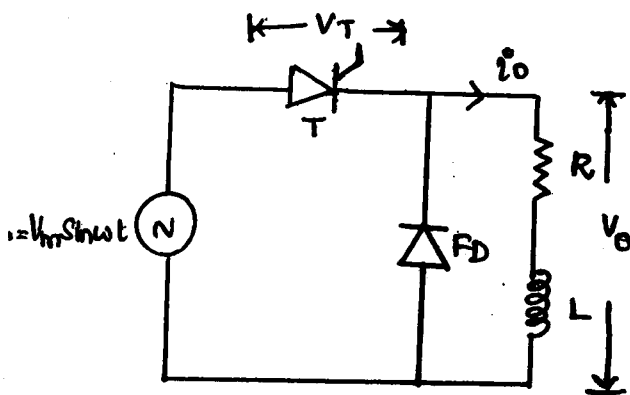

## In the positive half cycle.

\* SCR T is forward biased.

\* freewheeling diode is reverse biased.

$$\therefore V_T = V_s; \quad V_{FD} = V_{\text{across FD}} = -V_s.$$

\* At  $\omega t = \alpha$ ; SCR  $T_1$  is ON.

$\therefore V_{T_1} = 0$ ;  $V_{T_1}$  slowly increases towards max value.

$$V_o = V_s; \quad i_o = i_{T_1} = I^{\text{es}} \text{ slowly}.$$

## In the negative half cycle:-

Supply  $v_{ge}$   $V_s = 0$ .

At  $\omega t = \pi$ ; freewheeling diode is forward biased.

SCR is reverse biased and turns OFF.

The load current  $i_o$  decays through diode FD.

\* The freewheeling diode conducts till the SCR is turned ON again at  $(2\pi + \alpha)$

The operation can be explained in two modes.

(i) Conduction mode [from  $\alpha$  to  $\pi$ ,  $2\pi + \alpha$  to  $3\pi$ ]

In this mode the SCR conducts and the freewheeling diode is reverse biased.

$\therefore V_T = 0; V_{FD} = -V_s. I_o = I_{es}$  slowly.


(ii) Freewheeling mode:- [from  $\pi$  to  $2\pi + \alpha$ ;  $3\pi$  to  $4\pi + \alpha$ ]

In this mode SCR is reverse biased from  $\pi$  to  $2\pi$ ;  $3\pi$  to  $4\pi$  and diode (FD) conducts (Forward biased) from  $\pi$  to  $2\pi + \alpha$  and  $3\pi$  to  $4\pi + \alpha$ .

$V_T = -V_s$  (from  $\pi$  to  $2\pi$ );  $V_T = V_s$  ( $2\pi$  to  $2\pi + \alpha$ )  
 $V_{FD} = 0$  ( $3\pi$  to  $4\pi$ );  $V_{FD} = 0$  ( $2\pi$  to  $2\pi + \alpha$ )  
 $V_o = 0$   $V_o = 0$

Freewheeling diode will be ON till the SCR is turned ON again.

Period.	$V_o$	$I_o$	$V_T$	$V_{FD}$
0 to $\alpha$	0	0	$V_s$	-ve $V_{gc}$
$\alpha$ to $\pi$	+ve $V_{gc}$	increasing	0	-ve.
$\pi$ to $2\pi$	0	decreasing	$-V_s$	0
$2\pi$ to $2\pi + \alpha$	0	decreasing	$+V_s$	0
$2\pi + \alpha$ to $3\pi$	+ve	increasing	0	-ve.

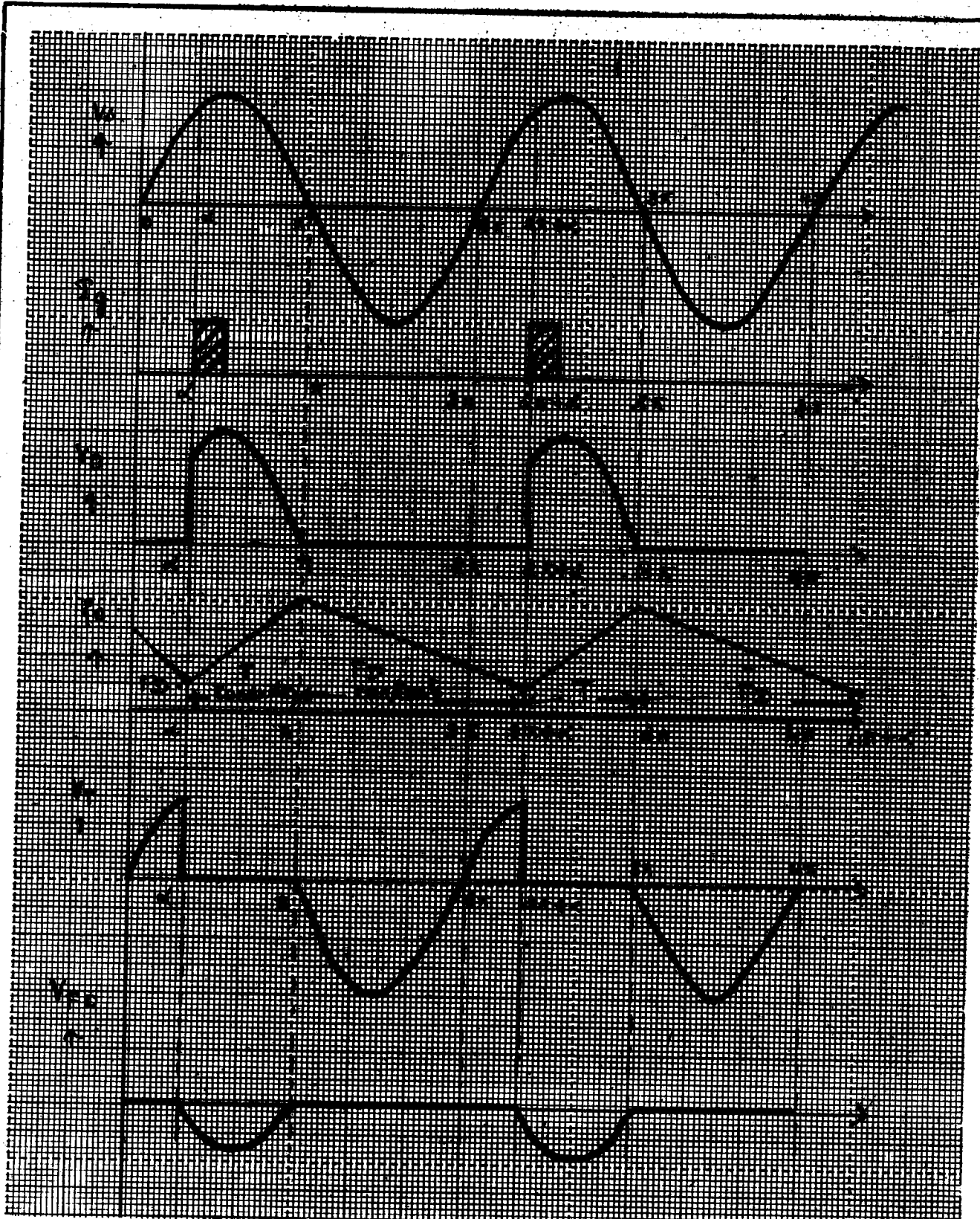


$$V_0(\text{avg}) = \frac{1}{2\pi} \int_{\alpha}^{\pi} v_m \sin \omega t d\omega t = \frac{V_m}{2\pi} (1 + \cos \alpha) \quad [\text{already derived}]$$

$$I_0 = \frac{V_0(\text{avg})}{R} = \frac{V_m}{2\pi R} [1 + \cos \alpha]$$


$$V_0(\text{rms}) = \sqrt{\frac{1}{2\pi} \int_{\alpha}^{\pi} V_m^2 \sin^2 \omega t d\omega t} = \frac{V_m}{2\sqrt{\pi}} \left[ \pi - \alpha + \frac{1}{2} \sin 2\alpha \right]$$

$$I_0(\text{rms}) = \frac{V_m}{2\sqrt{\pi}} \sqrt{[\pi - \alpha] + \frac{1}{2} \sin 2\alpha}$$
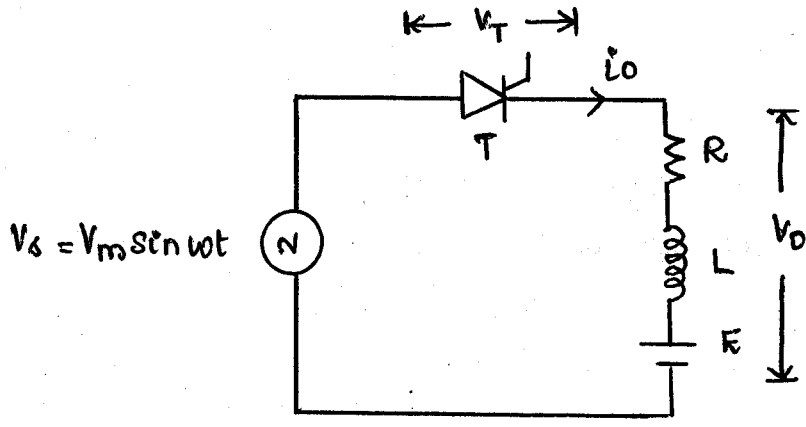
# 1 $\phi$ HALF WAVE CIRCUIT WITH RLE LOAD:-



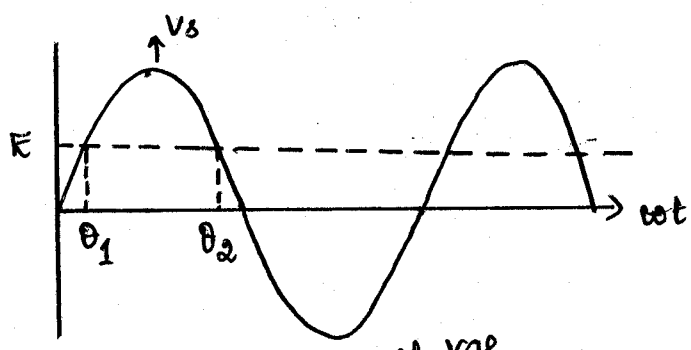- \*  $V_s = V_m \sin \omega t =$  Supply  $V_{ge}$ .
  - \*  $E =$  emf of load (motor) connected.
  - \*  $\therefore V_{ge}$  across SCR =  $V_T$ .
- $V_T = V_s - E$



- \* Till  $\omega t = \theta_1$ ,  $V_s$  is less than  $E$  when  $V_s < E$   
 $V_T = V_s - E = -ve$  value.

\* when a -ve value <sup>of  $v_{ge}$</sup>  is applied across an SCR, it is reverse biased and cannot be turned ON.

\* SCR can be triggered only after  $\theta_1$  i.e.  $\alpha > \theta_1$ . Because only after  $\theta_1$ ;  $V_s$  is  $> E$  and so  $V_T = V_s - E$  is +ve value and SCR will be forward biased.

$$\theta_1 = \sin^{-1} \left[ \frac{E}{V_m} \right]$$

Also after an angle  $\theta_2$ ,  $V_s$  is  $< E$  and so  $V_T = V_s - E = -ve$  value  
 so SCR cannot be triggered after  $\theta_2$ . [ $\theta_2 = \pi - \theta_1$ ]  
 $\therefore \theta_1 < \alpha < \theta_2$ .

### During +ve half cycle:

- \* SCR T is triggered at an angle " $\alpha$ ":  $\alpha$  is  $> \theta_1$ .
- \* from  $\omega t = 0$  to  $\alpha$ ; SCR is OFF.  
 $i_o = 0$  (load current).
- $v_{ge}$  across SCR =  $V_T$ .

till  $\theta_1$ ;  $V_s$  is  $< E$   $\therefore V_T = -V_e$  value  
After  $\theta_1$ ;  $V_s$  is  $> E$   $\therefore V_T = +ve$  value.

$$V_o = i_o R + E.$$

$i_o$  starts flowing only after SCR is ON.

$\therefore$  till  $\omega t = \alpha$ ;  $i_o = 0$ .

$\therefore$  From 0 to  $\alpha$ .

$$V_o = i_o R + E = E \quad (\because i_o = 0 \text{ till } \alpha).$$

$\therefore V_o = E$  (from 0 to  $\alpha$ ).

At  $\alpha$  when SCR is turned ON;  $i_o$  starts increasing.

$$\therefore V_o = i_o R + E \quad [\text{from } \alpha \text{ to } \pi]$$

$i_o = \text{increasing.}$

Vge across SCR =  $V_T = 0$ .

At  $\omega t = \pi$   $i_o$  is maximum.

In -ve half cycle:-

At  $\omega t = \pi$ ;  $i_o$  is maximum.


But the SCR 'T' is reverse biased, but it is not turned OFF because  $i_o$  is  $>$  than holding current.

$$\therefore V_o = -V_s \text{ (Reverse vge).}$$

$i_o$  decreases and reaches zero at  $\omega t = \beta$ .  $\therefore$  SCR turns OFF at  $\beta$ .

$\therefore$  At  $\omega t = \beta$ ;  $V_o = E$ ;  $i_o = 0$ ;  $V_{T1} = -V_s$ .

+

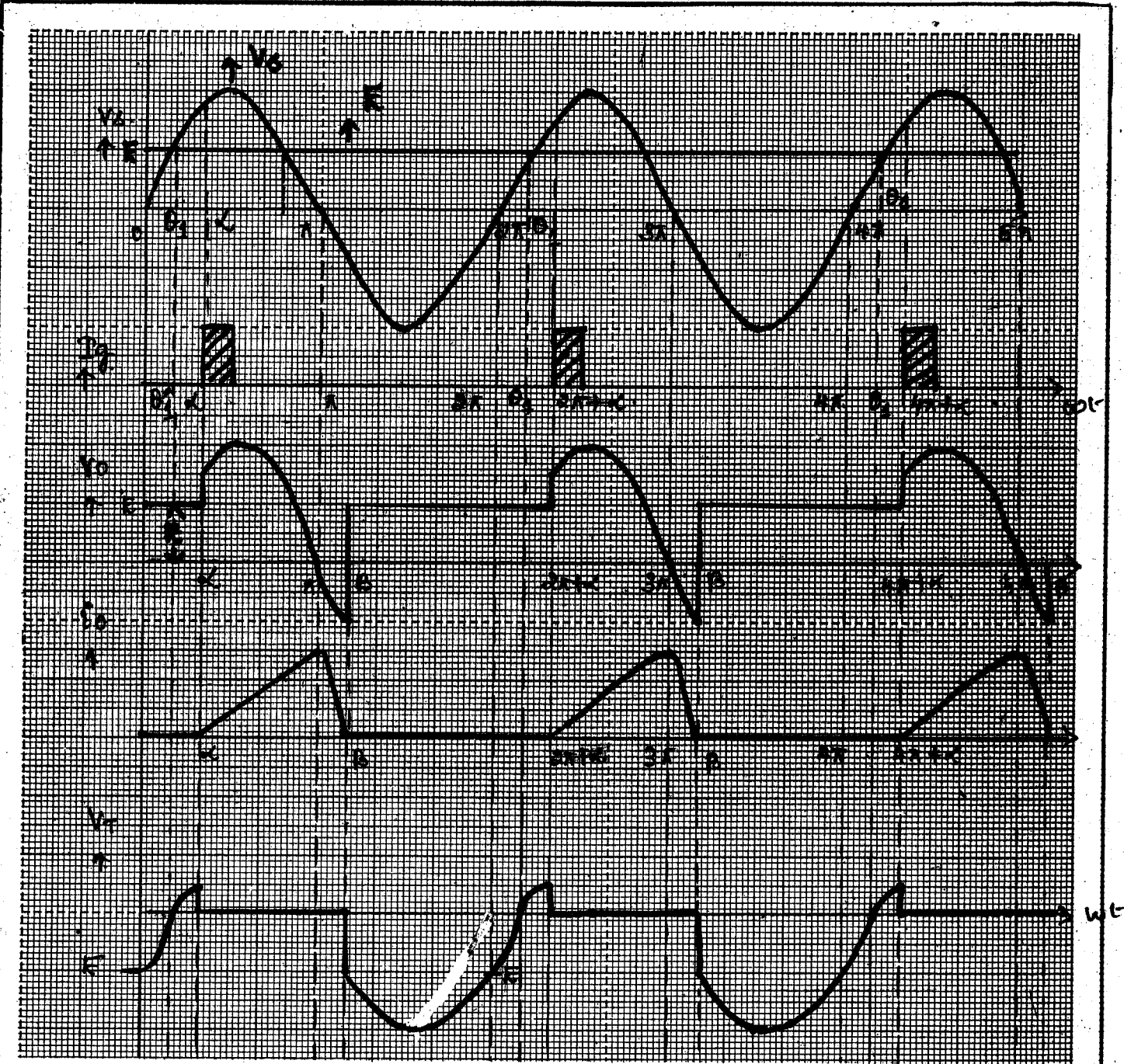

$$V_0 = i_0 R + E$$

$$i_0 = \frac{V_0 - E}{R}$$

$$\therefore I_0 = \frac{1}{2\pi R} \int_{\alpha}^{\beta} (V_m \sin \omega t - E) d\omega t.$$

$$I_0 = \frac{1}{2\pi R} \left\{ \left[ -V_m \cos \omega t \right]_{\alpha}^{\beta} - \left[ E \omega t \right]_{\alpha}^{\beta} \right\}$$

$$= \frac{-V_m}{2\pi R} [\cos \beta - \cos \alpha] - \frac{E}{2\pi R} [\beta - \alpha]$$

$$I_0 = \frac{V_m}{2\pi R} [\cos \alpha - \cos \beta] - \frac{E}{2\pi R} [\beta - \alpha]$$

$$\gamma = \beta - \alpha \quad ; \quad \therefore \beta = \alpha + \gamma$$

$$\therefore I_0 = \frac{1}{2\pi R} [V_m (\cos \alpha - \cos (\alpha + \gamma)) - E \cdot \gamma]$$

$$\text{W.K.T } \cos \alpha - \cos \gamma = 2 \sin \frac{\alpha + \gamma}{2} \cdot \sin \frac{\gamma - \alpha}{2}$$

$$I_0 = \frac{1}{2\pi R} [V_m \left( 2 \sin \frac{(\alpha + \gamma)}{2} \cdot \sin \frac{\gamma}{2} \right) - E \cdot \gamma]$$

$$I_0 = \frac{1}{2\pi R} [2V_m \sin \left( \alpha + \frac{\gamma}{2} \right) \cdot \sin \frac{\gamma}{2} - E \cdot \gamma]$$

$$V_0 = I_0 R + E = \frac{1}{2\pi} [2V_m \sin \left( \alpha + \frac{\gamma}{2} \right) \cdot \sin \frac{\gamma}{2} - E \cdot \gamma] + E$$

$$= \frac{2V_m \cdot \sin \left( \alpha + \frac{\gamma}{2} \right) \cdot \sin \frac{\gamma}{2}}{2\pi} - \frac{E \cdot \gamma}{2\pi} + E$$

$$V_0 = V_m \sin \left( \alpha + \frac{\gamma}{2} \right) \cdot \sin \frac{\gamma}{2} + E \left( 1 - \frac{\gamma}{2\pi} \right)$$



## 1 $\phi$ FULL WAVE RECTIFIERS:-

They are classified as

a) Fully controlled full wave rectifier.

b) Half controlled full wave rectifier (or) Semi-converter.

### a) Fully controlled full wave rectifier.

There are two type of Full wave rectifiers.

(i) Centre tapped (or) Midpoint type.

(ii) Bridge type.

Note:- (X)

\* The centre - tap rectifier uses 2 SCRs while the bridge type uses 4 SCRs.

\* Their output eqn and waveforms are the same.

\* Only the no of SCRs conducting will change.

\* During +ve half cycle.

In centre tap rectifier  $T_1$  conducts

In bridge rectifier  $T_1, T_2$  will conduct.

\* During -ve half cycle.


In centre tap rectifier  $T_2$  conducts

In bridge rectifier  $T_3, T_4$  will conduct.

Since their aqns and waveforms are same they are explained on comparison.


Centre-tap full wave rectifier with R load:-

(or)  
Midpoint

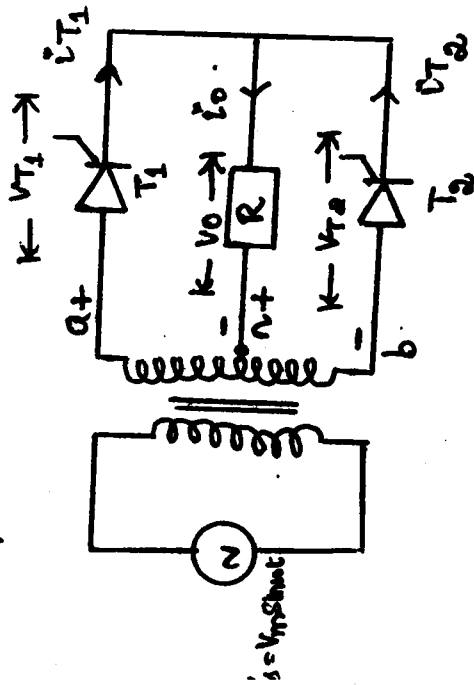

- \*  $V_s = V_m \sin \omega t =$  input supply voltage.
- \* Centre tap transformer is used.
- \*  $n$  is the midpoint of centre tap transformer.
- \* In +ve half cycle terminal 'a' is +ve w.r.t  $n$  and terminal 'b' is -ve w.r.t  $n$ .
- $\therefore V_{an} = V_{nb}$   
(or)  
 $V_{an} = -V_{bn}$
- $V_{an}$  supplies SCR  $T_1$
- $V_{bn}$  supplies SCR  $T_2$ .

Full wave bridge rectifier with R load:-

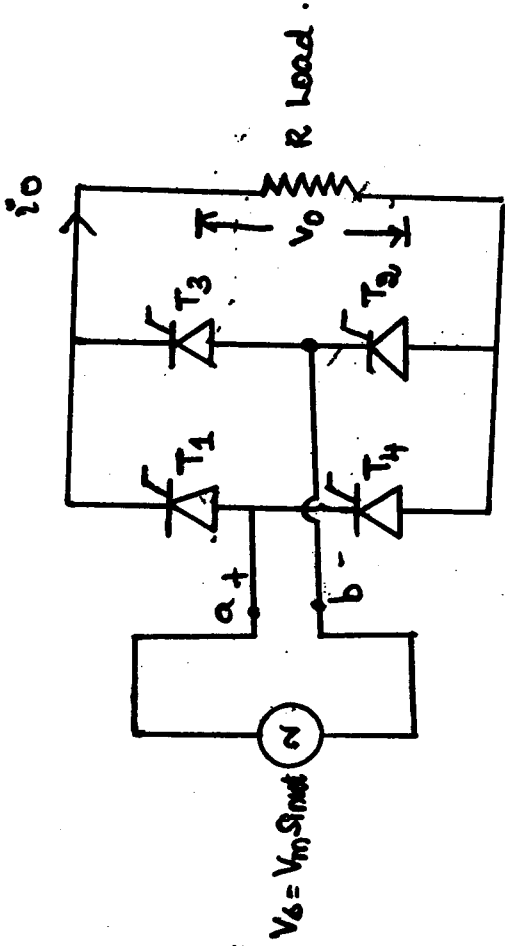

- \*  $V_s = V_m \sin \omega t =$  Supply voltage.
- \* Four SCRs  $T_1, T_2, T_3, T_4$  are used.
- \* In +ve half cycle terminal 'a' is +ve w.r.t. terminal 'b'.
- $\therefore V_{ab} = +V_m \sin \omega t$   
 $V_{ba} = -V_{ab}$
- \*  $V_{ab}$  supplies SCRs  $T_1, T_2$ .
- \*  $V_{ba}$  supplies SCRs  $T_3, T_4$ .

inve-rop rectifier:-

Working:-

Positive half cycle:-

- \* In +ve half cycle terminal 'a' is +ve w.r.t to terminal 'b'
- \* terminal a is +ve.
- \* terminal b is -ve.
- \*  $V_{an} = +V_m \sin \omega t$ .
- \*  $V_{bn} = -V_m \sin \omega t$ .

\*  $V_{an}$  gives supply to SCR  $T_1$ .

SCR  $T_1$  is forward biased by  $V_{ge}$ .

\*  $V_{bn}$  gives supply to SCR  $T_2$ .

SCR  $T_2$  is reverse biased by  $-V_{ge}$ .

\* Only the forward biased SCR can be turned ON.  $\therefore$  SCR  $T_1$  is turned ON at  $\omega t = \alpha$ .

From  $\omega t = 0$  to  $\alpha$

SCR  $T_1$  is forward biased

$\therefore V_{ge}$  across  $T_1 = V_{T1} = V_{an}$

$i_{T1} = 0$  ( $\therefore$  not conducting)

$\therefore i_o = i_{T1} + i_{T2} = 0$

$\therefore V_o = i_o R = 0$

$T_2$  is reverse biased.

$V_{ge}$  across  $T_2 = V_{T2} = V_{bn}$ .

$i_{T2} = 0$  (not conducting)

inve-rop rectifier:-

Working:-

Positive half cycle:-

- \* In +ve half cycle terminal 'a' is +ve w.r.t 'b'
- \* a is +ve; b is -ve.
- \*  $V_{ab} = +V_m \sin \omega t$ .
- \*  $V_{ba} = -V_m \sin \omega t$ .
- \*  $V_{ab}$  supplies SCR  $T_1$  and  $T_2$

So SCR  $T_1$  &  $T_2$  are forward biased in +ve cycle.

\*  $V_{ba}$  supplies SCR  $T_3$  &  $T_4$ .

$\therefore$  SCR  $T_3$  and  $T_4$  are reverse biased in +ve cycle.

SCR  $T_1, T_2$  are turned ON at  $\omega t = \alpha$ .

$\therefore$  load current flows through

$a - T_1 - R - T_2 - b$

From  $\omega t = 0$  to  $\alpha$ .

$T_1, T_2$  are forward biased.

$\therefore V_{T1} = V_{T2} = V_{ab}$


$i_{T1} = i_{T2} = 0$

$T_3, T_4$  are reverse biased

$\therefore V_{T3} = V_{T4} = V_{ba}$

$i_{T3} = i_{T4} = 0$

$\therefore i_o = i_o = 0$

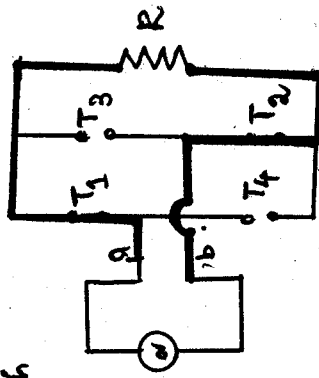

At  $\omega t = \alpha$ , SCR  $T_1$  is turned ON.

$\therefore$  From  $\omega t = \alpha$  to  $\pi$

SCR  $T_1$  remains ON.

$\therefore$  Vge across SCR  $T_1 = V_{T1} = 0$   
current through  $T_1 = i_{T1} = I_{avg}$

$T_2$  is OFF

$$\therefore V_{T2} = V_{bn}$$

$$i_{T2} = 0$$

$$\therefore i_o = i_{T1} + i_{T2} = i_{T1}$$

$$\therefore V_o = I_o R = i_{T1} R$$

During -ve half cycle.

In -ve half cycle terminal a is +ve w.r.t. terminal b; i.e.  $a = -ve$ ;  $b = +ve$

$$\therefore V_{an} = -V_m \sin \omega t; V_{bn} = +V_m \sin \omega t$$

$\therefore$   $V_{an}$  is -ve at  $\pi$ , SCR  $T_1$  is reverse biased due to -ve Vge  $V_{an}$  and is turned OFF at  $\omega t = \pi$ .

\* But SCR  $T_2$  is forward biased due to +ve Vge  $V_{bn}$ .

\* SCR  $T_2$  is triggered at an angle

$$\omega t = \pi + \alpha$$

Full wave bridge

At  $\omega t = \alpha$ ; SCRs  $T_1, T_2$  are turned ON.

$\therefore$  From  $\omega t = \alpha$  to  $\pi$

$T_1, T_2$  are ON

$T_3, T_4$  are OFF and reverse biased.

$$\therefore V_{T1} = V_{T2} = 0$$

$$i_{T1} = i_{T2} = I_o = I_{avg}$$

$$V_o = V_{ab} = I_o R$$

$$V_{T3} = V_{T4} = V_{ba}$$

$$i_{T3} = i_{T4} = 0$$

During -ve half cycle.

\* In -ve half cycle terminal a is -ve w.r.t. b;  $a = -ve$ ;  $b = +ve$ .


$$\therefore V_{ab} = -V_m \sin \omega t; V_{ba} = +V_m \sin \omega t$$

$\therefore$   $V_{ab} = -ve$  at  $\omega t = \pi$ ; SCRs  $T_1, T_2$  are turned OFF at  $\omega t = \pi$  due to -ve Vge.

$\therefore$  But since  $V_{ba}$  is +ve; SCRs  $T_3, T_4$  are forward biased.

\* SCRs  $T_3, T_4$  are turned ON at

$$\omega t = \pi + \alpha$$

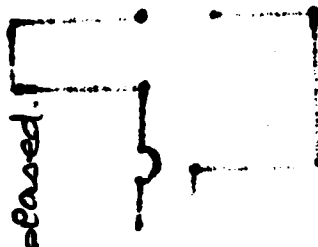

current thy rectifier.

from  $\omega t = \pi$  to  $\pi + \alpha$ .

$T_1$  is OFF at  $\omega t = \pi$

$$\therefore V_{T_1} = V_{an}$$

$$i_{T_1} = 0$$

$T_2$  is forward biased at  $\omega t = \pi$

$$\therefore V_{T_2} = V_{on}$$

$$i_{T_2} = 0$$

$$\therefore i_0 = i_{T_1} + i_{T_2} = 0$$

$$V_0 = i_0 R = 0$$

From  $\omega t = \pi + \alpha$  to  $2\pi$ .

at  $\pi + \alpha$ , SCR  $T_2$  is turned ON

$$\therefore V_{T_2} = 0$$

$i_{T_2}$  is increasing  $\uparrow$

$T_1$  is OFF;  $\therefore V_{T_1} = V_{an}$

$$i_{T_1} = 0$$

$$\therefore i_0 = i_{T_1} + i_{T_2} = i_{T_2}$$

$$V_0 = i_0 R = i_{T_2} * R$$

from  $\omega t = \pi$  to  $\pi + \alpha$

$T_1, T_2$  are turned OFF at  $\omega t = \pi$

$$\therefore V_{T_1} = V_{T_2} = V_{ab}$$

$$i_{T_1} = i_{T_2} = 0$$

$T_3, T_4$  are forward biased at  $\omega t = \pi$

$$\therefore V_{T_3} = V_{T_4} = V_{ba}$$

$$i_{T_3} = i_{T_4} = 0$$

$$i_0 = 0$$

$$V_0 = 0$$

From  $\omega t = \pi + \alpha$  to  $2\pi$ .

at  $\pi + \alpha$ , SCR  $T_3, T_4$  is turned ON.


$$\therefore V_{T_3} = V_{T_4} = 0 \quad V_{T_1} = V_{T_2} = V_{ab}$$



$$i_{T_3} = i_{T_4} = \uparrow \quad i_{T_1} = i_{T_2} = 0$$

$\therefore i_0$  is  $\uparrow$

$$V_0 = V_{ba}$$

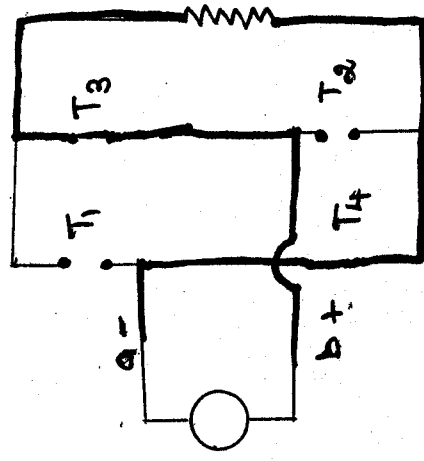$i_0$  flows through  
b -  $T_3$  - R -  $T_4$  - a.



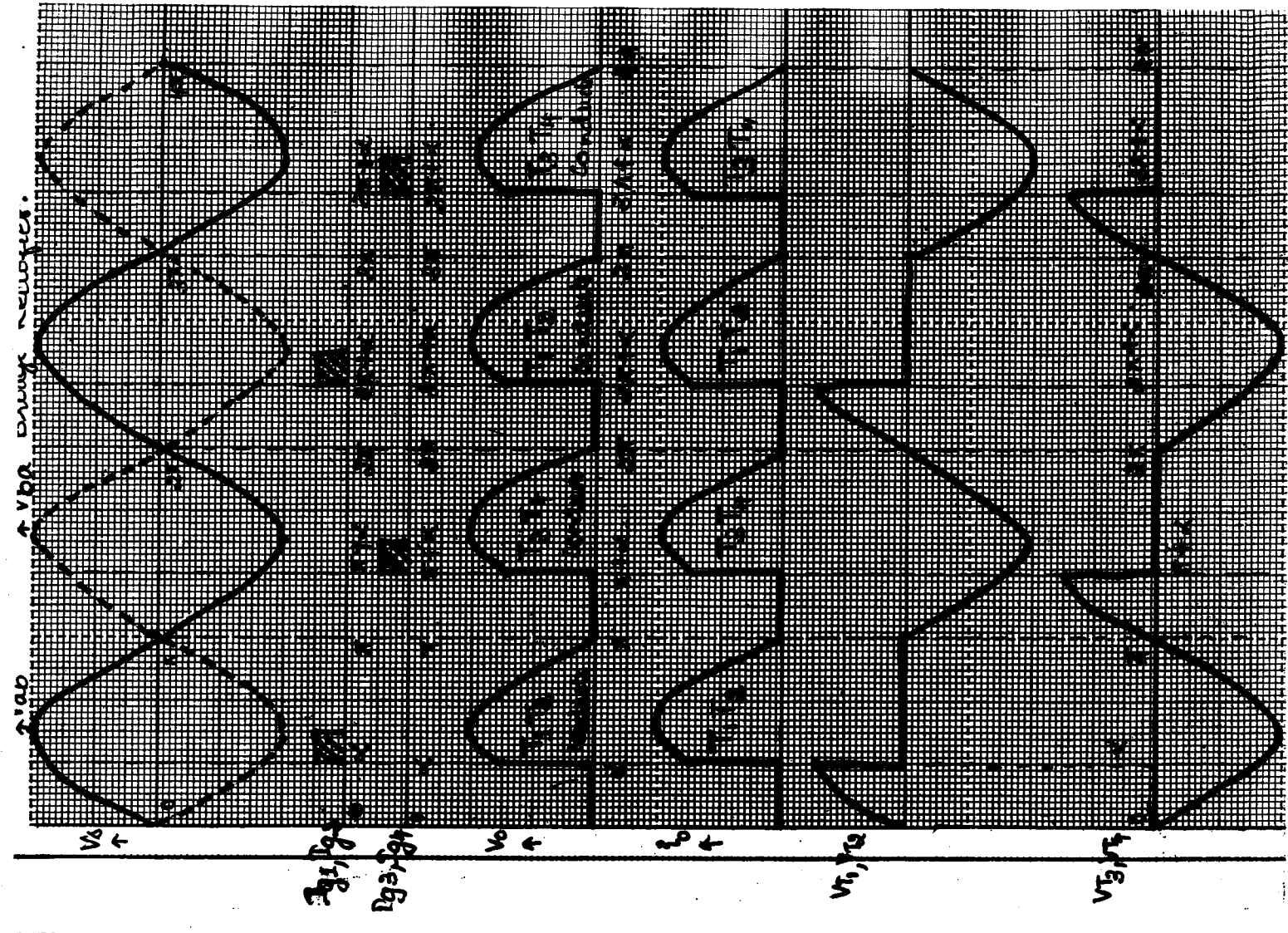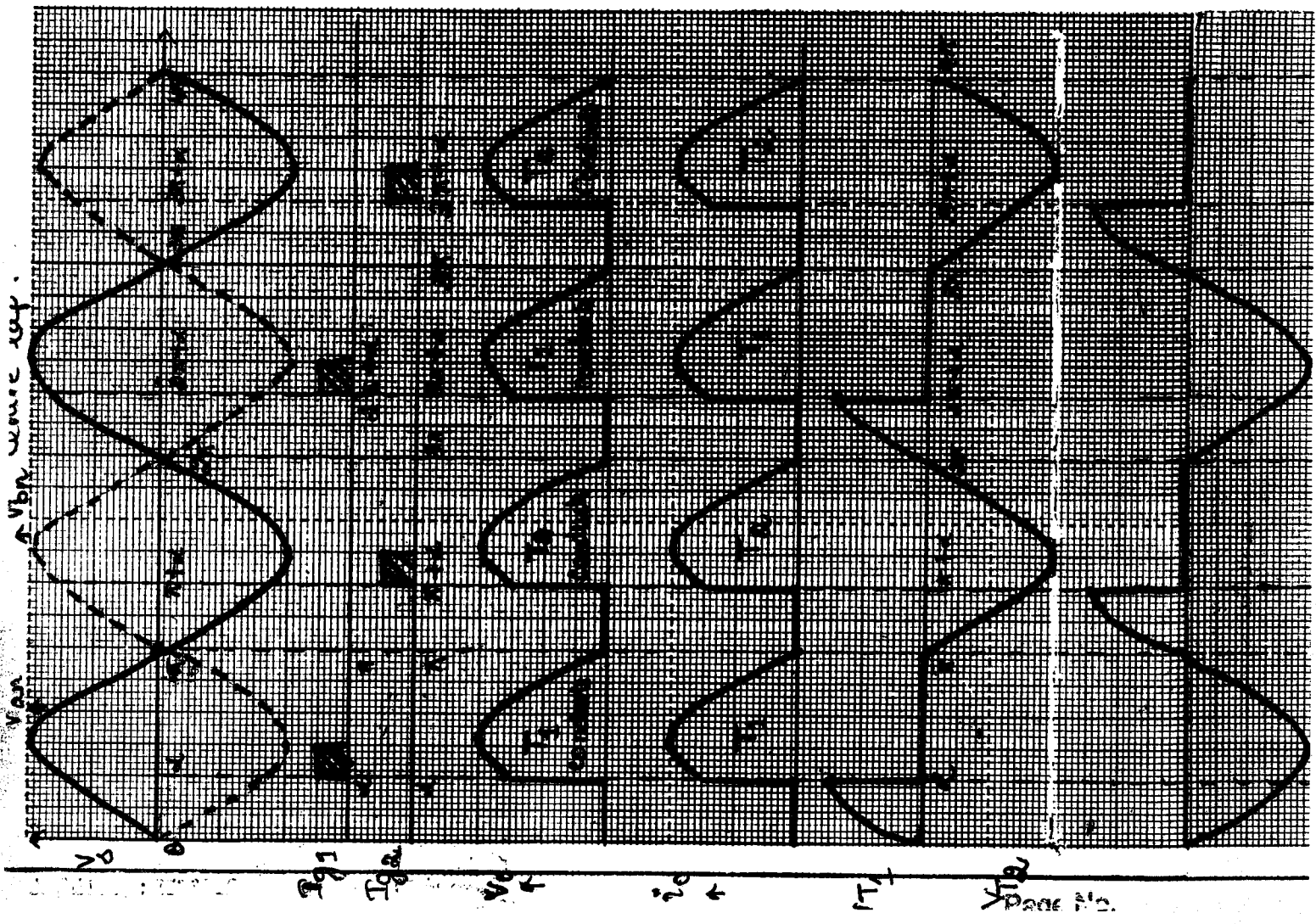

average

$$V_o(\text{avg}) = \frac{1}{\pi} \int_{\alpha}^{\pi} V_m \sin \omega t \cdot d\omega t = \frac{V_m}{\pi} \int_{\alpha}^{\pi} \sin \omega t \cdot d\omega t$$

$$= \frac{V_m}{\pi} [-\cos \omega t]_{\alpha}^{\pi} = -\frac{V_m}{\pi} [\cos \pi - \cos \alpha]$$

$$= -\frac{V_m}{\pi} [-1 - \cos \alpha] = \frac{V_m}{\pi} [1 + \cos \alpha]$$

$$\therefore V_o(\text{avg}) = \frac{V_m}{\pi} [1 + \cos \alpha]$$

$$I_o(\text{avg}) = \frac{V_o(\text{avg})}{R} = \frac{V_m}{\pi R} [1 + \cos \alpha]$$

$$V_{\text{orms}} = \sqrt{\frac{1}{\pi} \int_{\alpha}^{\pi} V_m^2 \sin^2 \omega t \cdot d\omega t}$$

$$= \sqrt{\frac{V_m^2}{\pi} \int_{\alpha}^{\pi} (1 - \cos 2\omega t) d\omega t}$$

$$= \sqrt{\frac{V_m^2}{2\pi} \left\{ [\omega t]_{\alpha}^{\pi} - \left[ \frac{\sin 2\omega t}{2} \right]_{\alpha}^{\pi} \right\}}$$

$\sin 2\pi = 0$

$$= \sqrt{\frac{V_m^2}{2\pi} \left\{ [\pi - \alpha] - \frac{1}{2} [\sin 2\pi - \sin 2\alpha] \right\}}$$

$$V_{\text{orms}} = \frac{V_m}{\sqrt{2\pi}} \sqrt{\pi - \alpha + \frac{1}{2} \sin 2\alpha}$$

$$I_{\text{orms}} = V_{\text{orms}} / R$$

Average value of voltages.

$$V_o(\text{avg}) = \frac{1}{\pi} \int_{\alpha}^{\pi} V_m \sin \omega t \cdot d\omega t$$

$$V_o(\text{avg}) = \frac{V_m}{\pi} [1 + \cos \alpha]$$

$$I_o(\text{avg}) = \frac{V_o(\text{avg})}{R} = \frac{V_m}{\pi R} [1 + \cos \alpha]$$

← derivation done in centre tap

$$V_{\text{orms}} = \sqrt{\frac{1}{\pi} \int_{\alpha}^{\pi} V_m^2 \sin^2 \omega t \cdot d\omega t}$$

$$V_{\text{orms}} = \frac{V_m}{\sqrt{2\pi}} \sqrt{\pi - \alpha + \frac{1}{2} \sin 2\alpha}$$

$$I_{\text{orms}} = \frac{V_{\text{orms}}}{R} = \frac{V_m}{R\sqrt{2\pi}} \sqrt{\pi - \alpha + \frac{1}{2} \sin 2\alpha}$$


$$P = V_{\text{orms}} \cdot I_{\text{orms}}$$

[From all above it's seen that the waveforms, eqns and working for centre tap and bridge rectifier are same. Only the no of SCRs conducting vary.]

\* NOTE:-

and midpoint or centre tap rectifier  
 Similarly even for bridge rectifier with RL, RLE load  
 the eqns and waveforms will remain the same.

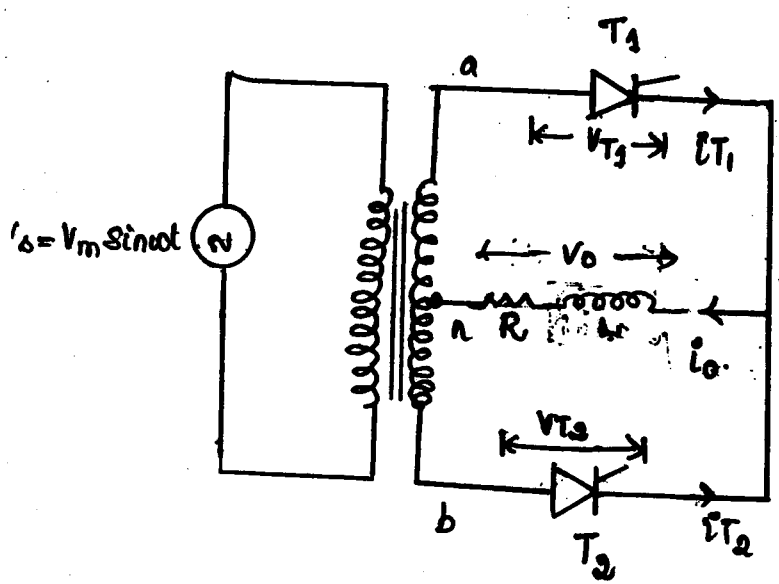MIDPOINT OR CENTRE TAPPED RECTIFIER WITH RL load:-



\* In +ve half cycle terminal a is +ve w.r.t. terminal b.

∴  $V_{an} = +V_m \sin \omega t$   
 $V_{bn} = -V_m \sin \omega t$

$V_{an}$  supplies  $T_1$   
 $V_{bn}$  supplies  $T_2$ .

- ∴ SCR  $T_1$  is forward biased in +ve half cycle.
- ∴ SCR  $T_2$  is reverse biased in +ve half cycle.

At  $\omega t = \alpha$  SCR  $T_1$  is turned ON.

From  $\omega t = 0$  to  $\alpha$ , SCR  $T_1$  is forward biased,  $T_2$  is reverse biased. [FB]

Vge across SCR  $T_1 = V_{T1} = V_{an}$  [FB]  
 " " "  $T_2 = V_{T2} = V_{bn}$ .  
 $i_{T1} = 0$ ;  
 $i_{T2} = 0$

∴  $i_o = 0$ ;  $V_o = 0$ .



+

At  $\omega t = \alpha$  SCR  $T_1$  is ON.

From  $\omega t = \alpha$  to  $\pi$ ;

SCR  $T_1$  is ON;  $T_2$  is Reverse biased. (RB)

$\therefore V_{ge}$  across SCR  $T_1 = V_{T1} = 0$ .

Due to Inductive load current thro' SCR  $T_1$  increases very slowly, so load current  $i_o = i_{T1} \uparrow$ .

$\therefore i_o \uparrow$  very slowly and reaches maximum value at  $\omega t = \pi$ .

$i_{T2} = 0$

$V_{T2} = V_{bn}$ .

At  $\omega t = \pi$  [During -ve half cycle]

\* At  $\omega t = \pi$ ;  $V_{ge}$  across SCR  $T_1$  is Reverse biased.

[ $\therefore a$  is -ve;  $b$  is +ve;  $V_{an} = -V_m \sin \omega t$ ;  $V_{bn} = +V_m \sin \omega t$ ]

\* SCR  $T_2$  is forward biased.

But,

\* SCR  $T_1$  does not turn OFF due to the reverse voltage

at  $\omega t = \pi$ ; the current  $i_o$  has not dropped below holding current.

\* It takes some time to drop to zero. The time taken by the current to fall to zero is " $\beta$ ". It is also called as extinction angle.

Based on the value of  $\beta$  we can divide the operation into two modes.

a) discontinuous mode. ( $\alpha > \beta$ ) (or)  $\beta < \alpha$

b) continuous mode. ( $\alpha = \beta$ )

a) discontinuous mode! -  $\alpha > \beta$

\* when  $\beta$  is less than  $\alpha$ , the current reaches to zero before the turning ON of the next SCR at  $\alpha$ .

b) continuous mode:  $\alpha = \beta$ .

\* when  $\alpha = \beta$  the current reaches to zero at the time when the next SCR is turned ON.

∴ From  $\pi$  to  $\beta$ .

$i_o$  gradually reduces and falls to zero and so SCR  $T_1$  is

turned OFF at  $\omega t = \beta$ .

$$V_{T_1} = 0 \text{ till } \beta$$

$$V_{T_1} = V_{an} \text{ at } \beta$$

$$V_{T_2} = V_{bn}$$

$$i_o = 0 \text{ at } \beta.$$

$$V_o = V_{an} \text{ till } \beta.$$

From  $\beta$  to  $\pi + \alpha$ :-

$$V_o = 0$$

$$i_o = 0$$

$$V_{T_1} = V_{an}$$

$$V_{T_2} = V_{bn}$$

At  $\pi + \alpha$ ,

At  $\omega t = \pi + \alpha$ , SCR  $T_2$  is ON. SCR  $T_1$  is RB.

$$\therefore V_{T_2} = 0$$

$$V_{T_1} = V_{an}.$$

$$i_{T_1} = 0$$

$i_{T_2} =$  slowly  $\uparrow$  due to RL load.

$i_o =$  " " " " " "

$$V_o = V_{bn}.$$

At  $\omega t = 2\pi$ : SCR  $T_2$  is RB, but does not turn OFF due to  $i_o$ .

At  $\omega t = 2\pi + \beta$ :  $i_o \downarrow$  to zero SCR  $T_2$  is OFF.

∴ at  $\omega t = \beta$ ;  $V_o = 0$ ;  $i_o = 0$ ;  $V_{T_2} = V_{bn}$ ;  $V_{T_1} = V_{an}$ .

Equations for discontinuous mode:-

$$V_0(\text{avg}) = \frac{1}{\pi} \int_{\alpha}^{\beta} V_m \sin \omega t \, d\omega t = \frac{V_m}{\pi} [-\cos \omega t]_{\alpha}^{\beta}$$

$$= -\frac{V_m}{\pi} [\cos \beta - \cos \alpha] = \frac{V_m}{\pi} [\cos \alpha - \cos \beta]$$

$$\therefore V_0(\text{avg}) = \frac{V_m}{\pi} [\cos \alpha - \cos \beta]$$

$$I_0(\text{avg}) = \frac{V_0(\text{avg})}{R} = \frac{V_m}{\pi R} [\cos \alpha - \cos \beta]$$

$$V_{\text{orms}} = \sqrt{\frac{1}{\pi} \int_{\alpha}^{\beta} V_m^2 \sin^2 \omega t \, d\omega t}$$


$$= \sqrt{\frac{V_m^2}{\pi} \int_{\alpha}^{\beta} (1 - \cos 2\omega t) \, d\omega t}$$

$$= \sqrt{\frac{V_m^2}{2\pi} [\omega t]_{\alpha}^{\beta} - \left(\frac{\sin 2\omega t}{2}\right)_{\alpha}^{\beta}}$$

$$V_{\text{orms}} = \frac{V_m}{\sqrt{2\pi}} \sqrt{[\beta - \alpha] - \frac{1}{2} [\sin 2\beta - \sin 2\alpha]}$$

$$I_{\text{orms}} = \frac{V_{\text{orms}}}{R}$$
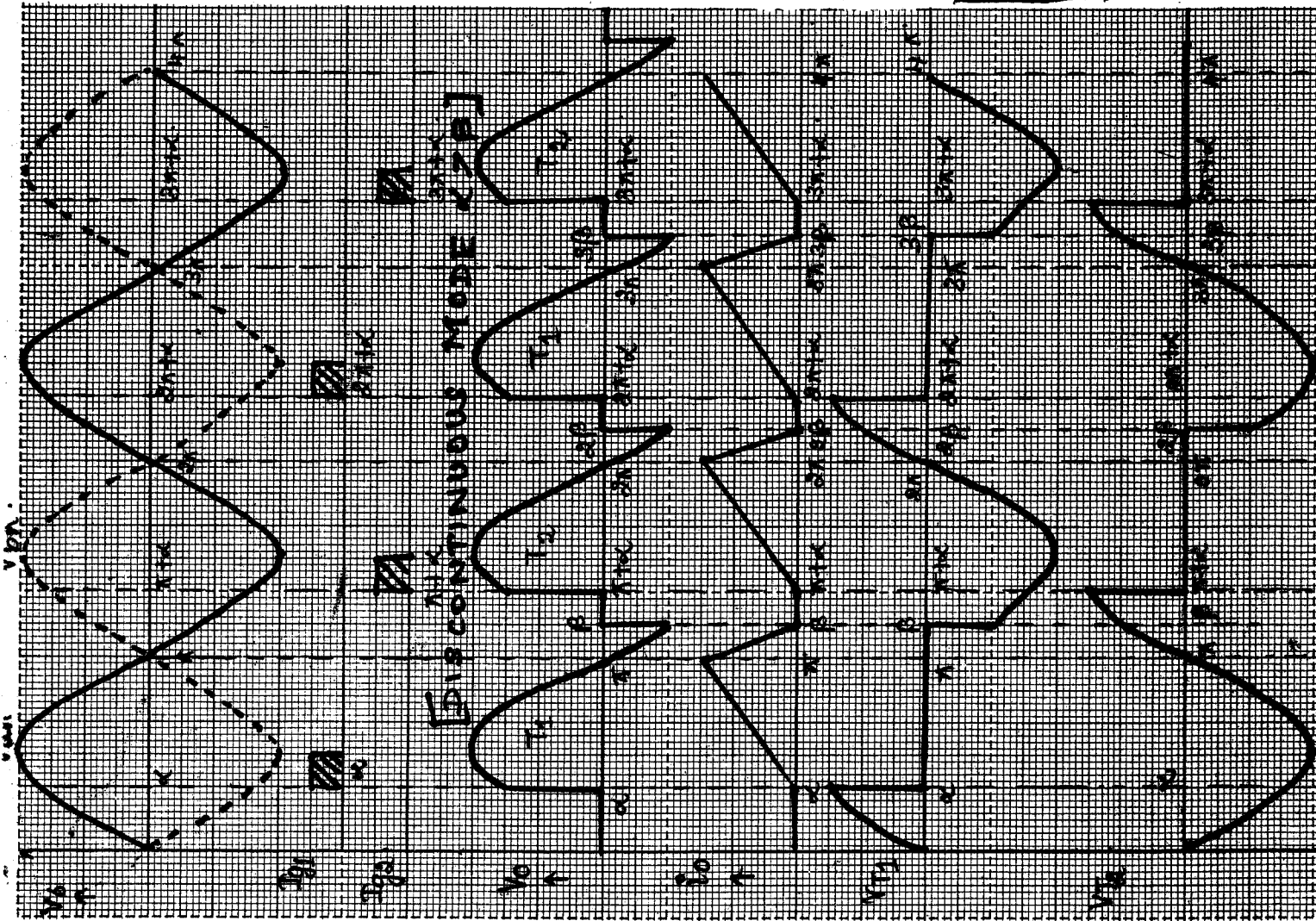
$$P = V_{\text{orms}} \times I_{\text{orms}}$$



for continuous mode:

$$V_o(\text{avg}) = \frac{1}{\pi} \int_{\alpha}^{\pi+\alpha} V_m \sin \omega t \, d\omega t$$

$$= \frac{V_m}{\pi} [\cos \omega t]_{\alpha}^{\pi+\alpha}$$

$$\cos(\pi+\alpha) = -\cos \alpha$$

$$= -\frac{V_m}{\pi} [\cos(\pi+\alpha) - \cos \alpha]$$

$$= -\frac{V_m}{\pi} [-\cos \alpha - \cos \alpha] = \frac{V_m}{\pi} [2 \cos \alpha]$$

$$V_o(\text{avg}) = 2 \frac{V_m}{\pi} \cos \alpha$$


$$V_o(\text{rms}) = \sqrt{\frac{1}{\pi} \int_{\alpha}^{\pi+\alpha} V_m^2 \sin^2 \omega t \, d\omega t}$$

$$= \frac{V_m}{\sqrt{\pi}} \int_{\alpha}^{\pi+\alpha} (1 - \cos 2\omega t) \, d\omega t$$


$$= \frac{V_m}{\sqrt{2\pi}} \left[ \omega t - \frac{1}{2} \sin 2\omega t \right]_{\alpha}^{\pi+\alpha}$$

$$= \frac{V_m}{\sqrt{2\pi}} \left[ (\pi+\alpha-\alpha) - \frac{1}{2} [\sin 2(\pi+\alpha) - \sin 2\alpha] \right]$$
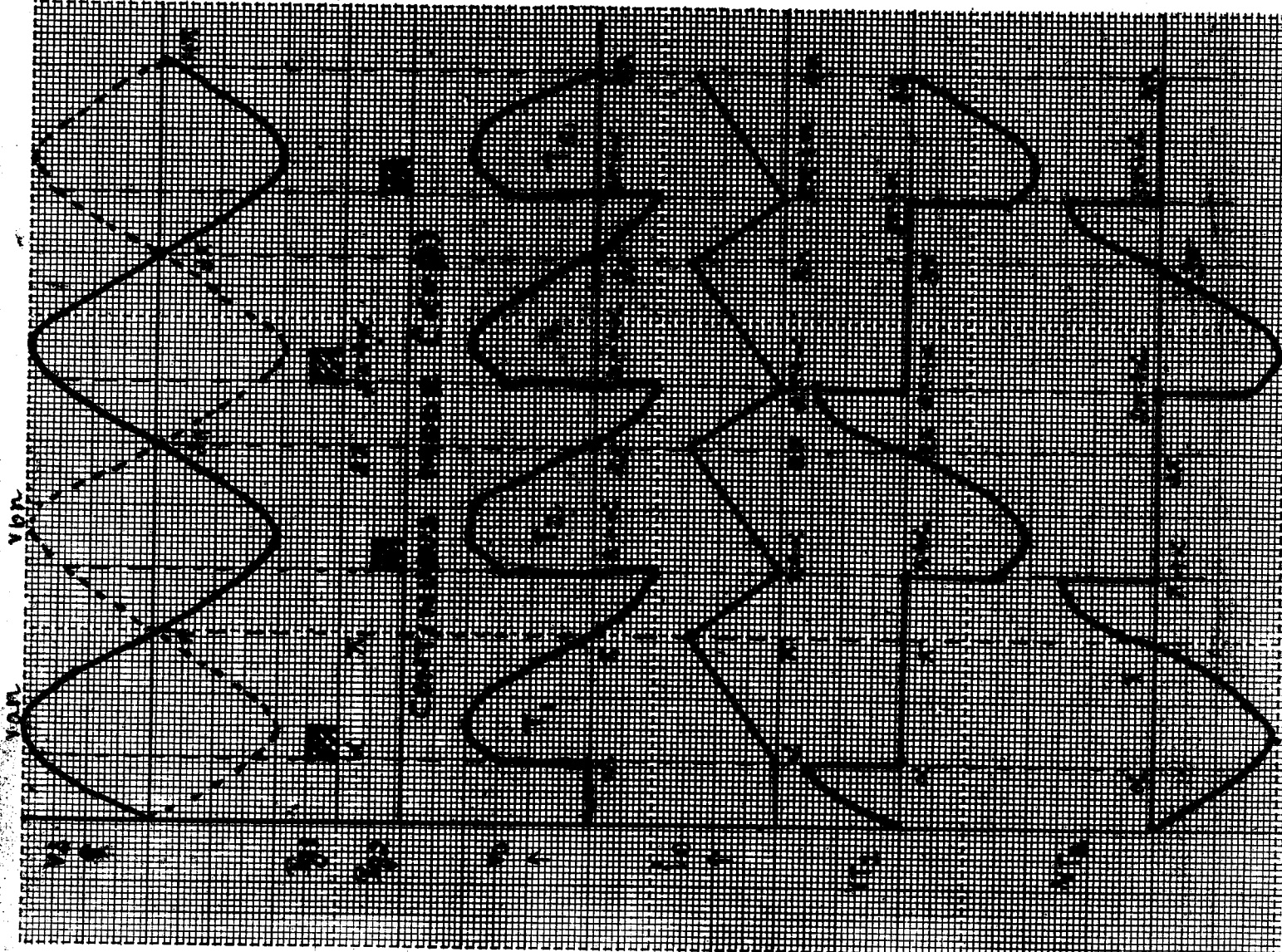
$$V_o(\text{rms}) = \frac{V_m}{\sqrt{2\pi}} \left[ \pi - \frac{1}{2} [\sin 2(\pi+\alpha) - \sin 2\alpha] \right]$$


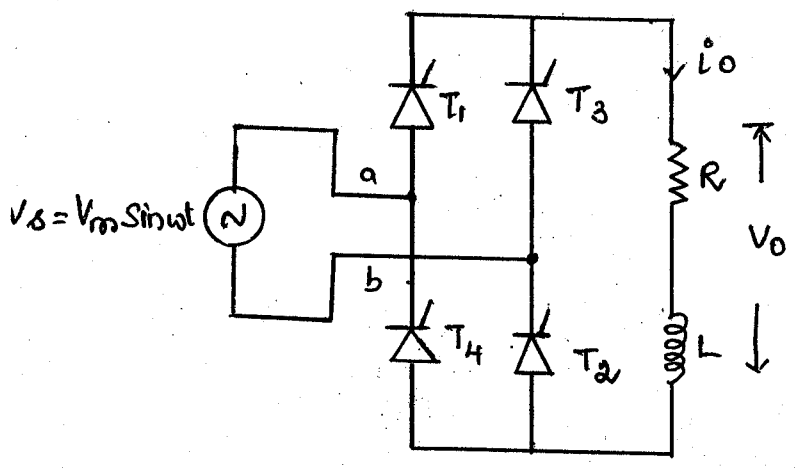
# 1 $\phi$ FULL WAVE BRIDGE RECTIFIER WITH RL LOAD:-




- \*  $V_s = V_m \sin \omega t = \text{Supply } V_{ge}$ .
- \* SCRs  $T_1, T_2$  conduct in +ve half cycle.
- \* SCRs  $T_3, T_4$  conduct in -ve half cycle.

## \* In +ve half cycle:-

- \* In +ve half cycle terminal 'a' is +ve w.r.t. terminal 'b'.
- \* a is +ve; b is -ve.
- \*  $V_{ab} = +V_m \sin \omega t$ .
- \*  $V_{ba} = -V_m \sin \omega t$ .
- \*  $V_{ab}$  supplies SCRs  $T_1, T_2$  so they are forward biased.
- \*  $V_{ba}$  supplies SCRs  $T_3, T_4$ , so they are reverse biased.
- \* SCR  $T_1, T_2$  are turned on at  $\omega t = \alpha$ .
- $\therefore$  load current flows through  $a - T_1 - R - L - T_2 - b$ .
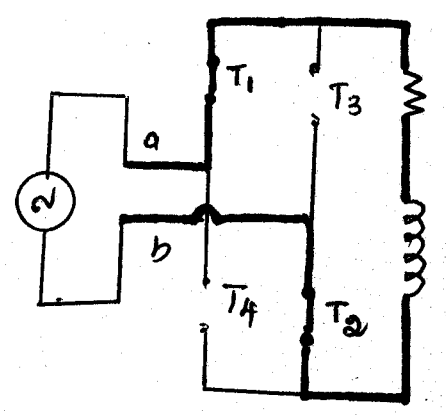
## From $\omega t = 0$ to $\alpha$ ,

- \* SCR  $T_1, T_2$  is FB
- \* SCR  $T_3, T_4$  is RB
- $V_{T_1} = V_{T_2} = V_{ab}$
- $V_{T_3} = V_{T_4} = V_{ba}$
- $i_o = 0$
- $v_o = 0$



At  $\omega t = \alpha$  SCR  $T_1, T_2$  are turned ON.

From  $\omega t = \alpha$  to  $\pi$ .

\* SCR  $T_1, T_2$  are ON

\*  $\therefore V_{T_1} = V_{T_2} = 0$

\* Due to inductive load current through SCR  $T_1, T_2$   $\uparrow$ es very slowly.  $\therefore i_o =$  increases slowly.

\*  $i_o = \uparrow$ es and reaches maximum at  $\omega t = \pi$ .

\*  $V_o = V_s$

At  $\omega t = \pi$  [During -ve half cycle]:-

\* At  $\omega t = \pi$ , SCR  $T_1, T_2$  are reverse biased.

[ $\because$  in -ve cycle, a is -ve, b is +ve;  $\therefore V_{ab} = -V_m \sin \omega t$ ;  $V_{ba} = +V_m \sin \omega t$ ]

\* SCR  $T_3, T_4$  are forward biased.

\* Though SCR  $T_1, T_2$  are reverse biased at  $\omega t = \pi$ , they do not turn OFF because the current  $i_o$  does not drop below holding current.

\*  $i_o$  takes some time to fall to zero. The time taken by  $i_o$  to fall to zero is " $\beta$ ". It is called extinction angle.

Based on the value of  $\beta$  we can divide the operation into two modes.

a) discontinuous mode ( $\alpha > \beta$ )

... when  $\beta$  is less than  $\alpha$ ,  $i_o$  reaches zero at  $\beta$  before the turning ON of the next SCR at  $\alpha$ .

b) continuous mode: ( $\alpha = \beta$ )

... when  $\alpha = \beta$  the current reaches to zero at the same time when the next SCR is turned ON.

∴ From  $\pi$  to  $\beta$  :-

\*  $i_o$  gradually reduces and falls to zero at  $\omega t = \beta$ .

∴ SCR  $T_1, T_2$  is turned OFF at  $\omega t = \beta$ .

∴  $V_{T1} = V_{T2} = 0$  till  $\beta$ .

$V_{T3} = V_{T4} = V_{ba}$

$i_o = 0$  at  $\beta$ .

$V_o = V_{ab}$  till  $\beta$ .

From  $\beta$  to  $\pi + \alpha$  :- NO SCR conducts.

$V_o = 0$

$T_1, T_2 = RB$

$i_o = 0$

$T_3, T_4 = FB$

$V_{T1} = V_{T2} = V_{ab}$

$V_{T3} = V_{T4} = V_{ba}$ .

At  $\omega t = \pi + \alpha$

At  $\omega t = \pi + \alpha$  SCR  $T_3, T_4$  is turned ON.

∴  $V_{T3} = V_{T4} = 0$

SCR  $T_1, T_2$  are RB, ∴  $V_{T1} = V_{T2} = V_{ab}$

$i_o =$  slowly  $\uparrow$  due to RL load.

$V_o = V_b$ .

\*  $i_o$  flows through  $b - T_3 - R - L - T_4 - a$ .

At  $\omega t = 2\pi$  :-

\* SCR  $T_3, T_4$  is FB, but does not turn OFF because  $i_o$  is not less than holding current.


∴  $V_o = V_{ba}$ .

At  $\omega t = 2\pi + \beta$

\*  $i_o \downarrow$  to zero ∴ SCR  $T_3, T_4$  is OFF.

∴ at  $\omega t = 2\pi + \beta$ ,  $V_o = 0$ ;  $i_o = 0$ ,  $V_{T3} = V_{T4} = V_{ba}$

$V_{T1} = V_{T2} = V_{ab}$ .

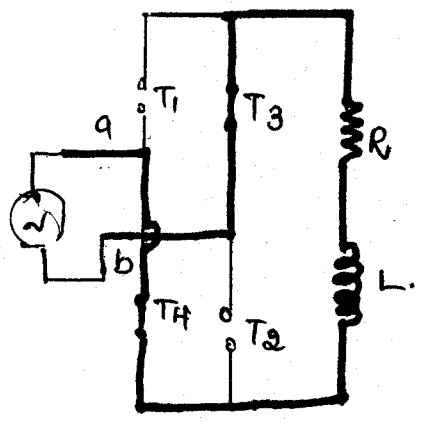

Equations for discontinuous mode:-

$$V_o(\text{avg}) = \frac{1}{\pi} \int_{\alpha}^{\beta} V_m \sin \omega t \cdot d\omega t$$

$$V_o(\text{avg}) = \frac{V_m}{\pi} [\cos \alpha - \cos \beta]$$

already solved in page (62)


$$I_o(\text{avg}) = \frac{V_m}{\pi R} [\cos \alpha - \cos \beta]$$

$$V_o(\text{rms}) = \sqrt{\frac{1}{\pi} \int_{\alpha}^{\beta} V_m^2 \sin^2 \omega t \cdot d\omega t}$$

$$V_o(\text{rms}) = \frac{V_m}{\sqrt{2\pi}} \left[ \beta - \alpha \right] - \frac{1}{2} \left[ \sin 2\beta - \sin 2\alpha \right]$$

$$P_{\text{orms}} = \frac{V_{\text{orms}}^2}{R}$$
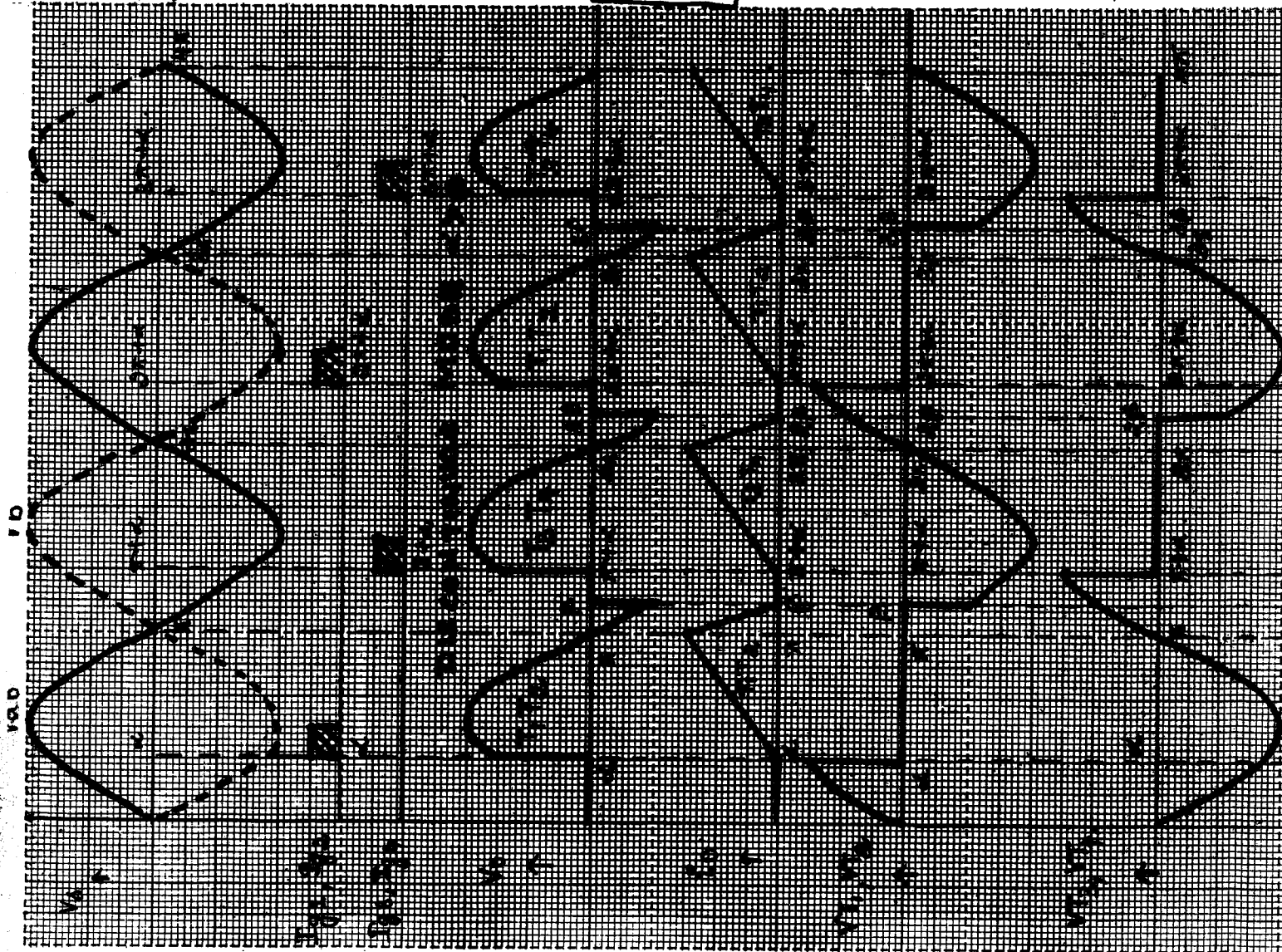
$$P = V_{\text{orms}} \times I_{\text{orms}}$$





Egns for continuous mode:-

$$V_o(\text{avg}) = \frac{1}{\pi} \int_{\alpha}^{\pi+\alpha} V_m \sin \omega t \cdot dt$$


$$V_o(\text{avg}) = \frac{2V_m}{\pi} \cos \alpha$$

$$V_{orms} = \sqrt{\frac{1}{\pi} \int_{\alpha}^{\pi+\alpha} V_m^2 \sin^2 \omega t \cdot dt}$$


$$V_{orms} = \frac{V_m}{\sqrt{2\pi}} \sqrt{\pi - \frac{1}{2} [\sin 2(\pi+\alpha) - \sin 2\alpha]}$$

$$P = V_{orms} \cdot I_{orms}$$

$$I_{orms} = \frac{V_{orms}}{R}$$

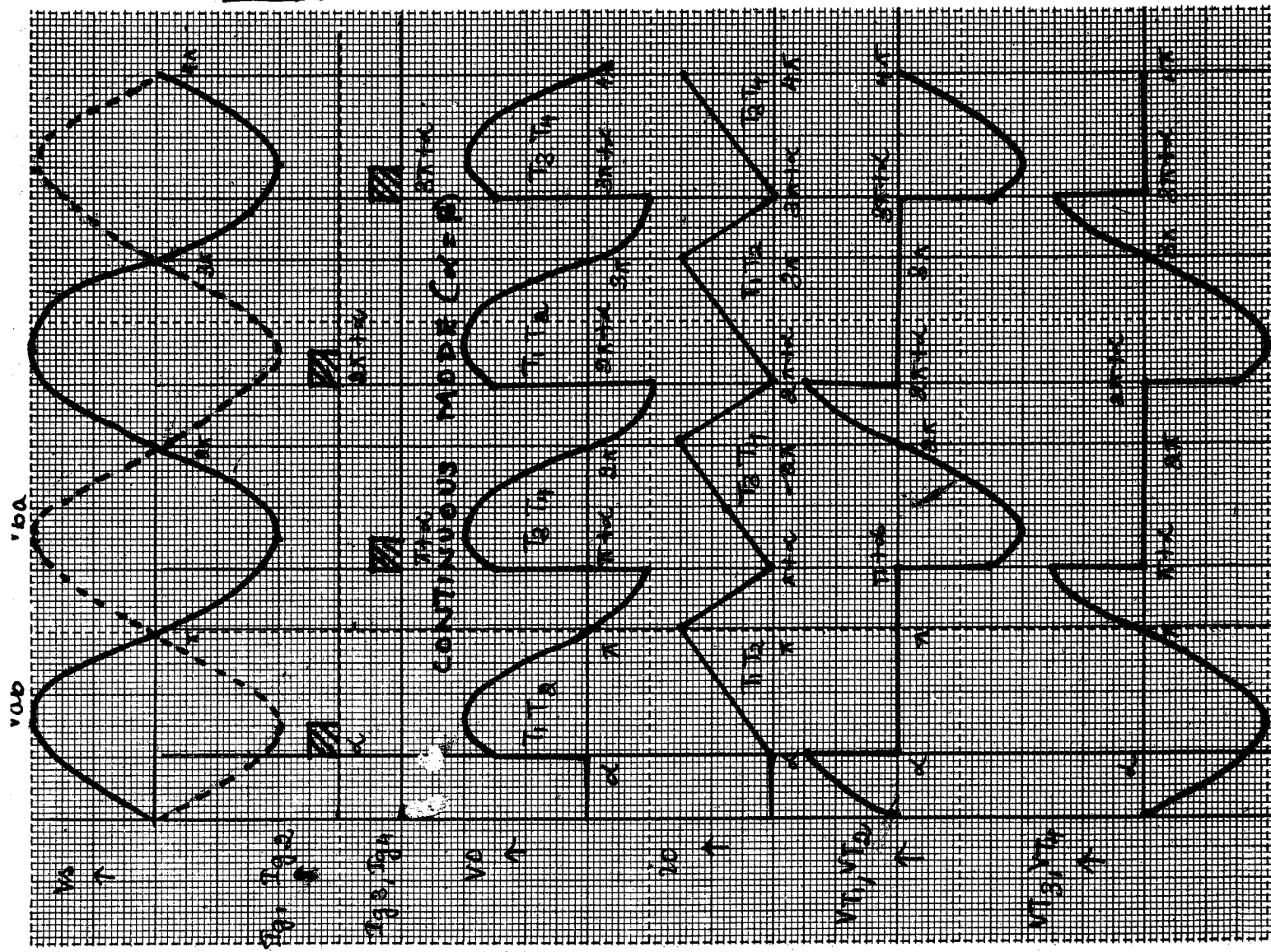

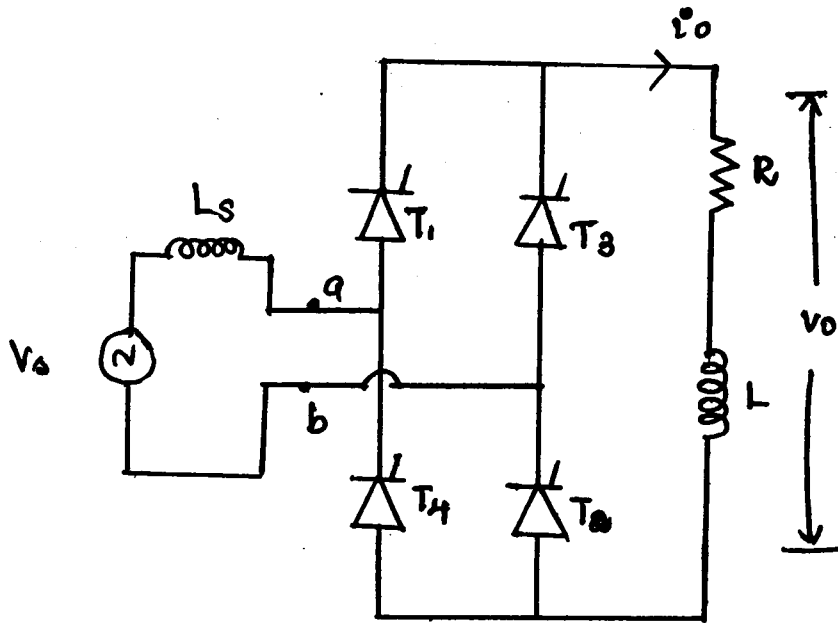
# EFFECT OF SOURCE INDUCTANCE ( $L_s$ ) ON PERFORMANCE OF RECTIFIER WITH RL LOAD



$L_s$  = Source Inductance

$L$  = Load Inductance.

Equivalent circuit:

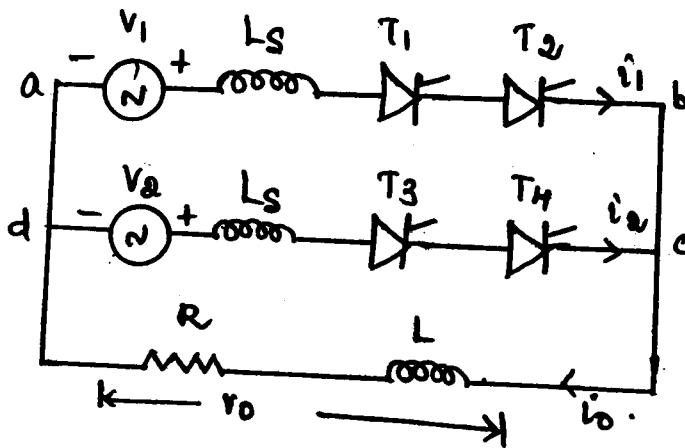

\* Load current  $i_o$  is assumed constant.

\* when terminal 'a' of source  $v_{ge}$  is +ve, current  $i_1$  flows thro'  $L_s, T_1$ , load and  $T_2$  and this is shown in equivalent circuit as  $V_1 - L_s - T_1 - T_2 - RL$  load.

\* when terminal 'b' of source  $v_{ge}$  is +ve; current  $i_2$  flows thro'  $L_s, T_3$ , load,  $T_4$  and this is shown in equiv ckt as  $V_2 - L_s - T_3 - T_4 - RL$  load.

+

\* when  $T_1, T_2$  are triggered at firing angle  $\alpha$ , the SCRs  $T_3, T_4$  which have been already conducting will be commutating.

\* i.e., the current through the incoming SCRs  $T_1, T_2$  builds up very slowly, whereas due to presence of source inductance ( $L_s$ ) the current through the outgoing SCRs  $T_3, T_4$  decreases very slowly.

\*  $\therefore$  during this period all 4 SCRs  $T_1, T_2, T_3, T_4$  are conducting. This period is called as overlap period and the angle is called as overlap angle " $\mu$ ".

Working:-

From  $(\alpha + \mu$  to  $\pi + \alpha)$ :-

\* From  $\omega t = \alpha + \mu$  to  $\pi + \alpha$ , SCRs  $T_1$  and  $T_2$  will be conducting.

\* At  $\omega t = \pi + \alpha$ , the supply vge is -ve.

\* SCRs  $T_3$  and  $T_4$  are triggered at  $\omega t = \pi + \alpha$ .  $\therefore$

Current through  $T_3, T_4$  <sup>↑</sup>es slowly.


\* At  $\omega t = \pi + \alpha$ , SCRs  $T_1, T_2$  does not turn OFF because energy stored in source inductance ( $L_s$ ) induces a vge

that fwd biases  $T_1, T_2$ .


$\therefore$  from  $\omega t = \pi + \alpha$  to  $\omega t = \pi + \alpha + \mu$  SCRs  $T_1, T_2$ ,

$T_3, T_4$  are conducting. This period is called overlap period.

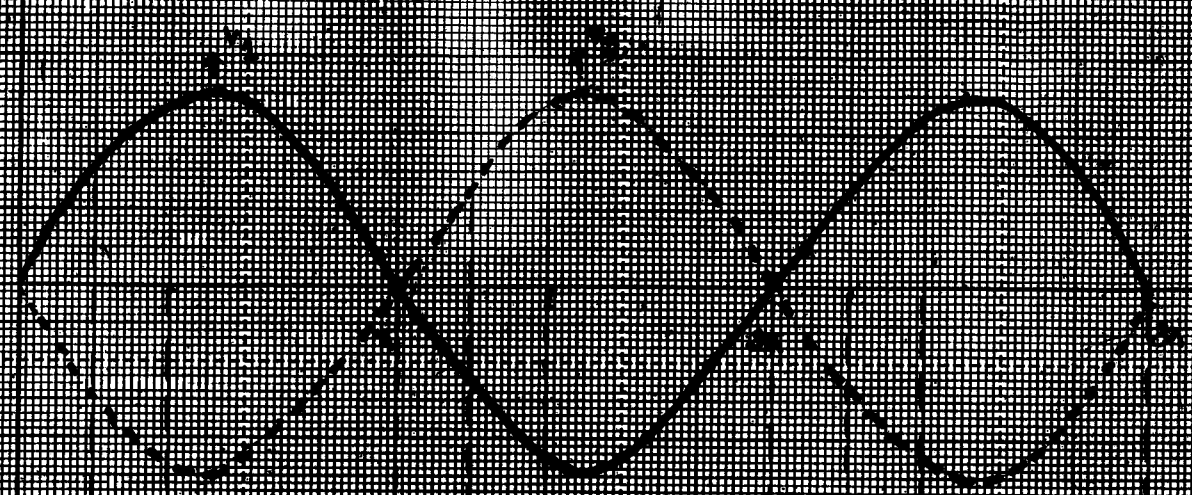\* At  $\omega t = \pi + \alpha + \mu$  current thro'  $T_1, T_2$  reduces to zero and turns OFF. and current thro'  $T_3, T_4$  reaches max value.



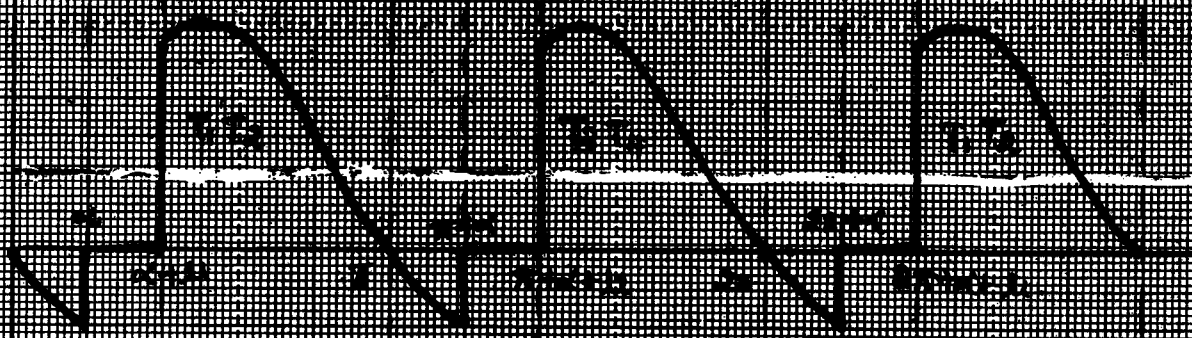$\sin(\omega t)$        $\sin(\omega t + \frac{\pi}{2})$        $\sin(\omega t - \frac{\pi}{2})$   
 $\cos(\omega t)$        $-\sin(\omega t)$        $\sin(\omega t)$



$\sin(\omega t)$        $\sin(\omega t + \frac{\pi}{2})$        $\sin(\omega t - \frac{\pi}{2})$   
 $\cos(\omega t)$        $-\sin(\omega t)$        $\sin(\omega t)$

$\sin(\omega t)$        $\sin(\omega t + \frac{\pi}{2})$        $\sin(\omega t - \frac{\pi}{2})$   
 $\cos(\omega t)$        $-\sin(\omega t)$        $\sin(\omega t)$

$\sin(\omega t)$        $\sin(\omega t + \frac{\pi}{2})$        $\sin(\omega t - \frac{\pi}{2})$   
 $\cos(\omega t)$        $-\sin(\omega t)$        $\sin(\omega t)$

From the equivalent circuit

$v_{ge}$  across  $ab = v_{ge}$  across  $ed$  ( $\because$  they are in parallel paths)

i.e., 
$$V_1 - L_s \frac{di_1}{dt} = V_2 - L_s \frac{di_2}{dt}$$

$$V_1 - V_2 = L_s \frac{di_1}{dt} - L_s \frac{di_2}{dt} = L_s \left[ \frac{di_1}{dt} - \frac{di_2}{dt} \right]$$

$V_1 = V_m \sin \omega t$  ;  $V_2 = -V_m \sin \omega t$  ;  $\therefore V_1 - V_2 = V_m \sin \omega t - (-V_m \sin \omega t)$

$$V_1 - V_2 = 2V_m \sin \omega t$$

$\therefore 2V_m \sin \omega t = L_s \left[ \frac{di_1}{dt} - \frac{di_2}{dt} \right]$  ;  $\frac{di_1}{dt} - \frac{di_2}{dt} = \frac{2V_m \sin \omega t}{L_s} \rightarrow \textcircled{1}$

we know that  $i_1 + i_2 = i_0$  [But  $i_0$  is constant]

$\therefore \frac{di_1}{dt} + \frac{di_2}{dt} = 0 \rightarrow \textcircled{2}$

On adding eqn  $\textcircled{1}$  and  $\textcircled{2}$

$$\frac{di_1}{dt} + \frac{di_2}{dt} + \frac{di_1}{dt} - \frac{di_2}{dt} = \frac{2V_m \sin \omega t}{L_s} ; \quad \frac{2di_1}{dt} = \frac{2V_m \sin \omega t}{L_s}$$

$\therefore \frac{di_1}{dt} = \frac{V_m \sin \omega t}{L_s}$

$$di_1 = \frac{V_m \sin \omega t}{L_s} dt$$

$\omega \cdot t_0 T$  ;  $i_1 = i_0$  at  $\omega t = \alpha + \pi$  ;  $i_2 = 0$  at  $\omega t = \alpha$   
(or)  $t = \frac{\alpha + \pi}{\omega}$  ;  $t = \frac{\alpha}{\omega}$

$\therefore \int_0^{i_0} di_1 = \int_{\frac{\alpha}{\omega}}^{\frac{\alpha + \pi}{\omega}} \frac{V_m \sin \omega t}{L_s} dt$  ;  $[i_1]_0^{i_0} = -\frac{V_m}{L_s} \left[ \frac{\cos \omega t}{\omega} \right]_{\frac{\alpha}{\omega}}^{\frac{\alpha + \pi}{\omega}}$

$\therefore i_0 = -\frac{V_m}{\omega L_s} \left[ \cos \omega t * \frac{\alpha + \pi}{\omega} - \cos \omega t * \frac{\alpha}{\omega} \right]$

$i_0 = \frac{V_m}{\omega L_s} \left[ \cos \alpha - \cos(\alpha + \pi) \right] \rightarrow \textcircled{3}$

$$v_o(\text{avg}) = \frac{1}{\pi} \int_{\alpha+\mu}^{\alpha+\pi} v_m \sin \omega t \cdot dt = -\frac{v_m}{\pi} [\cos \omega t]_{\alpha+\mu}^{\alpha+\pi}$$

$$= -\frac{v_m}{\pi} [\cos(\alpha+\pi) - \cos(\alpha+\mu)] = -\frac{v_m}{\pi} [-\cos \alpha - \cos(\alpha+\mu)]$$

$$v_o(\text{avg}) = \frac{v_m}{\pi} [\cos \alpha + \cos(\alpha+\mu)] \rightarrow \textcircled{4}$$

From eqn (3)

$$i_o = \frac{v_m}{\omega L_s} [\cos \alpha - \cos(\alpha+\mu)]$$

$$i_o \frac{\omega L_s}{v_m} = \cos \alpha - \cos(\alpha+\mu) \quad \text{(or)}$$

$$\cos(\alpha+\mu) = \cos \alpha - \frac{i_o \omega L_s}{v_m} \rightarrow \textcircled{5}$$

Substituting (5) in (4)

$$v_o(\text{avg}) = \frac{v_m}{\pi} [\cos \alpha + \cos \alpha - \frac{i_o \omega L_s}{v_m}]$$

$$v_o(\text{avg}) = \frac{2v_m}{\pi} \cos \alpha - \frac{i_o \omega L_s}{\pi} \rightarrow \textcircled{6}$$

From eqn (3)


$$i_o = \frac{v_m}{\omega L_s} [\cos \alpha - \cos(\alpha+\mu)] \quad \text{(or)} \quad \cos \alpha = \frac{i_o \omega L_s}{v_m} + \cos(\alpha+\mu) \rightarrow \textcircled{7}$$

Substituting (7) in (6)

$$v_o(\text{avg}) = \frac{v_m}{\pi} \left[ \frac{i_o \omega L_s}{v_m} + \cos(\alpha+\mu) + \cos(\alpha+\mu) \right]$$


$$v_o(\text{avg}) = \frac{i_o \omega L_s}{\pi} + \frac{2v_m}{\pi} \cos(\alpha+\mu) \rightarrow \textcircled{8}$$

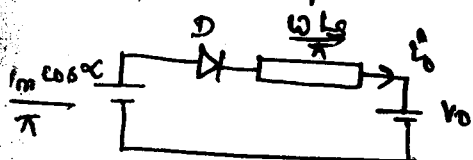From eqn (8) de equiv a ckt is drawn as follows.



1Ø FULL WAVE BRIDGE RECTIFIER WITH RL LOAD AND


FREE WHEELING DIODE

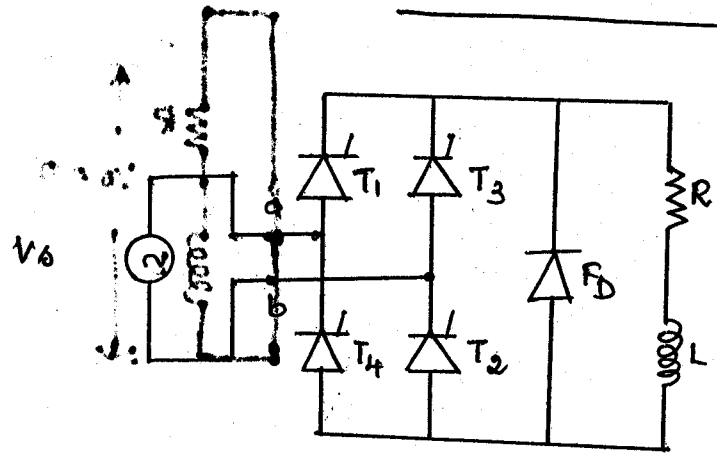

- \* Waveform of load current  $i_0$  is improved by connecting a free-wheeling diode (FD) across the load.
- \* FD prevents the reversal of load  $v_{ge}$ .

Advantages of  $F_D$  :-

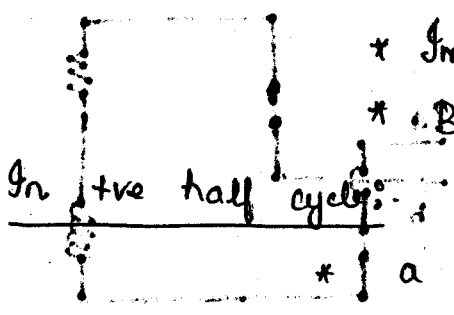- \* Improves input power factor angle.
- \* Improves load current waveform.
- \* Better load performance.



- \*  $a$  is +ve;  $b$  is -ve;  $V_{ab} = +V_m \sin \omega t$ ;  $V_{ba} = -V_m \sin \omega t$ .
- \*  $V_{ab}$  forward biases SCR  $T_1, T_2$ .
- \*  $V_{ba}$  reverse biases SCR  $T_3, T_4$ .
- \* Forward biased SCR  $T_1, T_2$  are turned ON at  $\omega t = \alpha$ .


From  $\omega t = 0$  to  $\alpha$  :-

- \* SCR  $T_1, T_2$  is FB
- \* SCR  $T_3, T_4$  is RB
- $V_{T1} = V_{T2} = V_{ab}$
- $V_{T3} = V_{T4} = V_{ba}$
- $i_0 = 0$
- $v_0 = 0$
- \*  $F_D$  is RB and does not conduct.
- $V_{FD} = V_0$

At  $\omega t = \alpha$ ; SCR  $T_1, T_2$  are turned ON

From  $\omega t = \alpha$  to  $\pi$

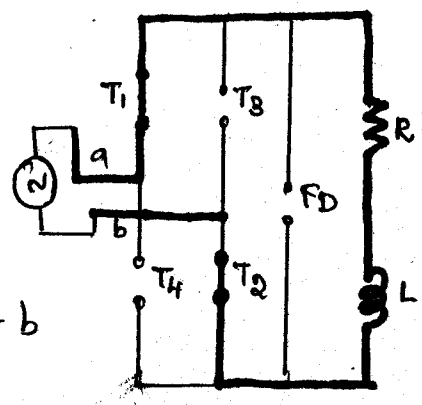- \*  $T_1, T_2$  are ON
- \*  $\therefore V_{T1} = V_{T2} = 0$
- \* Due to RL load  $i_0 \uparrow$  very slowly and reaches max value at  $\omega t = \pi$ ;  $i_0 = I_0$
- \*  $i_0$  flows thro'  $a - T_1 - R - L - T_2 - b$
- \*  $v_0 = V_0$
- \*  $V_{FD} = V_0$



At  $\omega t = \pi$  to  $\omega t = \pi + \alpha$ .

SCR  $T_1, T_2$  is RB

\*  $T_3, T_4$  are FB

\*  $F_D$  is forward biased and conducts.

\* So current  $i_0$  discharges thro'  $F_D$ .

\*  $\therefore F_D$  is connected in  $\parallel$  to load, when  $F_D$  conducts  $V_{ge}$  across  $F_D = 0$ ,

$\therefore V_{ge}$  across load  $V_0 = 0$

$i_0 = \downarrow$  thro'  $F_D$ .

$F_D$  conducts till the next SCR is turned ON.

At  $\omega t = \pi + \alpha$ :-

$F_D$  is RB and turns OFF

SCR  $T_3, T_4$  are turned ON

$\therefore V_{FD} = V_s$

$V_{T3} = V_{T4} = 0$

$i_0 \uparrow$  slowly and flows thro'  $b - T_3 - R - L - T_4 - a$ .  
From  $\omega t = \pi + \alpha$  to  $2\pi$ .

$T_3, T_4$  conducts

$\therefore V_{T3} = V_{T4} = 0$

due to RL load  $i_0 \uparrow$  slowly and reaches max at  $\omega t = 2\pi$

$\therefore i_0 = \uparrow$

$V_0 = V_s$

$F_D$  is reverse biased  $\therefore V_{FD} = V_s$ .

At  $\omega t = 2\pi$   $V_0 = 0$ ;  $T_3, T_4$  are RB;  $\therefore V_{T3} = V_{T4} = V_{ba}$ .


At  $\omega t = 2\pi$   $F_D$  is FB and conducts;  $\therefore V_{FD} = 0$

From  $\omega t = 2\pi$  to  $2\pi + \alpha$ .

Diode  $F_D$  conducts.

$i_0 \downarrow$  and reaches zero at  $2\pi + \alpha$ .


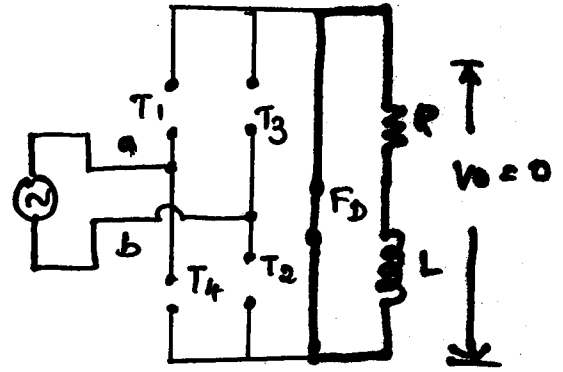
$F_D$  conducts till the next SCR turns ON.



$$V_{T1} = V_{T2} = V_{ab}$$

$$V_{T3} = V_{T4} = V_{ba}$$

$$V_{FD} = 0$$

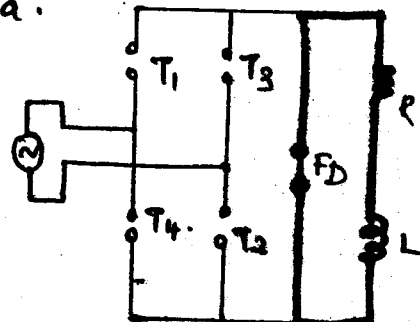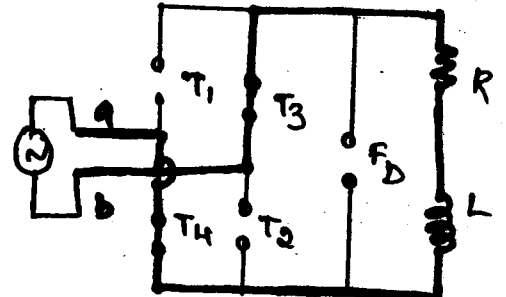



$$V_o(\text{avg}) = \frac{1}{\pi} \int_{\alpha}^{\pi} V_m \sin \omega t \cdot dt$$

$$\therefore V_o(\text{avg}) = \frac{V_m}{\pi} [1 + \cos \alpha]$$


$$I_o(\text{avg}) = \frac{V_m}{R} [1 + \cos \alpha]$$

$$V_{\text{orms}} = \sqrt{\frac{1}{\pi} \int_{\alpha}^{\pi} V_m^2 \sin^2 \omega t \cdot dt}$$



$$V_{\text{orms}} = \frac{V_m}{\sqrt{2\pi}} \int_{\alpha}^{\pi} (\pi - \alpha) + \frac{1}{2} \sin 2\alpha$$

$$I_{\text{orms}} = \frac{V_m}{R \sqrt{2\pi}} \int_{\alpha}^{\pi} \pi - \alpha + \frac{1}{2} \sin 2\alpha$$
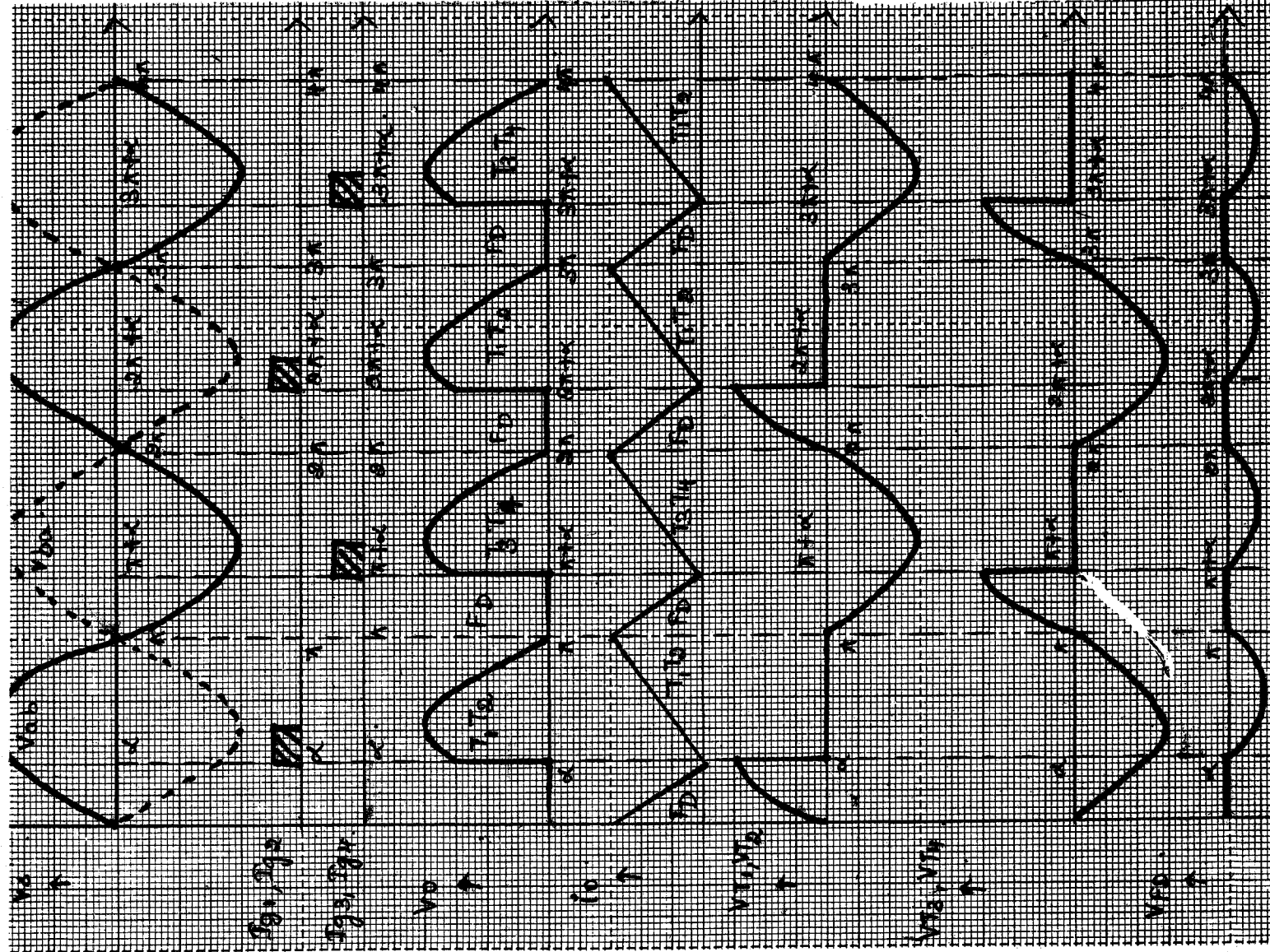
$$P = V_{\text{orms}} * I_{\text{orms}}$$


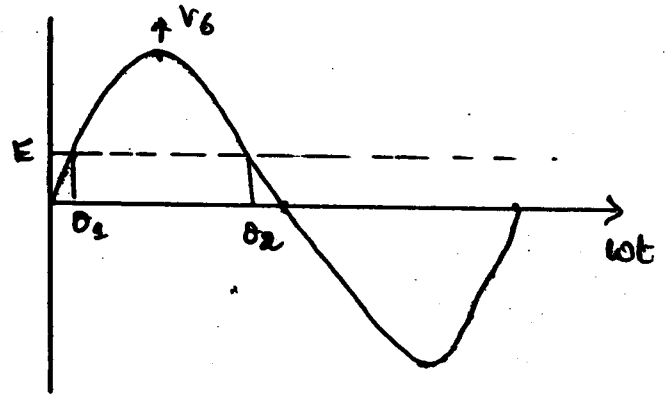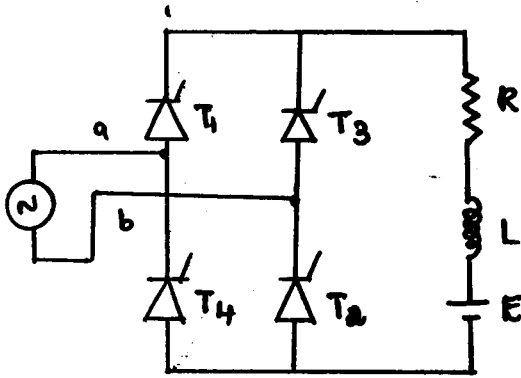
# 1 $\phi$ FULL WAVE CONVERTER WITH RLE LOADS:



- \* It is an RLE load, where E is load circuit emf.
- \* E may be due to battery in load (or) may be generated emf of a dc motor.
- \* Till  $\omega t = \theta_1$ ;  $V_b$  is  $< E$  so SCR will be Reverse biased and cannot be turned ON.
- \* SCR can be triggered only after  $\theta_1$ .

During +ve half cycle:-

At  $\omega t = \alpha$ , SCR  $T_1, T_3$  conduct

From  $\omega t = 0$  to  $\alpha$

SCR  $T_1, T_3$  is FB

From  $\omega t = \alpha$  to  $\pi$

$T_1, T_3$  conducts

$$V_{T_1} = V_{T_3} = 0$$

$$i_o = \uparrow$$

$$V_o = V_b$$

At  $\omega t = \pi$

$$T_1, T_3 = RB$$

$$i_o = \downarrow$$

$$V_o = V_b$$

At  $\omega t = \pi + \alpha$

$$i_o = 0$$

$$V_o = 0$$

$$T_1, T_3 = OFF$$


From  $\omega t = \pi + \alpha$  to  $2\pi$

$T_2, T_4$  = conducts

$$V_{T_2} = V_{T_4} = 0$$

$$i_o = \uparrow$$

$$V_o = V_b$$

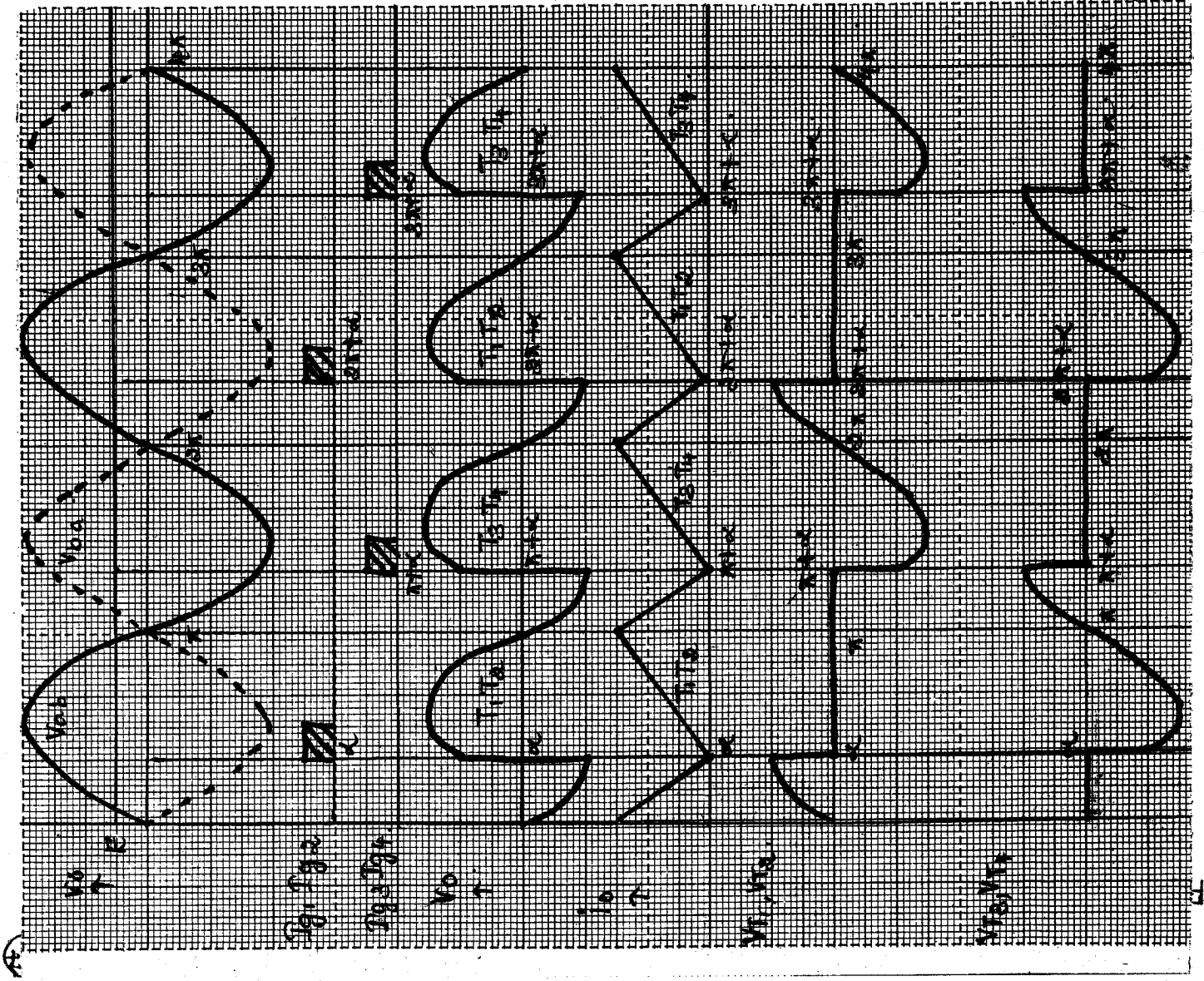

$$V_0 (\text{avg}) = \frac{1}{\pi} \int_0^{\pi} v_m \sin \omega t \cdot d\omega t$$

$$V_0 (\text{avg}) = \frac{2 v_m \cos \alpha}{\pi}$$

$$V_0 (\text{rms}) = \sqrt{\frac{1}{\pi} \int_0^{\pi} v_m^2 \sin^2 \omega t \cdot d\omega t}$$

$$V_{0 \text{ rms}} = \frac{v_m}{\sqrt{2\pi}} \sqrt{\pi - \frac{1}{2} [\sin 2(\pi t) - \sin 2\alpha]}$$

$$P = V_{0 \text{ rms}} \times I_{0 \text{ rms}}$$

# 1 $\phi$ FULL WAVE HALF CONTROLLED BRIDGE RECTIFIER [OR]

## SEMICONVERTER.



\* Semiconductor is a combination of diodes and SCRs.

### 1 $\phi$ SEMICONVERTER WITH R LOAD:-

\* Semiconductor is connected in two configurations

a) Symmetrical configuration

b) Asymmetrical configuration.

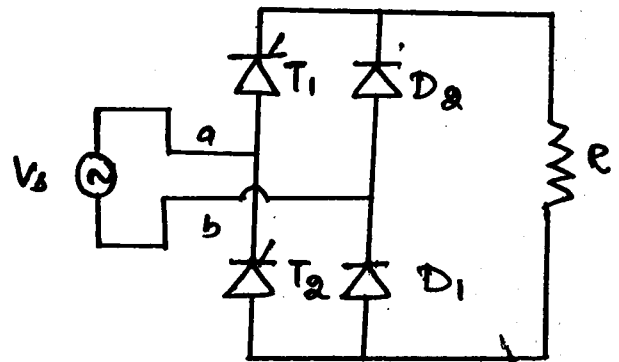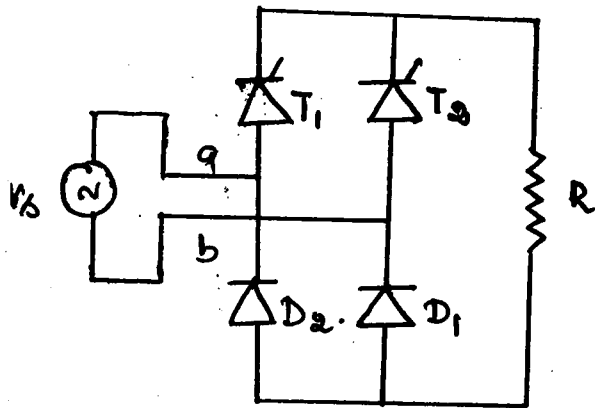

### Symmetrical configuration:-

\* In this configuration, cathodes of two SCRs are at same potential.

\* So their gates can be connected together and a single gate pulse can be used to trigger both the SCRs.

\* which ever SCR is forward biased will turn ON.

### Asymmetrical configuration:-

In this configuration separate triggering circuits

are used.

Here only waveforms for symmetrical configuration is explained. (71)

Positive half cycle:-

- \* Terminal a is +ve, b is -ve
- $V_{ab} = V_m \sin \omega t$ ,  $V_b = -V_m \sin \omega t$ .
- $V_{ab}$  supplies SCR  $T_1$  and diode  $D_1$ .
- \*  $T_1$  and  $D_1$  are forward biased.
- \* At  $\omega t = \alpha$  SCR  $T_1$  is turned ON.
- \*  $i_o$  flows thro'  $a - T_1 - R - D_1 - b$

From  $\omega t = 0$  to  $\alpha$ .

$T_1$  and  $D_1$  are forward biased

$$\therefore V_{T_1} = V_{ab}$$

$$V_{D_1} = 0$$

$$i_o = 0$$

$$V_o = 0$$

From  $\omega t = \alpha$  to  $\pi$

$T_1$  is turned ON at  $\omega t = \alpha$

$$\therefore V_{T_1} = 0$$

$$V_{D_1} = 0$$

$i_o = \uparrow$  and reaches zero at  $\omega t = \pi$

$V_o = V_s$  and reaches zero at  $\omega t = \pi$

At  $\omega t = \pi$ ;  $i_o = V_o = 0$

At  $\omega t = \pi$ ; supply  $v_{ge}$  reaches zero and so  $T_1$  and  $D_1$  and RB and is turned OFF.

From  $\omega t = \pi$  to  $\pi + \alpha$


at  $\omega t = \pi$ ;  $T_2$  and  $D_2$  are forward biased

$$\therefore V_{T_2} = V_{ba}$$

$$V_{D_2} = 0$$

$$i_o = 0$$

$$V_o = 0$$

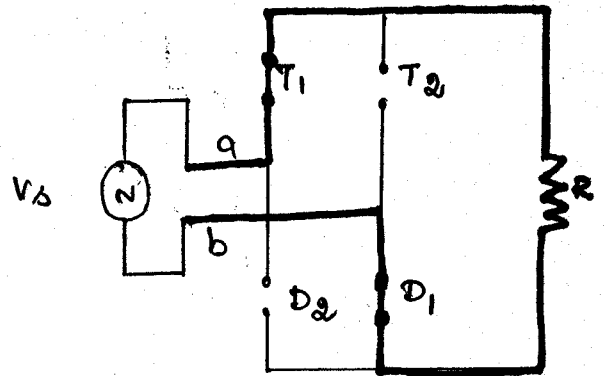

From  $\omega t = \pi + \alpha$  to  $2\pi$ .

\* At  $\omega t = \pi + \alpha$ ; SCR  $T_2$  is ON


\*  $D_2$  is already ON

$$V_{T_2} = 0$$

$$V_{D_2} = 0$$

$$i_o = I_{avg}$$

$$V_o = V_s$$

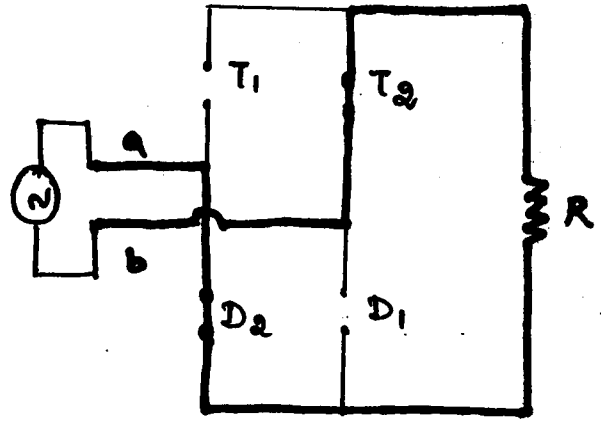

\* At  $\omega t = 2\pi$ ;  $i_o = 0$ ;  $V_o = 0$

also at  $\omega t = 2\pi$  SCR  $T_2$  and diode  $D_2$  is RB and is turned OFF.

$$\therefore V_o(\text{avg}) = \frac{1}{\pi} \int_{\alpha}^{\pi} V_m \sin \omega t \cdot d\omega t$$

$$V_o(\text{avg}) = \frac{V_m}{\pi} [1 + \cos \alpha]$$


$$V_o(\text{rms}) = \sqrt{\frac{1}{\pi} \int_{\alpha}^{\pi} V_m^2 \sin^2 \omega t \cdot d\omega t}$$

$$V_{o\text{rms}} = \frac{V_m}{\sqrt{2\pi}} \sqrt{\pi - \alpha + \frac{1}{2} \sin 2\alpha}$$

$$I_o(\text{avg}) = \frac{V_o(\text{avg})}{R} = \frac{V_m}{\pi R} [1 + \cos \alpha]$$

$$I_{o\text{rms}} = \frac{V_m}{R\sqrt{2\pi}} \sqrt{\pi - \alpha + \frac{1}{2} \sin 2\alpha}$$

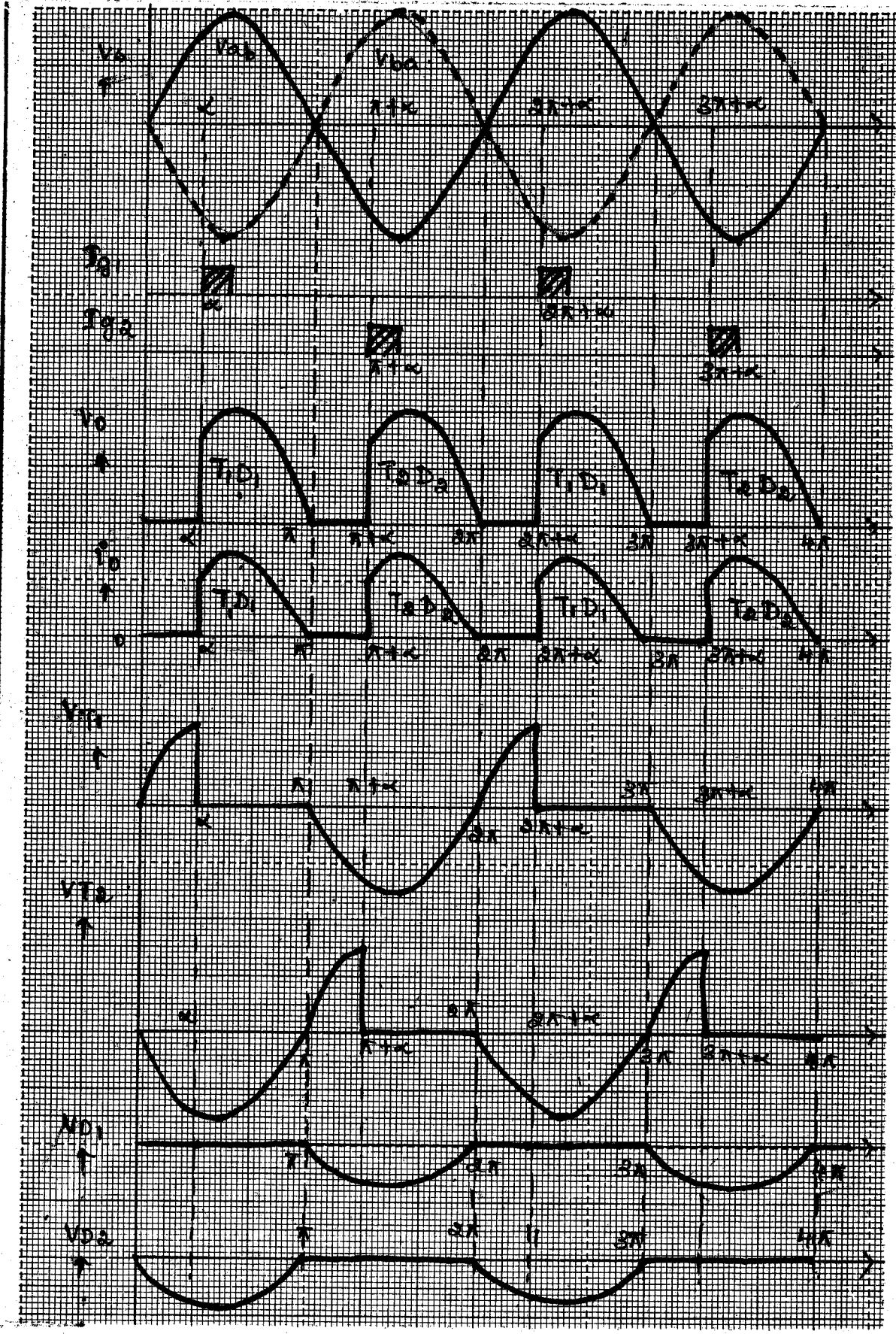
$$P = V_{o\text{rms}} * I_{o\text{rms}}$$



2002-10-10  
 2002-10-10

# 1Ø SEMI CONVERTER WITH RL LOAD:-

## SYMMETRICAL CONFIGURATION:-

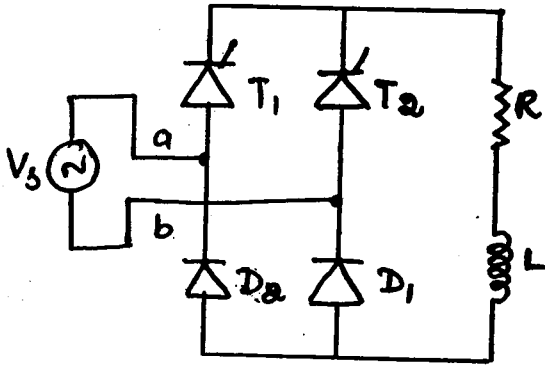

In the +ve half cycle:-

- \* a is +ve; b is -ve.
- \* SCR  $T_1$  and diode  $D_1$  is FB
- \* At  $\omega t = \alpha$ ; SCR  $T_1$  is turned ON.

From  $\omega t = 0$  to  $\alpha$ :-

SCR  $T_1$  and diode  $D_1$  are FB.

$$\therefore V_{T_1} = V_{ab}; V_{D_1} = 0$$

$$i_0 = 0; V_0 = 0$$

From  $\omega t = \alpha$  to  $\pi$ :-

At  $\omega t = \alpha$ ; SCR  $T_1$  is ON


$$\therefore V_{T_1} = 0$$

$$V_{D_1} = 0$$

$i_0 = I_{ing}$  slowly due to RL load.

$$V_0 = V_s$$

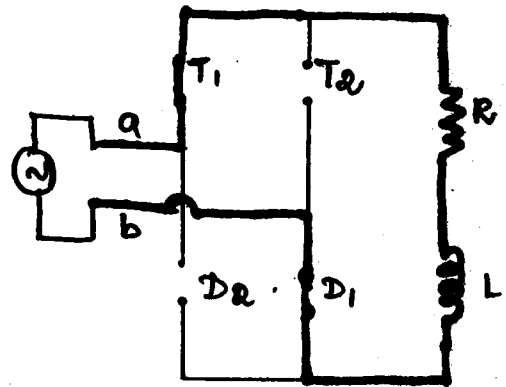At  $\omega t = \pi$ ; SCR  $T_1$  and  $D_1$  are reverse biased.



At  $\omega t = \pi$  to  $\pi + \alpha$

Though at  $\omega t = \pi$ ; SCR  $T_1$  is RB it is not turned OFF  $\because$   $i_0$  is higher than holding current.


But at  $\omega t = \pi$ ;  $D_1$  is RB and turns OFF

But at  $\omega t = \pi$ ; SCR  $T_2$  and Diode  $D_2$  is ON

$\therefore$  From  $\omega t = \pi$  to  $\pi + \alpha$   $T_2$  and  $D_2$  conducts.  $\therefore V_0 = 0$

At  $\pi + \alpha$   $i_0 = 0$  and SCR  $T_1$  is OFF.  $\therefore$  the load is shorted

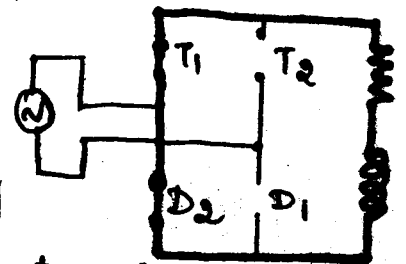Also at  $\pi + \alpha$  SCR  $T_2$  is turned ON.






At  $\omega t = \pi + \alpha$ ; SCR  $T_2$  is ON

$D_2$  is FB and is already ON

From  $\omega t = \pi + \alpha$  to  $2\pi$

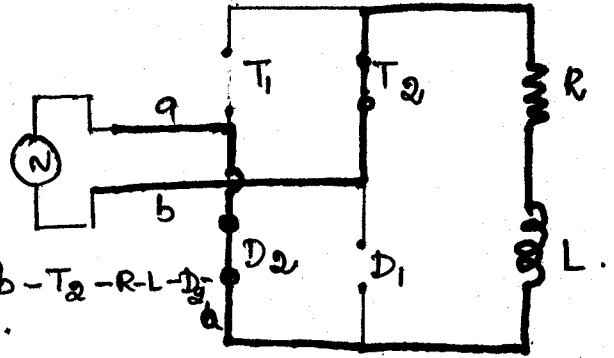- \*  $T_2$  and  $D_2$  conduct;
- \*  $V_{T_2} = 0$ ;  $V_{D_2} = 0$ ;  $i_o$  flows thro'  $b-T_2-R-L-a$
- \*  $i_o =$  slowly  $\uparrow$  due to RL load.
- \*  $i_o =$  max at  $\omega t = 2\pi$ .



At  $\omega t = 2\pi$ ; SCR  $T_2$  is RB but does not turn OFF because.

$i_o$  is higher than holding current.


But diode  $D_1$  and SCR  $T_1$  is FB at  $\omega t = 2\pi$ .

From  $\omega t = 2\pi$  to  $2\pi + \alpha$ .

$i_o \downarrow$  slowly and reaches to zero at  $2\pi + \alpha$ .

$\therefore T_2$  and  $D_1$  conduct from  $\omega t = 2\pi$  to  $2\pi + \alpha$ .

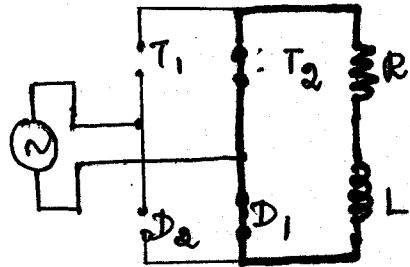$\therefore V_{T_2} = V_{D_1} = 0 \therefore V_o = 0$



At  $\omega t = 2\pi + \alpha$   $i_o$  reaches zero and so SCR  $T_2$  is turned OFF.

At  $\omega t = 2\pi + \alpha$  SCR  $T_1$  is turned ON.


\* already diode  $D_1$  is ON

$\therefore T_1$  and  $D_1$  conducts

From  $\omega t = 2\pi + \alpha$  to  $3\pi$

$T_1$  and  $D_1$  conducts

$V_{T_1} = 0$ ;  $V_{D_1} = 0$ .

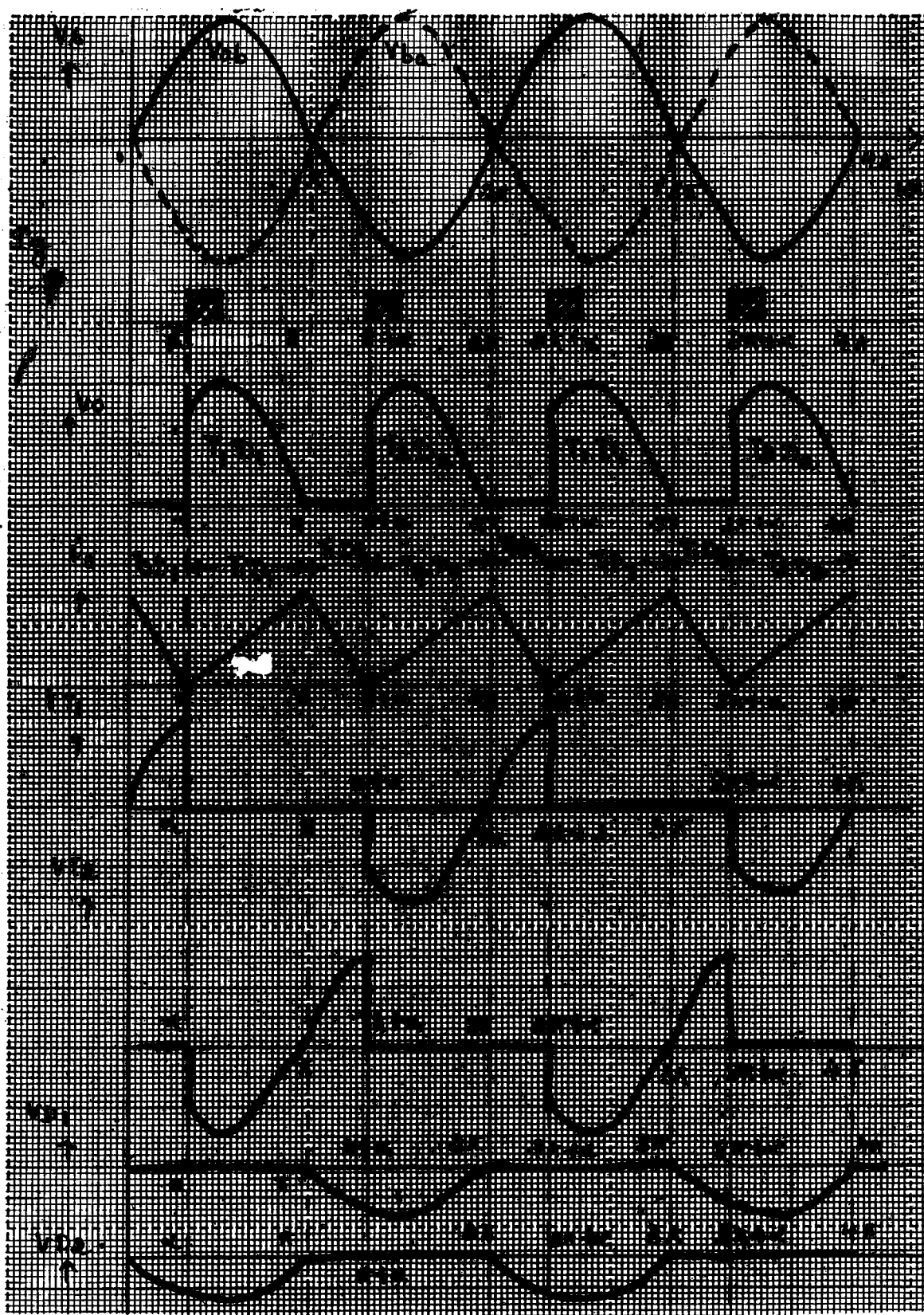


$$V_0(\text{avg}) = \frac{1}{\pi} \int_{\alpha}^{\pi} V_m \sin \omega t \cdot d\omega t = \frac{V_m}{\pi} [1 + \cos \alpha] \quad [\text{already solved}]$$

$$V_0(\text{rms}) = \sqrt{\frac{1}{\pi} \int_{\alpha}^{\pi} V_m^2 \sin^2 \omega t \cdot d\omega t} = \frac{V_m}{\sqrt{2\pi}} \sqrt{\pi - \alpha + \frac{1}{2} \sin 2\alpha}$$

# 1 $\phi$ SEMICONVERTER WITH RL LOAD:-

## ASYMMETRICAL CONFIGURATION:-

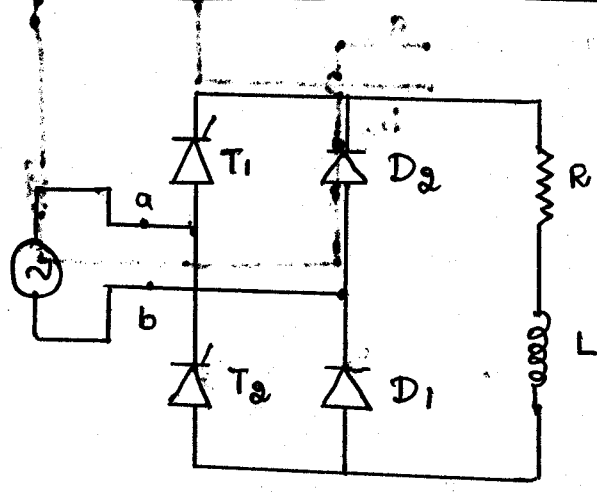

In the +ve half cycle

- \* a is +ve, b is -ve.
- \* SCR T<sub>1</sub> and diode D<sub>1</sub> is FB
- \* At  $\omega t = \alpha$ , SCR T<sub>1</sub> is turned ON.

From  $\omega t = 0$  to  $\alpha$ :-

\* SCR T<sub>1</sub> and D<sub>1</sub> are FB

$\therefore V_{T1} = V_{ab}; V_{D1} = 0$

$i_o = 0; V_o = 0$

From  $\omega t = \alpha$  to  $\pi$ :-

\* At  $\omega t = \alpha$ , SCR T<sub>1</sub> is ON

$\therefore V_{T1} = 0; V_{D1} = 0$

$i_o = \uparrow$  slowly due to RL load.

$\therefore$  T<sub>1</sub> and D<sub>1</sub> conducts  $i_o$  flows thro' a - T<sub>1</sub> - R - L - D<sub>1</sub> - b.

$V_o = V_s$

At  $\omega t = \pi$

\* SCR T<sub>1</sub> is RB and turns OFF

\* SCR T<sub>2</sub> is FB

$\therefore V_{T1} = V_{ab}; V_{T2} = V_{ba}$

\*  $i_o$  is max at  $\omega t = \pi$



From  $\omega t = \pi$  to  $\pi + \alpha$

\* Diode D<sub>1</sub> and D<sub>2</sub> conducts.

\* So  $i_o$  freewheels thro' D<sub>1</sub>, D<sub>2</sub>.

\*  $i_o \downarrow$  and reaches zero at  $\omega t = \pi + \alpha$ .

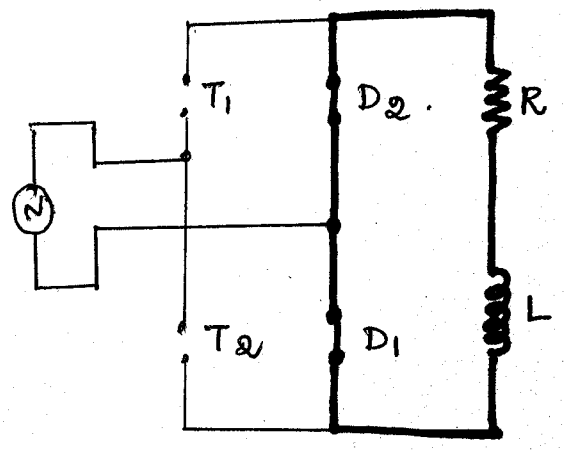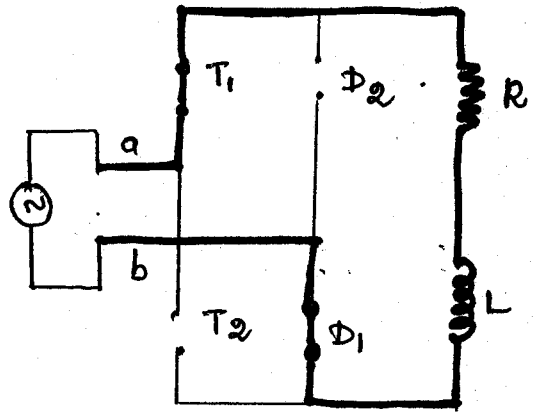$\therefore$  from  $\pi$  to  $\pi + \alpha$ ;  $V_o = 0$   $\therefore$  load is shorted.



At  $\omega t = \pi + \alpha$ ; SCR  $T_2$  is ON.

From  $\omega t = \pi + \alpha$  to  $2\pi$   
Diode  $D_2$  is FB

$V_{T_2} = 0$


$V_{D_2} = 0$

$\therefore T_2$  and  $D_2$  conducts.

$V_o = V_s$

$i_o = I^s$  slowly due to RL load.

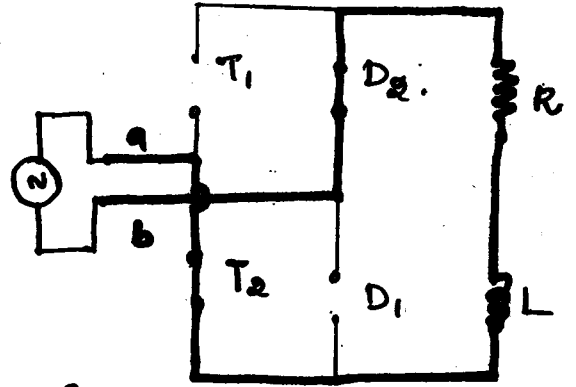$i_o$  flows thro'  $b - D_2 - R - L - T_2 - a$ .



At  $\omega t = 2\pi$

SCR  $T_2$  is RB and turns OFF


$\therefore V_{T_2} = V_{ba}$

From  $\omega t = 2\pi$  to  $2\pi + \alpha$

\* Diode  $D_1$  and  $D_2$  conducts


$i_o$  thro' diode  $D_1, D_2$  and reaches zero


$V_{D_1} = V_{D_2} = 0$

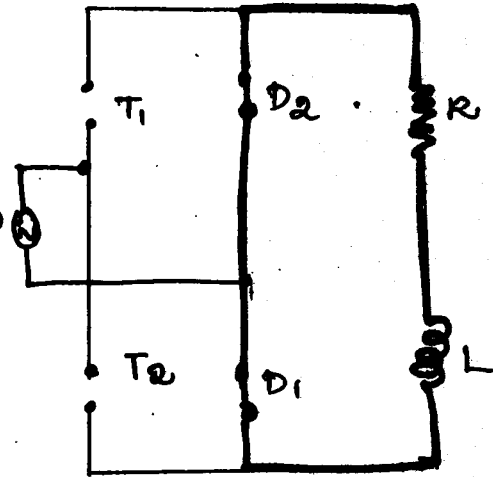

At  $\omega t = 2\pi + \alpha$

Again  $T_1$  &  $D_1$  will conduct.

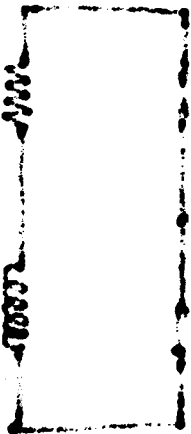


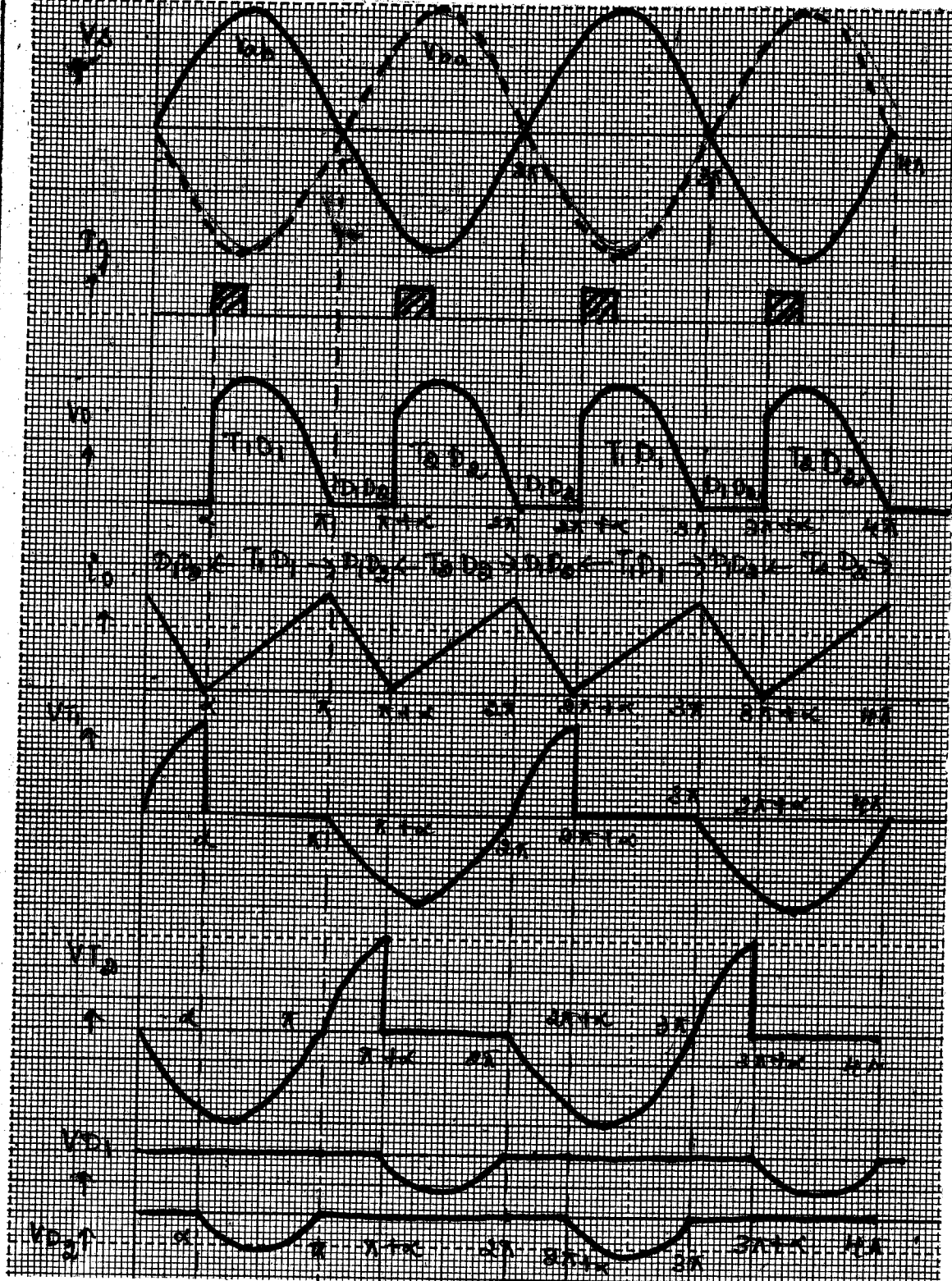

$$V_o(\text{avg}) = \frac{1}{\pi} \int_{\alpha}^{\pi} V_m \sin \omega t \cdot d\omega t = \frac{V_m}{\pi} [1 + \cos \alpha]$$

$$V_o(\text{rms}) = \sqrt{\frac{1}{\pi} \int_{\alpha}^{\pi} V_m^2 \sin^2 \omega t \cdot d\omega t} = \frac{V_m}{\sqrt{2\pi}} \sqrt{\pi - \alpha + \frac{1}{2} \sin 2\alpha}$$
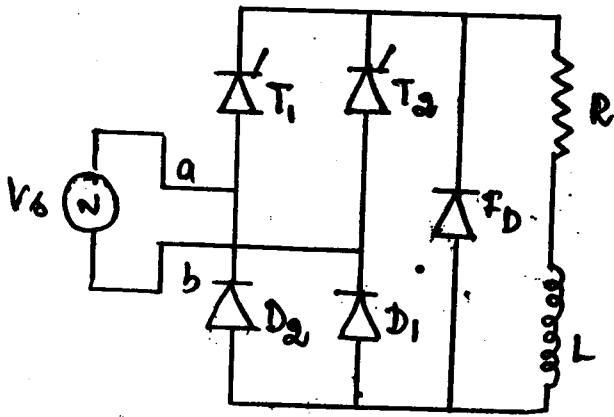
# 1 $\phi$ SEMICONVERTER WITH RL LOAD AND FREEMHEELING DIODE



In +ve half cycle

From  $\omega t = 0$  to  $\alpha$ .

\*  $T_1$  and  $D_1$  is FB

[Give explanation as in previous cases]

At  $\omega t = \alpha$ :-


\*  $T_2$  is turned ON.

From  $\omega t = \alpha$  to  $\pi$ :-

\*  $T_1$  and  $D_1$  conducts.

\*  $i_o \uparrow$  due to RL load.

\*  $V_o = V_s$

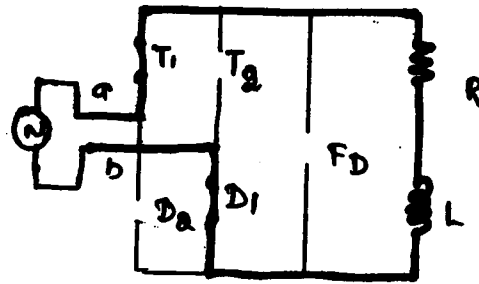


From  $\pi$  to  $\pi + \alpha$ :-

$F_D$  conducts.

$i_o = 0$  at  $\pi + \alpha$ .

$V_o = 0$ .

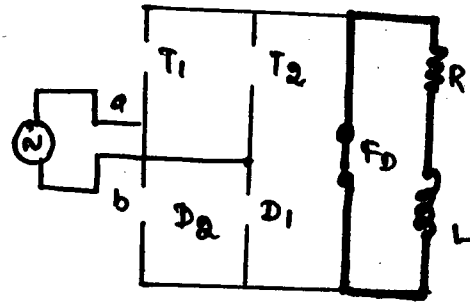


From  $\omega t = \pi + \alpha$  to  $2\pi$

$T_2, D_2$  conducts.

$i_o = \uparrow$  due to RL load.

$V_o = V_s$ .

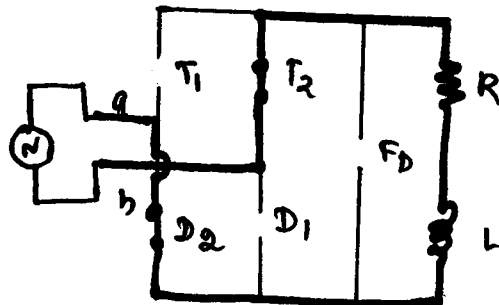



From  $\omega t = 2\pi$  to  $2\pi + \alpha$

$F_D$  conducts

$i_o \downarrow$  to zero

$V_o = 0$ .

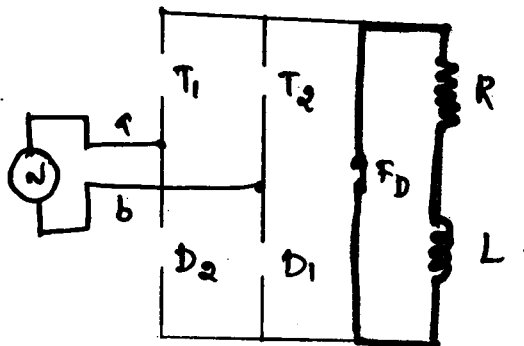


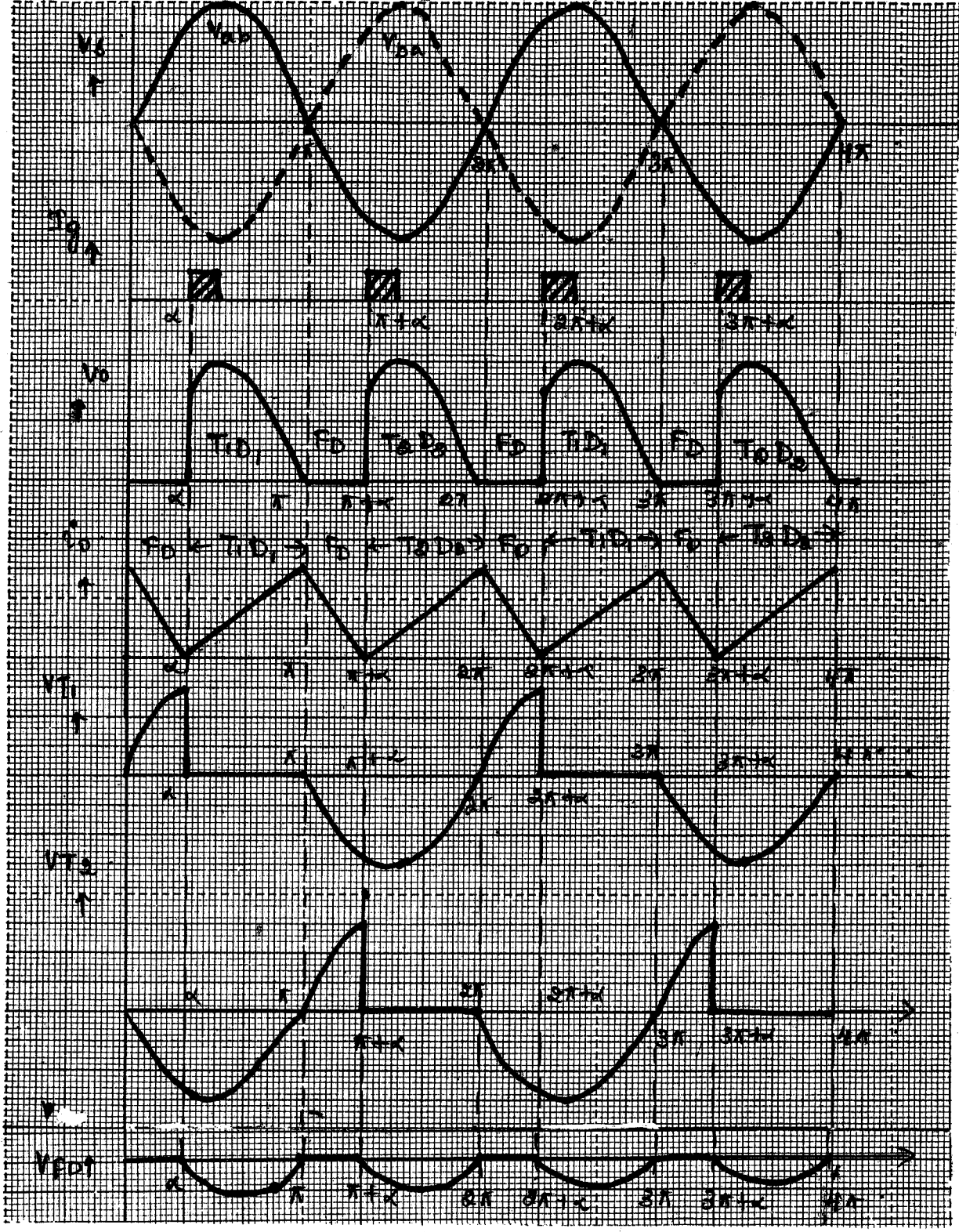

$$V_o(\text{avg}) = \frac{1}{\pi} \int_{\alpha}^{\pi} V_m \sin \omega t \cdot d\omega t = \frac{V_m}{\pi} [1 + \cos \alpha]$$

$$V_o(\text{rms}) = \sqrt{\frac{1}{\pi} \int_{\alpha}^{\pi} V_m^2 \sin^2 \omega t \cdot d\omega t} = \frac{V_m}{\sqrt{2\pi}} \sqrt{\pi - \alpha + \frac{1}{2} \sin 2\alpha}$$

# 1 $\phi$ SEMICONVERTER WITH RL LOAD!

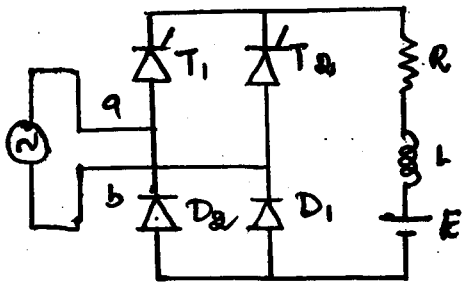

when no device is conducting  $V_o = E$   
In +ve half cycle:-

From 0 to  $\alpha$ .

$T_1, D_1$  is FB  
 But  $T_1$  is NOT ON  
 So  $V_o = E$

From  $\omega t = \alpha$  to  $\pi$

$T_1$  is ON at  $\alpha$   
 $V_o = V_s$  slowly  
 $i_o = I_a$  due to RL load.

at  $\omega t = \pi$

$T_1$  is RB and OFF

$V_o = E$   
 $i_o = \downarrow$


From  $\omega t = \pi$  to  $\pi + \alpha$

$T_1$  OFF,  $D_1$  OFF  
 $T_2, D_2 = FB$   
 $V_o = E$   
 $i_o = \downarrow$  to zero.

From  $\omega t = \pi + \alpha$  to  $2\pi$

$T_2, D_2 = ON$   
 $V_o = V_s$  slowly  
 $i_o = I_a$  due to RL load
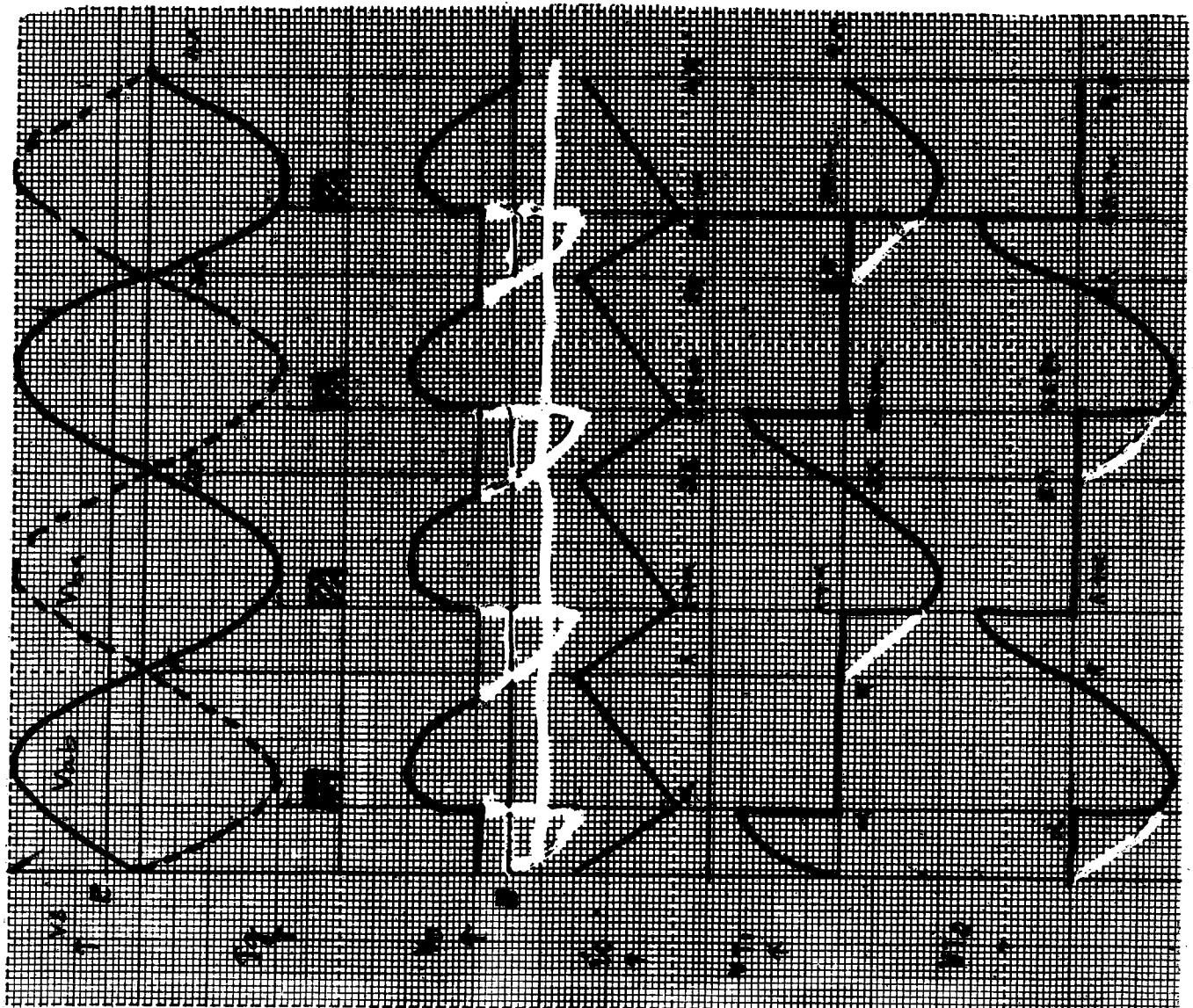
$$V_o = \frac{1}{\pi} \int_{\alpha}^{\pi + \alpha} V_m \sin \omega t \, d\omega t = \frac{2V_m \cos \alpha}{\pi}$$





# THREE PHASE CONVERTER:-



The advantages of three phase converter over single phase converter is

- \* average output voltage is high.
- \* Distortion is low.
- \* Amplitude of ripple is reduced.

## Types of three phase converter:-

- \* Three phase half wave converter.
- \* Three phase full wave converter.
  - 3 $\phi$  semi converter [half controlled]
  - 3 $\phi$  full converter [full controlled]
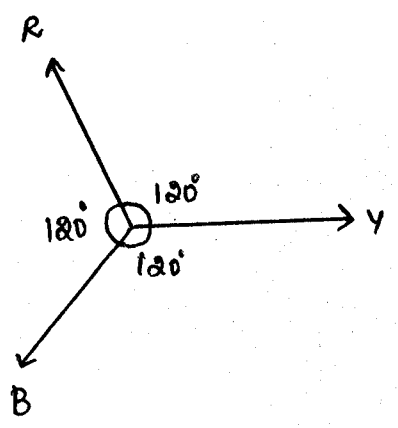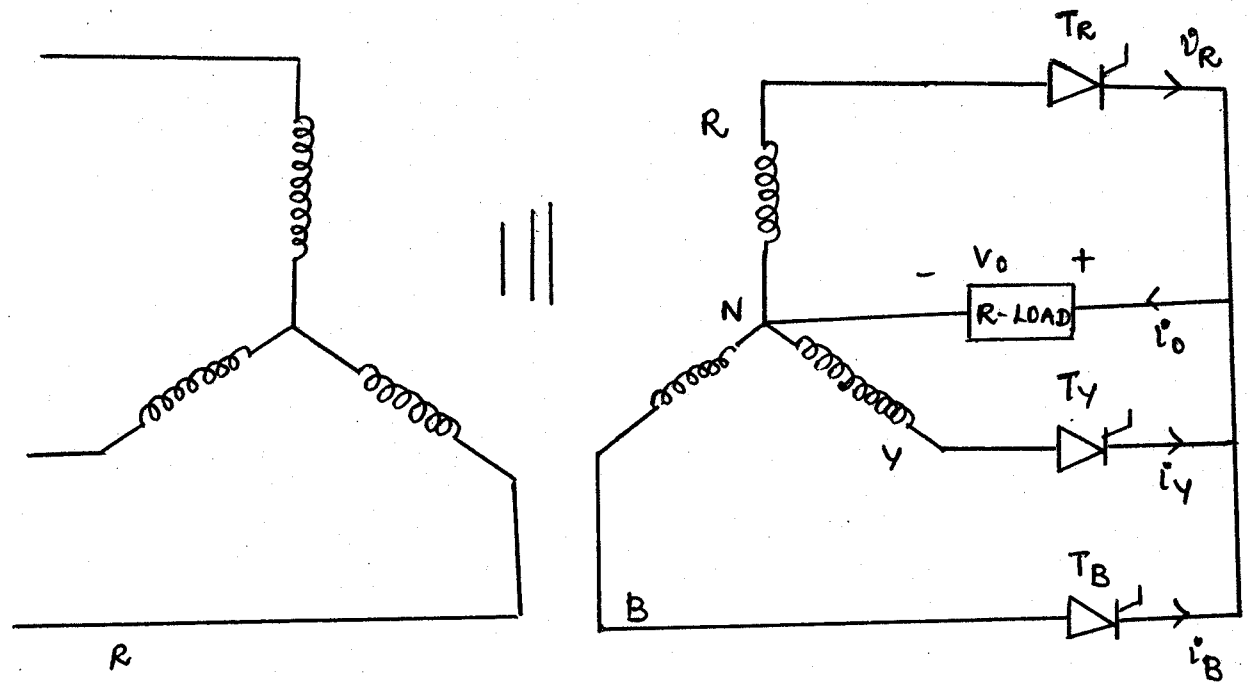
## THREE PHASE HALF WAVE CONVERTER WITH R LOAD:-



- \* SCRs TR, TY, TB are connected to the supply R, Y and B
- \* The phase sequence is RYB.

\* All the three phases are displaced from each other by an angle of  $120^\circ$ .

\* R-phase is taken as reference.

\* Y phase lags R by an angle of  $120^\circ$

\* B phase lags R by an angle of  $240^\circ$ .

\* Among the three phases, the SCR connected to the phase with highest positive voltage can be triggered

\* No SCR can be triggered below a phase angle of  $30^\circ$ .

\* i.e., If R phase is more positive,  $T_R$  can be turned ON.

\* If Y phase is more positive,  $T_Y$  can be ON.

\* If B phase is more +ve,  $T_B$  can be ON.

\* Every SCR will conduct for a maximum of  $120^\circ$  after it has been turned ON.

\* At  $\omega t = 30^\circ$ ;  $V_{RN}$  is more positive than  $V_{BN}, V_{CN}$ .

$\therefore$  SCR connected to R phase i.e.  $T_R$  can be triggered, because it is forward biased.

\*  $T_R$  cannot be turned ON before  $\omega t = 30^\circ$

because it is reverse biased by the already conducting SCRs.

NOTE:-

$\therefore \omega t = 30$  corresponds to  $\alpha = 0$ ;

(or)  $\boxed{\omega t = \alpha + 30^\circ}$  (or)  $\boxed{\alpha = \omega t - 30^\circ}$ .

$\therefore$  If we say  $\alpha = 0$ , it means  $\omega t = 30^\circ$ .

∴ If an SCR is triggered at  $\alpha=0$  ( $\omega t=30$ ) it will conduct for  $120^\circ$  i.e.  $\alpha=0+120=120^\circ$  ( $\omega t=\alpha+30=120+30=150^\circ$ ).

\* Similarly the next SCR will be triggered  $120^\circ$  after the first SCR is triggered.

\* i.e. if SCR  $T_R$  is triggered at  $\alpha=30^\circ$  ( $\omega t=60$ )

then  $T_Y$  will be triggered at  $\alpha=150^\circ$  ( $\omega t=180$ ) and so on.

\*  $T_B$  will be triggered at  $\alpha=270^\circ$  ( $\omega t=300$ ).

Max value of  $\alpha$  is  $180^\circ$ . SCR

Modes:-

- When  $\alpha \leq 30^\circ \rightarrow$  conduction mode.
- When  $\alpha > 30^\circ$  and  $< 150^\circ \rightarrow$  discontinuous mode.
- When  $\alpha \geq 150^\circ \rightarrow$  no conduction mode.

or  $\alpha=0^\circ$  [i.e.  $\omega t=30^\circ$ ]

$T_R$  is turned ON at  $\omega t=30^\circ$

$T_Y$  is turned ON at  $\omega t=150^\circ$

$T_B$  is turned ON at  $\omega t=270^\circ$

Duration	More Positive	Forward bias	Fired SCR	O/P v <sub>ge</sub> .
$\omega t = 30^\circ$ to $150^\circ$	R phase is more +ve	$T_R$ is FB	$T_R$ is ON	$V_o = V_{RN}$
$\omega t = 150^\circ$ to $270^\circ$	Y phase is more +ve	$T_Y$ is FB	$T_Y$ is ON	$V_o = V_{YN}$
$\omega t = 270^\circ$ to $390^\circ$	B is +ve	$T_B$ is FB	$T_B$ is ON	$V_o = V_{BN}$

For  $\alpha = 30^\circ$ ;  $\omega t = 60^\circ$

$\therefore T_R$  is ON at  $\omega t = 60^\circ$ ;  $T_Y$  is ON at  $\omega t = 180^\circ$ ;  $T_B$  is ON at  $\omega t = 300^\circ$ .


Duration	More Positive Phase.	Forward bias	conducting SCR	O/P $V_{ge}$ .
$t = 60$ to $180^\circ$	R is more +ve	$T_R$	$T_R$	$V_0 = V_{RN}$
$t = 180$ to $300$	Y is more +ve	$T_Y$	$T_Y$	$V_0 = V_{YN}$
$t = 300$ to $420$	B is more +ve	$T_B$	$T_B$	$V_0 = V_{BN}$

For  $\alpha = 60^\circ$ ,  $\omega t = 90^\circ$

$T_R$  is ON at  $\omega t = 90^\circ$ ;  $T_Y$  is ON at  $\omega t = 210^\circ$ ;  $T_B$  is ON at  $\omega t = 330^\circ$

Duration ( $\omega t = 90$ to $210$ )	More Positive Phase	Forward bias	conducting SCR	O/P $V_{ge}$ .
$t = 90$ to $180$	R is +ve	$T_R$	$T_R$	$V_0 = V_{RN}$
from $t = 180$ to $210$	Y is +ve	$T_Y$	No conduction $\because T_Y$ is ON only at $\omega t = 210$	$V_0 = 0$
$t = 210$ to $330$	Y is +ve B is +ve	$T_Y$ $T_B$	$T_Y$ No conduction $\because T_B$ is ON only at $\omega t = 330$	$V_0 = V_{YN}$ $V_0 = 0$
$t = 330$ to $450$	B is +ve R is +ve	$T_B$ $T_R$	$T_B$ No conduction	$V_0 = V_{BN}$ $V_0 = 0$

+

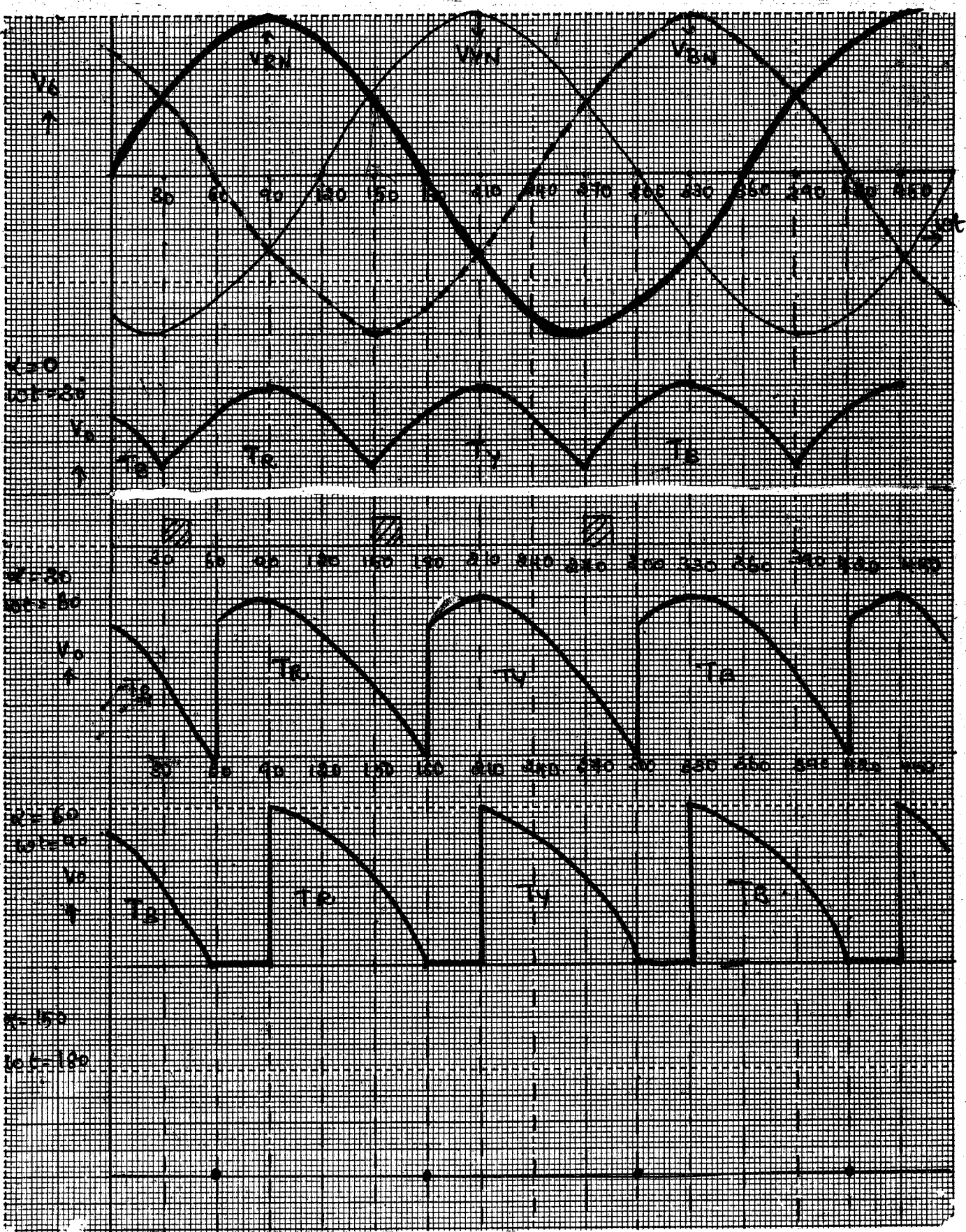

$$V_0(\text{avg}) = \frac{1}{2\pi/3} \int_{\frac{\pi}{6} + \alpha}^{\frac{5\pi}{6} + \alpha} V_m \sin \omega t \cdot d\omega t = \frac{3V_m}{2\pi} \left[ -\cos \omega t \right]_{\frac{\pi}{6} + \alpha}^{\frac{5\pi}{6} + \alpha}$$

$$= -\frac{3V_m}{2\pi} \left[ \cos \left( \frac{5\pi}{6} + \alpha \right) - \cos \left( \frac{\pi}{6} + \alpha \right) \right]$$

$$V_0(\text{avg}) = -\frac{3V_m}{2\pi} \left[ \cos \frac{5\pi}{6} \cos \alpha - \sin \frac{5\pi}{6} \sin \alpha - \cos \frac{\pi}{6} \cos \alpha + \sin \frac{\pi}{6} \sin \alpha \right]$$

$$\left[ \sin \frac{\pi}{6} = 0.5; \sin \frac{5\pi}{6} = 0.5; \cos \frac{5\pi}{6} = -\frac{\sqrt{3}}{2}; \cos \frac{\pi}{6} = \frac{\sqrt{3}}{2} \right]$$

$$= -\frac{3V_m}{2\pi} \left[ \cos \frac{5\pi}{6} \cos \alpha - \sin \frac{5\pi}{6} \sin \alpha + \cos \frac{\pi}{6} \cos \alpha + \sin \frac{\pi}{6} \sin \alpha \right]$$

$$= -\frac{3V_m}{2\pi} \left[ 2 \cos \frac{5\pi}{6} \cos \alpha \right] = \frac{3V_m}{2\pi} \left[ \frac{\sqrt{3}}{2} \cos \alpha \right]$$

$$\therefore V_0(\text{avg}) = \frac{3\sqrt{3} V_m \cos \alpha}{2\pi}$$

$$V_0(\text{rms}) = \sqrt{\frac{1}{2\pi/3} \int_{\frac{\pi}{6} + \alpha}^{\frac{5\pi}{6} + \alpha} V_m^2 \sin^2 \omega t \cdot d\omega t} = \sqrt{\frac{3V_m^2}{2\pi} \int_{\frac{\pi}{6} + \alpha}^{\frac{5\pi}{6} + \alpha} \left( \frac{1 - \cos 2\omega t}{2} \right) d\omega t}$$

$$= \sqrt{\frac{3V_m^2}{4\pi} \left[ \omega t - \frac{\sin 2\omega t}{2} \right]_{\frac{\pi}{6} + \alpha}^{\frac{5\pi}{6} + \alpha}}$$

$$= \sqrt{\frac{3V_m^2}{4\pi} \left[ \frac{5\pi}{6} - \frac{\pi}{6} - \frac{1}{2} \left[ \sin 2 \left( \frac{5\pi}{6} + \alpha \right) - \sin 2 \left( \frac{\pi}{6} + \alpha \right) \right] \right]}$$

$$= \frac{\sqrt{3} V_m}{2\sqrt{\pi}} \sqrt{\frac{2\pi}{3} - \frac{1}{2} \left[ \sin \left( \frac{5\pi}{3} + 2\alpha \right) - \sin \left( \frac{\pi}{3} + 2\alpha \right) \right]}$$

$$\left[ \sin \frac{\pi}{3} = \frac{\sqrt{3}}{2}; \cos \frac{\pi}{3} = 0.5; \sin \frac{5\pi}{3} = -\frac{\sqrt{3}}{2}; \cos \frac{5\pi}{3} = 0.5 \right]$$


$$= \frac{\sqrt{3} V_m}{2\sqrt{\pi}} \sqrt{\frac{2\pi}{3} - \frac{1}{2} \left[ \sin \frac{5\pi}{3} \cos 2\alpha + \cos \frac{5\pi}{3} \sin 2\alpha - \sin \frac{\pi}{3} \cos 2\alpha - \cos \frac{\pi}{3} \sin 2\alpha \right]}$$

$$= \frac{\sqrt{3} V_m}{2\sqrt{\pi}} \sqrt{\frac{2\pi}{3} - \frac{1}{2} \left[ \sin \frac{5\pi}{3} \cos 2\alpha + \cos \frac{5\pi}{3} \sin 2\alpha + \sin \frac{\pi}{3} \cos 2\alpha - \cos \frac{\pi}{3} \sin 2\alpha \right]}$$

$$= \frac{\sqrt{3} V_m}{2\sqrt{\pi}} \sqrt{\frac{2\pi}{3} - \frac{1}{2} \cdot 2 \sin \frac{5\pi}{3} \cos 2\alpha} = \frac{\sqrt{3} V_m}{2\sqrt{\pi}} \sqrt{\frac{2\pi}{3} + \frac{\sqrt{3}}{2} \cos 2\alpha}$$

$$\therefore V_0(\text{rms}) = \frac{\sqrt{3} V_m}{2\sqrt{\pi}} \sqrt{\frac{2\pi}{3} + \frac{\sqrt{3}}{2} \cos 2\alpha}$$
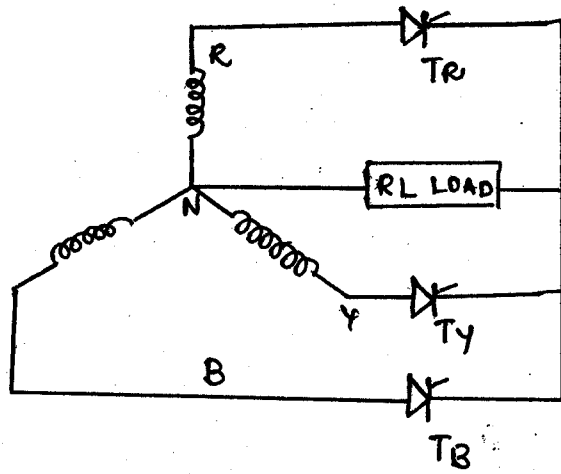
# 3 $\phi$ HALF WAVE CONVERTER WITH RL LOAD!



\*  $T_R, T_Y$  and  $T_B$  are 3 SCRs connected across R, Y and B phase respectively.

\* The SCR connected to the phase with highest +ve value is triggered.

- \*  $T_R$  is triggered when R phase is more +ve ( $\bar{u} V_{RN}$  is +ve)
- \*  $T_Y$  is triggered when Y phase is more +ve.
- \*  $T_B$  is triggered when B phase is more +ve.
- \* Every SCR will conduct for a maximum of  $120^\circ$  after it has been turned ON. Next SCR will turn ON  $120^\circ$  after the previous SCR.
- \* If we say  $\alpha = 0$ , it means  $\omega t = 30^\circ$ .

$\alpha$  can vary b/w  $0$  to  $120^\circ$  (or)  $\omega t = 30^\circ$  to  $150^\circ$ .

For  $\alpha = 0^\circ$ ;  $\omega t = 30^\circ$  [ $T_R$  is ON at  $\omega t = 30^\circ$ ;  $T_Y$  is ON at  $\omega t = 150^\circ$ ;  $T_B$  is ON at  $\omega t = 270^\circ$ ]

Duration.	More +ve	Forward bias	conducting SCR	o/p vge.
$\omega t = 30^\circ \rightarrow 150^\circ$	R phase is more +ve	$T_R$	$T_R$	$V_o = V_{RN}$
$\omega t = 150^\circ \rightarrow 270^\circ$	Y phase is more +ve	$T_Y$	$T_Y$	$V_o = V_{YN}$
$\omega t = 270^\circ \rightarrow 390^\circ$	B phase is more +ve	$T_B$	$T_B$	$V_o = V_{BN}$

For  $\alpha = 30^\circ$ ,  $\omega t = 60^\circ$

$\therefore T_R$  is ON at  $\omega t = 60$ ,  $T_Y$  is ON at  $\omega t = 180$ ;  $T_B$  is ON at  $\omega t = 300$ .

Duration	More +ve phase.	Forward biased SCR	Conducting SCR	O/p $V_{gr}$
$\omega t = 60 \rightarrow 180$	R is more +ve.	$T_R$	$T_R$	$V_O = V_{RN}$
$\omega t = 180$ to $300$	Y is more +ve	$T_Y$	$T_Y$	$V_O = V_{YN}$
$\omega t = 300$ to $420$	B is more +ve	$T_B$	$T_B$	$V_O = V_{BN}$





or  $\alpha = 60^\circ$ ,  $\omega t = 90^\circ$

$T_R$  is ON at  $\omega t = 90$ ,  $T_Y$  is ON at  $\omega t = 210$ ;  $T_B$  is ON at  $\omega t = 330$ .

Duration	More +ve phase.	Forward biased SCR	Conducting SCR	O/p $V_{gr}$
$\omega t = 90 \rightarrow 180$	R is more +ve	$T_R$	$T_R$	$V_O = V_{RN}$
$\omega t = 180 \rightarrow 210$	Y is more +ve	$T_Y$ ↓ though $T_Y$ is FB it is turned ON only at $\omega t = 210$	$T_R$ conducts because due to RL load current takes time to reach zero.	$V_O = V_{RN}$
$\omega t = 210 \rightarrow 330$	Y is +ve	$T_Y$	$T_Y$	$V_O = V_{YN}$
$\omega t = 300 \rightarrow 330$	B is +ve	$T_B$ is FB (ON only at 330)	$T_Y$ still conducts due to RL load current reaches zero slowly	$V_O = V_{YN}$
$\omega t = 330 \rightarrow 420$	B is +ve.	$T_B$	$T_B$	$V_O = V_{BN}$
$\omega t = 420 \rightarrow 450$	R is +ve	$T_R$	$T_B$ still conducts because current takes time to reach zero due to RL load	$V_O = V_{BN}$



+

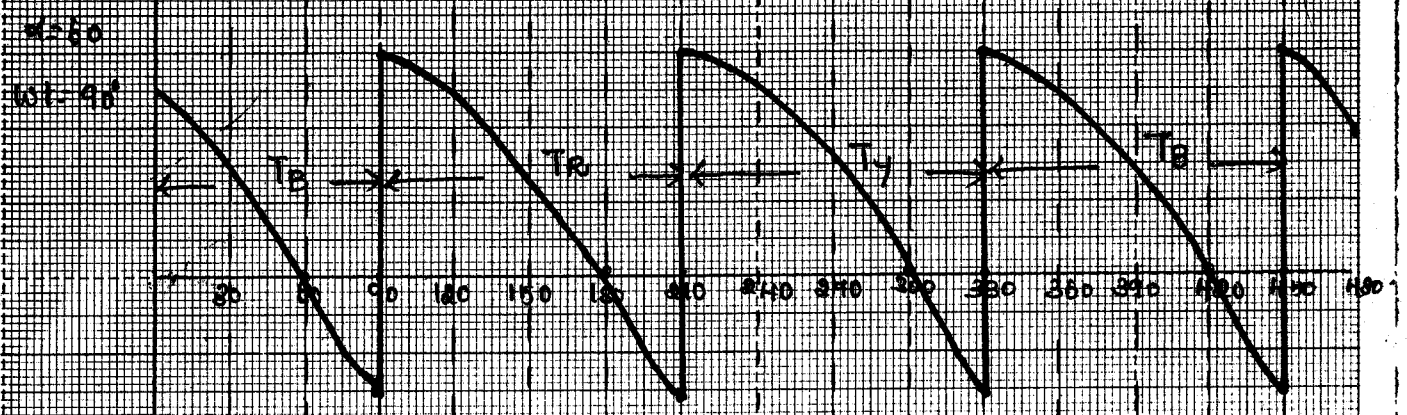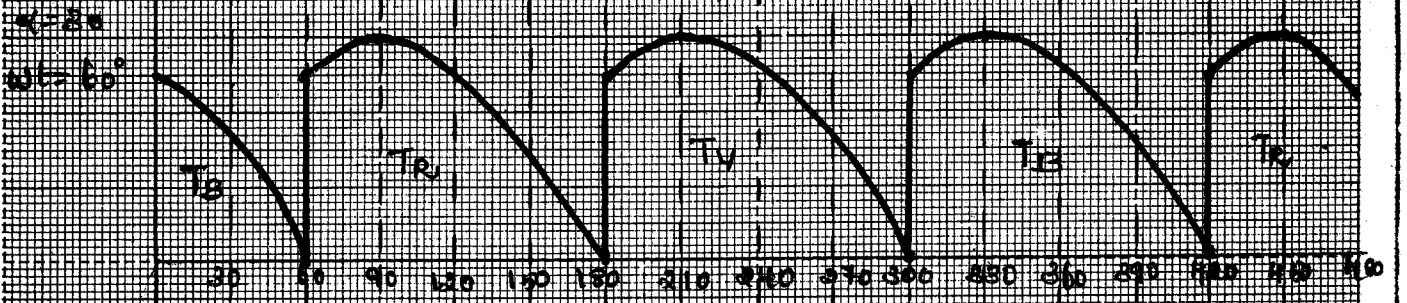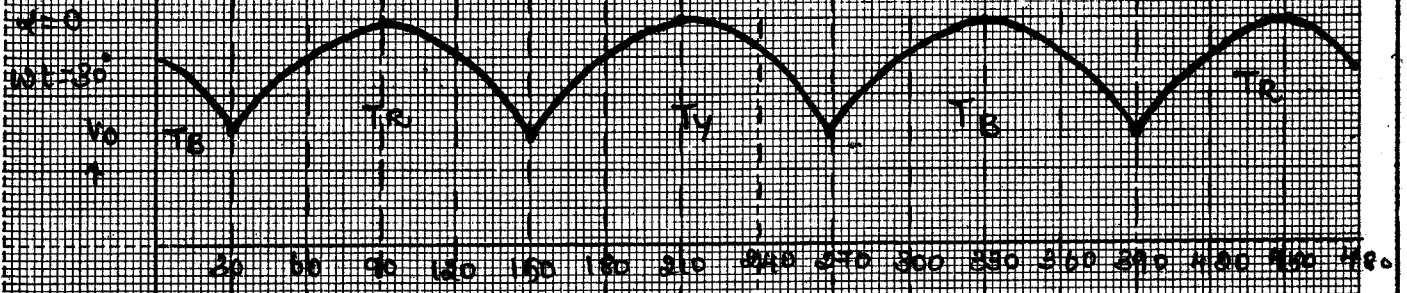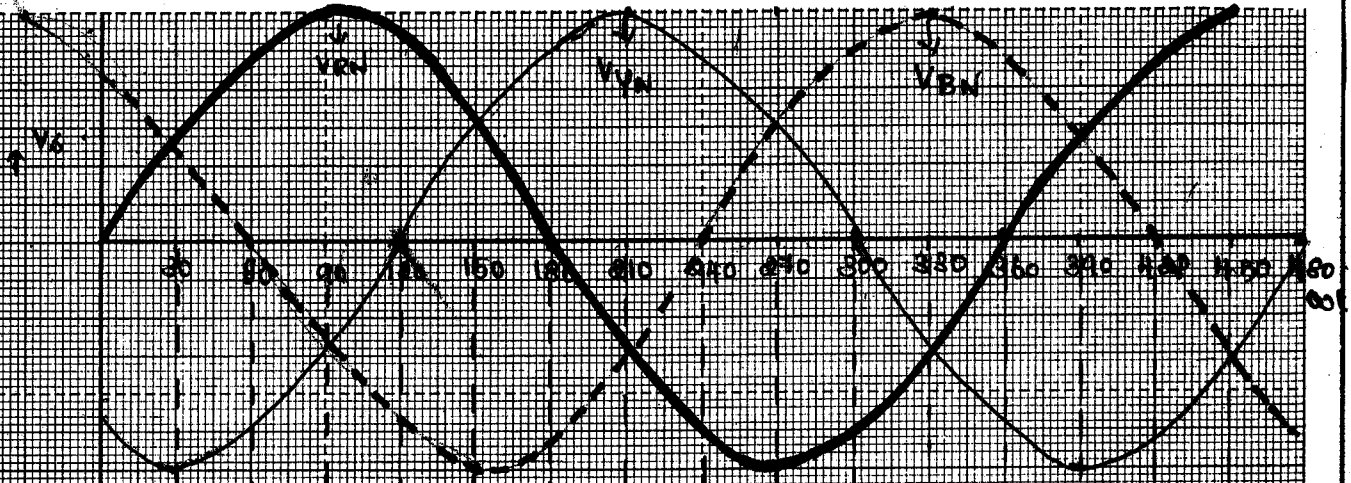


## 3 $\phi$ FULLWAVE CONVERTER:-

It is further divided into

- 3 $\phi$  full wave half controlled converter (or) 3 $\phi$  semiconverter.
- 3 $\phi$  full wave fully controlled converter (or) 3 $\phi$  Full converter.
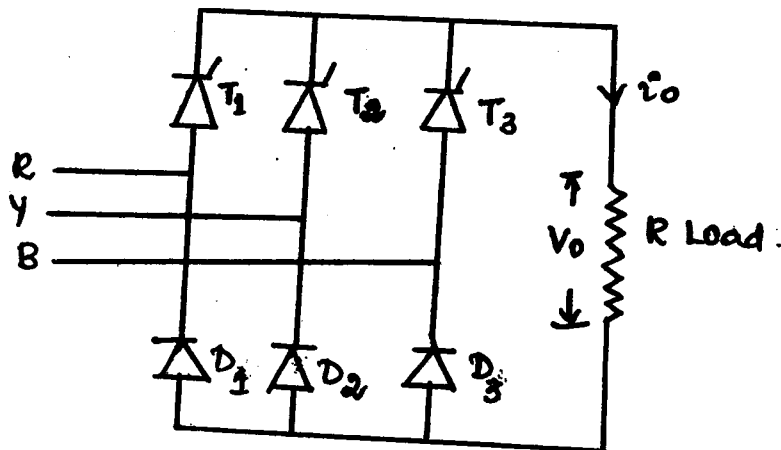
## 3 $\phi$ SEMICONVERTER:- [with R load].



\* Semiconverter uses 3 SCRs  $T_1, T_2, T_3$  and three diodes  $D_1, D_2, D_3$ .

\*  $T_1, T_2$  and  $T_3$  are the POSITIVE GROUP SCRs.

\*  $D_1, D_2$  and  $D_3$  are the NEGATIVE GROUP diodes.

\* By varying the firing angle of the conduction of SCRs in the positive group is varied. But the conduction of diodes in the negative group remains the same.

\* The combination of diodes and SCRs conduct for a time period of  $120^\circ$ .


\* During every 120° one device from the +ve group and one device from the -ve group will conduct.

\* SCR connected to the more +ve phase will conduct.

\* Diode connected to the more -ve phase will conduct.

\*  $V_{RN}, V_{YN}$  &  $V_{BN}$  are phase vgs

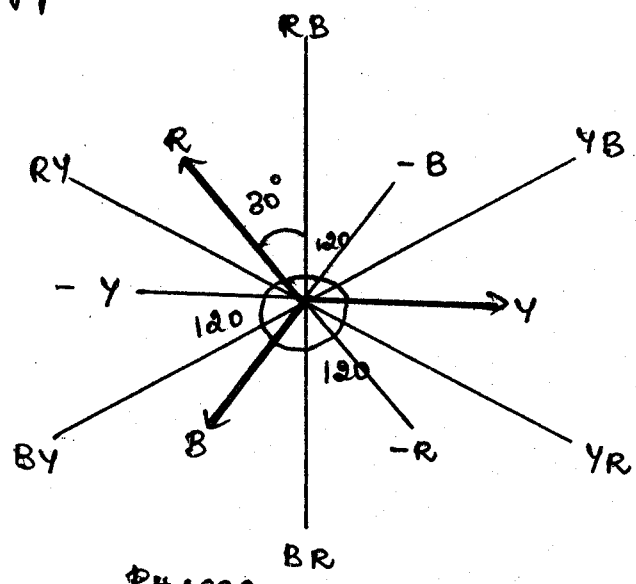\* when any SCR and diode conducts the line vgs is applied to the load. ∴ it is necessary to draw line vgs.



$V_{RY}$  leads R by 30°  
 $V_{RB}$  lags R by 30°

- ↓ RYB
- $V_{RY} - V_{RB}$
  - $V_{YB}$
  - $V_{YR}$
  - $V_{BR}$
  - $V_{BY}$

Phase	SCR	DIODE
R	$T_1$	$D_1$
Y	$T_2$	$D_2$
B	$T_3$	$D_3$

For  $\alpha = 0^\circ$ ; PHASOR  
 $\omega t = 30^\circ$

- $T_1$  is turned ON at  $\omega t = 30^\circ$ ;
- $T_2$  is turned ON at  $\omega t = 150^\circ$ ;
- $T_3$  is turned ON at  $\omega t = 270^\circ$ ;

From  $\omega t = 30^\circ \rightarrow 90^\circ$

\* R phase is more +ve and Y phase is more -ve.

∴  $T_1$  is connected to R phase is turned ON.

$D_2$  connected to Y phase is forward biased

∴  $T_1 D_2$  conducts.

$T_1 D_2$   
 $R - Y = V_{RY}$

∴  $V_o = V_{RY}$ . (o/p traces  $V_{RY}$  line waveform).

From  $\omega t = 90 \rightarrow 150^\circ$

\* R phase is more +ve; B phase is more -ve.

\*  $T_1$  is connected to R phase.

\*  $D_3$  is connected to B phase.

$\therefore T_1 D_3$  conducts

$$V_o = V_{RB}.$$

From  $\omega t = 150 \rightarrow 210^\circ$

\* Y phase is more +ve; B phase is more -ve.

\*  $T_2$  is connected to Y phase. It is triggered at  $\omega t = 150$ .

\*  $D_3$  is connected to B phase

$\therefore T_2 D_3$  conducts.

$$V_o = V_{YB}.$$

From  $\omega t = 210 \rightarrow 270$ .

\* Y phase is more +ve, R phase is more -ve.

\*  $T_2$  is connected to Y phase.

\*  $D_1$  is connected to R phase.

\*  $T_2 D_1$  conducts

$$V_o = V_{YR}.$$

From  $\omega t = 270 \rightarrow 330^\circ$

\* B phase is more +ve; R phase is more -ve.

\*  $T_3$  is connected to B phase;  $D_1$  is connected to R phase.

\*  $T_3 D_1$  conducts;  $V_o = V_{BR}.$

From  $\omega t = 330 \rightarrow 390^\circ$

\* B phase is more +ve; Y phase is more -ve.

\*  $T_3$  is connected to B phase;  $D_2$  is connected to Y phase.

\*  $T_3 D_2$  conducts;  $V_o = V_{BY}$

$$V_0(\text{avg}) = \frac{1}{2\pi/3} \int_{\frac{\pi}{6} + \alpha}^{\frac{5\pi}{6} + \alpha} V_m \sin \omega t \cdot d\omega t = \frac{3}{2\pi} \left\{ \int_{\frac{\pi}{6} + \alpha}^{\frac{\pi}{2}} V_{RY} d\omega t + \int_{\frac{\pi}{2}}^{\frac{5\pi}{6} + \alpha} V_{RB} d\omega t \right\} \quad (83)$$

From phasor diagram,  $V_{RY} = \sqrt{3} V_m \sin(\omega t + 30^\circ) = \sqrt{3} V_m \sin(\omega t + \frac{\pi}{6})$

$$V_{RB} = \sqrt{3} V_m \sin(\omega t - 30^\circ) = \sqrt{3} V_m \sin(\omega t - \frac{\pi}{6})$$

$$\therefore V_0(\text{avg}) = \frac{3}{2\pi} \left\{ \int_{\frac{\pi}{6} + \alpha}^{\frac{\pi}{2}} \sqrt{3} V_m \sin(\omega t + \frac{\pi}{6}) d\omega t + \int_{\frac{\pi}{2}}^{\frac{5\pi}{6} + \alpha} \sqrt{3} V_m \sin(\omega t - \frac{\pi}{6}) d\omega t \right\}$$

$$= \frac{3\sqrt{3} V_m}{2\pi} \left\{ \left[ -\cos(\omega t + \frac{\pi}{6}) \right]_{\frac{\pi}{6} + \alpha}^{\frac{\pi}{2}} + \left[ -\cos(\omega t - \frac{\pi}{6}) \right]_{\frac{\pi}{2}}^{\frac{5\pi}{6} + \alpha} \right\}$$

$$= \frac{-3\sqrt{3} V_m}{2\pi} \left\{ \left[ \cos(\frac{\pi}{2} + \frac{\pi}{6}) - \cos(\frac{\pi}{6} + \alpha + \frac{\pi}{6}) \right] + \left[ \cos(\frac{5\pi}{6} + \alpha - \frac{\pi}{6}) - \cos(\frac{\pi}{2} - \frac{\pi}{6}) \right] \right\}$$

$$= \frac{-3\sqrt{3} V_m}{2\pi} \left\{ \cos \frac{2\pi}{3} - \cos(\frac{\pi}{3} + \alpha) + \cos(\frac{2\pi}{3} + \alpha) - \cos \frac{\pi}{3} \right\}$$

$$= \frac{-3\sqrt{3} V_m}{2\pi} \left\{ \cos \frac{2\pi}{3} - \cos \frac{\pi}{3} \cos \alpha + \sin \frac{\pi}{3} \sin \alpha + \cos \frac{2\pi}{3} \cos \alpha - \sin \frac{2\pi}{3} \sin \alpha - \cos \frac{\pi}{3} \right\}$$

$$= \frac{-3\sqrt{3} V_m}{2\pi} \left\{ -\frac{1}{2} - \frac{1}{2} * \cos \alpha + \frac{\sqrt{3}}{2} \sin \alpha + -\frac{1}{2} \cos \alpha - \frac{\sqrt{3}}{2} \sin \alpha - \frac{1}{2} \right\}$$

$$= \frac{3\sqrt{3} V_m}{2\pi} \left[ \frac{1}{2} + \frac{1}{2} \cos \alpha + \frac{1}{2} \cos \alpha + \frac{1}{2} \right]$$

$$= \frac{3\sqrt{3} V_m}{2\pi} [1 + \cos \alpha]$$

This is derived for  $\alpha = 30^\circ$  (or) for  $\alpha < 60^\circ$

$$\therefore \boxed{V_0(\text{avg}) = \frac{3\sqrt{3} V_m}{2\pi} [1 + \cos \alpha]}$$

For  $\alpha \geq 60^\circ$


$$V_0 = \frac{1}{2\pi/3} \int_{\frac{\pi}{6} + \alpha}^{\frac{\pi}{2} + \pi/6} \sqrt{3} V_m \sin(\omega t - \pi/6) d\omega t = \frac{3\sqrt{3} V_m}{2\pi} [1 + \cos \alpha]$$


Phase  
in deg

Lines  
in deg

$\alpha = 0$   
 $\omega = 30$


No  
→

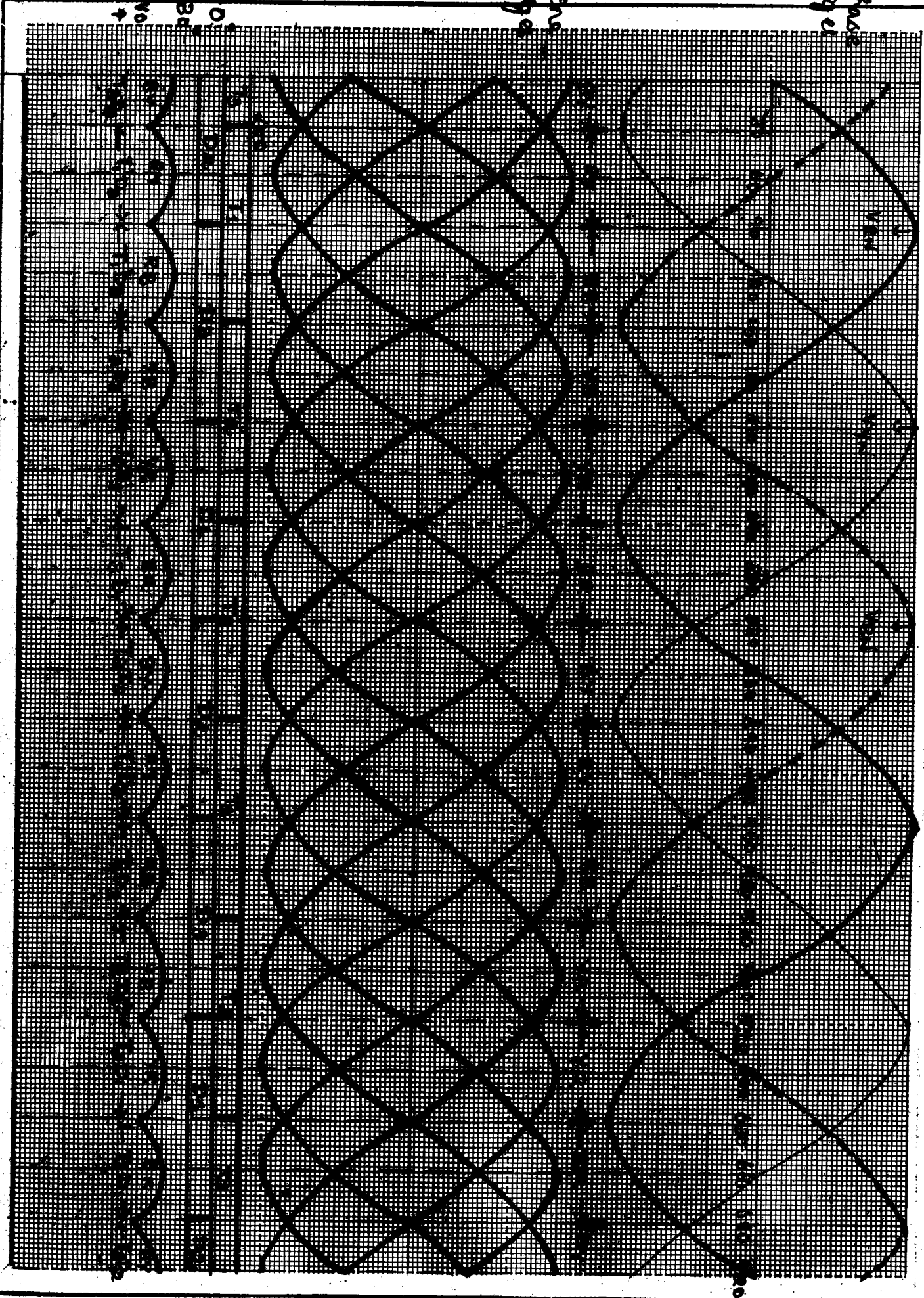

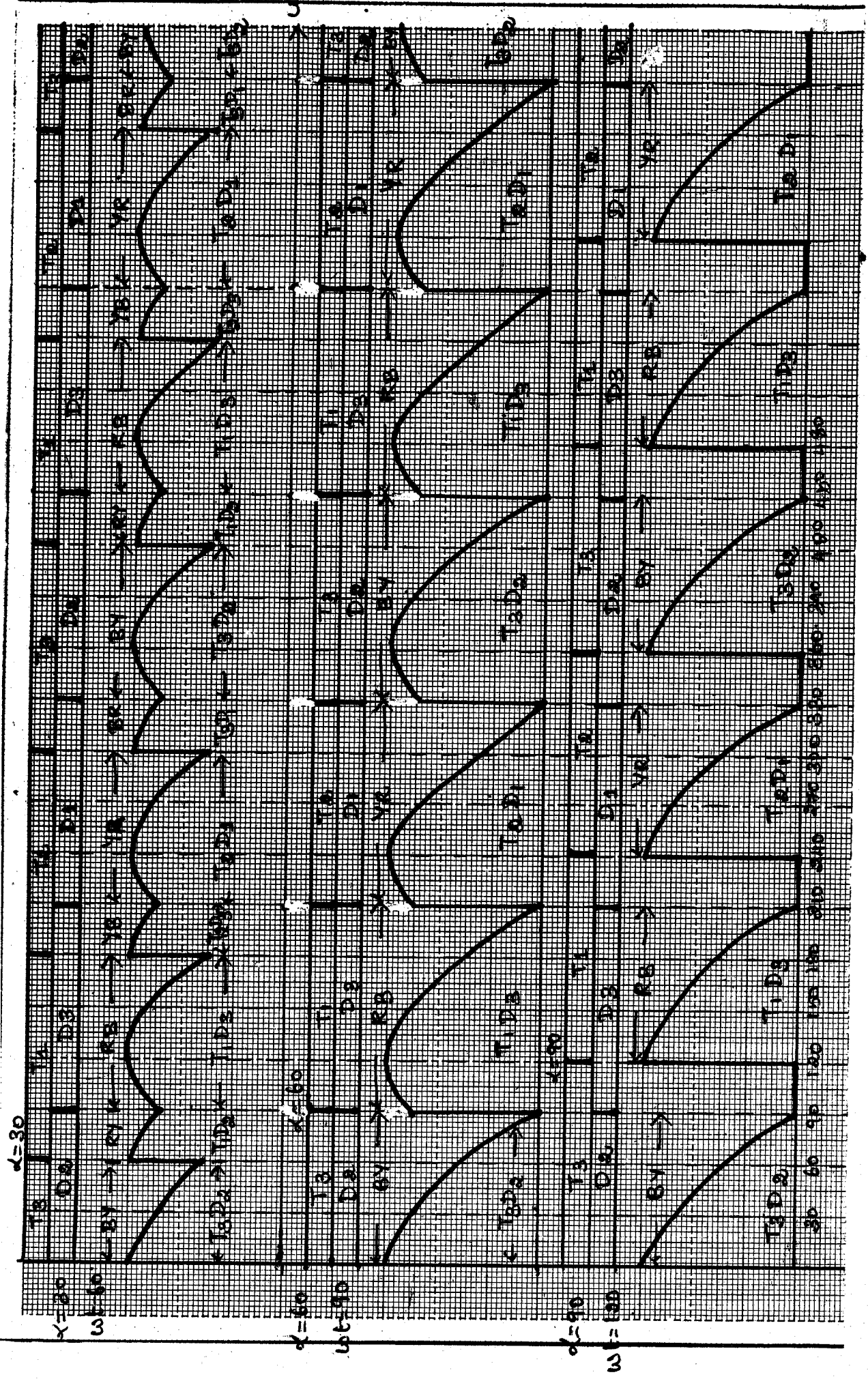
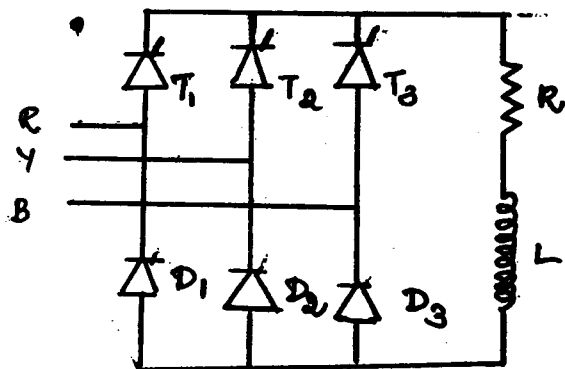
## 3 $\phi$ SEMICONVERTER WITH RL load.

[The wave forms and explanations are same as that of R load]



- \*  $T_1, T_2, T_3$  are SCRs
- \*  $D_1, D_2, D_3$  are diodes.
- \*  $T_1, T_2, T_3$  are +ve group SCRs
- \*  $D_1, D_2, D_3$  are -ve group diodes

\* By varying the firing angle, the conduction of SCRs in the +ve group is varied. But the conduction of diodes in the -ve group remains the same.

\* The combination of diodes and SCRs conduct for a time period of  $120^\circ$ .

\* For every  $120^\circ$ , one device from the +ve group and one device from the -ve group will conduct.

\* SCR connected to the more +ve phase will conduct.

\* Diode connected to more -ve phase will conduct.

\* When any SCR and diode conduct the line voltage is applied to the load.  $\therefore$  it is necessary to draw line vgs.

For  $\alpha = 0^\circ$ ;  $\omega t = 30^\circ$

$T_1$  is turned ON at  $\omega t = 30^\circ$ ,  $T_2$  is turned ON at  $\omega t = 150^\circ$ .

$T_3$  is turned ON at  $\omega t = 270^\circ$ .



From  $\omega t = 30 \rightarrow 90$

- \* R phase is more +ve; Y phase is more -ve.
  - \*  $T_1$  is connected to R phase and is turned ON.
  - \*  $D_2$  is connected to Y phase and conducts.
- $\therefore T_1 D_2$  conducts.
- $\therefore V_o = V_{RY}$ .

From  $\omega t = 90$  to  $150$

- \* R is +ve; B is more -ve.
  - \*  $T_1$  is connected to R phase.
  - \*  $D_3$  is connected to B phase.
- $\therefore T_1 D_3$  conducts

$$V_o = V_{RB}$$

From  $\omega t = 150$  to  $210$

- \* Y is more +ve; B is more -ve.
  - \*  $T_2$  is connected to Y phase.
  - \*  $D_3$  is connected to B phase.
- \*  $T_2 D_3$  conducts.

$$V_o = V_{YB}$$

From  $\omega t = 210$  to  $270$

- \* Y phase is more +ve; R phase is more -ve.
  - \*  $T_2$  is connected to Y phase.
  - \*  $D_1$  is connected to R phase.
- \*  $T_2 D_1$  conducts.


$$\therefore V_o = V_{YR}$$

From  $\omega t = 270 \rightarrow 330$

- \* B phase is more +ve; R phase is more -ve.
- \*  $T_3$  is connected to B phase.
- \*  $D_1$  is connected to R phase.
- \*  $T_3 D_1$  conducts.
- \*  $V_o = V_{BR}$ .

From  $\omega t = 330 \rightarrow 390$

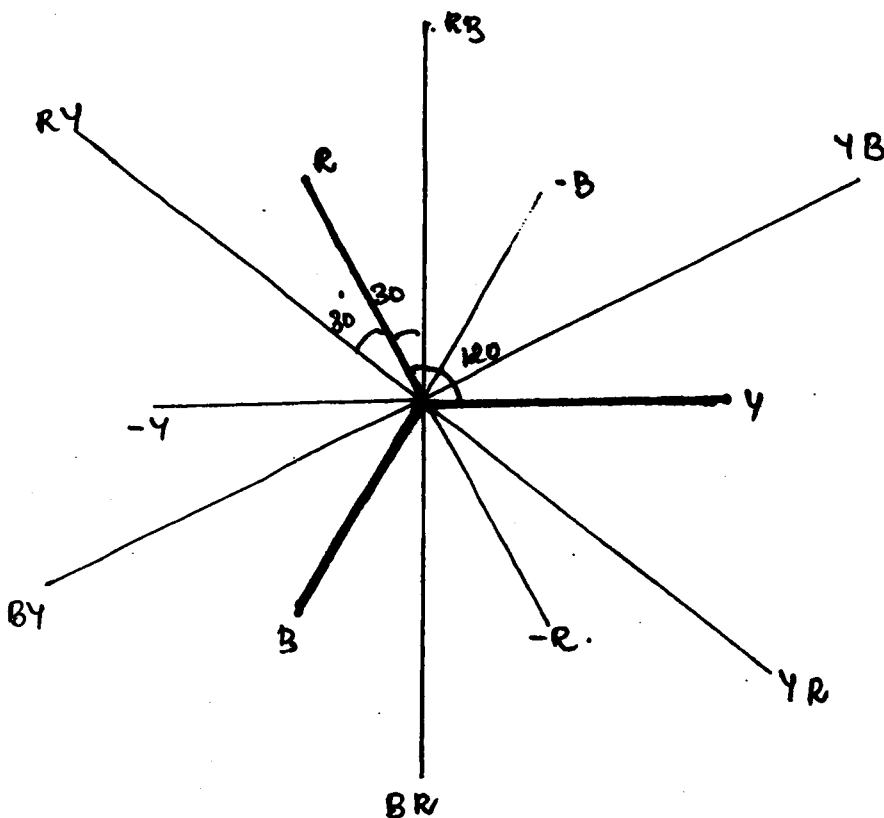- \* B phase is more +ve; Y phase is more -ve.
- \*  $T_3$  is connected to B phase.
- \*  $D_2$  is connected to Y phase.
- \*  $T_3 D_2$  conducts.
- \*  $V_o = V_{BY}$ .



phase	SCR	diode
R	$T_1$	$D_1$
Y	$T_2$	$D_2$
B	$T_3$	$D_3$

Similarly From  $\omega t = 330 \rightarrow 360$   $T_2$  follows reverse  $v_{ge}$   
 From  $\omega t = 450 \rightarrow 480$   $T_3$  follows reverse  $v_{ge}$ .

For  $\alpha < 60^\circ$

$$V_o(\text{avg}) = \frac{1}{2\pi/3} \int_{\frac{\pi}{6} + \alpha}^{\frac{5\pi}{6} + \alpha} V_m \sin \omega t \cdot d\omega t$$

$$= \frac{3}{2\pi} \left\{ \int_{\frac{\pi}{6} + \alpha}^{\frac{\pi}{2}} V_{RY} d\omega t + \int_{\frac{\pi}{2}}^{\frac{5\pi}{6} + \alpha} V_{RB} d\omega t \right\}$$

$V_{RY} = \sqrt{3} V_m \sin(\omega t + \frac{\pi}{6})$  ;  $V_{RB} = \sqrt{3} V_m \sin(\omega t - \frac{\pi}{6})$

[Refer phasor diagram in page 82]

$$V_o(\text{avg}) = \frac{3}{2\pi} \left\{ \int_{\frac{\pi}{6} + \alpha}^{\frac{\pi}{2}} \sqrt{3} V_m \sin(\omega t + \frac{\pi}{6}) \cdot d\omega t + \int_{\frac{\pi}{2}}^{\frac{5\pi}{6} + \alpha} \sqrt{3} V_m \sin(\omega t - \frac{\pi}{6}) d\omega t \right\}$$

(Already solved in page 83)

$$= \frac{3\sqrt{3} V_m}{2\pi} [1 + \cos \alpha]$$

$\therefore V_o(\text{avg}) = \frac{3\sqrt{3} V_m}{2\pi} [1 + \cos \alpha]$

For  $\alpha \geq 60^\circ$


$$V_o(\text{avg}) = \frac{1}{2\pi} \int_{\frac{\pi}{6} + \alpha}^{\frac{7\pi}{6}} V_{RB} d\omega t = \frac{3}{2\pi} \int_{\frac{\pi}{6} + \alpha}^{\frac{7\pi}{6}} \sqrt{3} V_m \sin(\omega t - \frac{\pi}{6}) d\omega t$$

$\therefore V_o(\text{avg}) = \frac{3\sqrt{3} V_m}{2\pi} [1 + \cos \alpha]$

Phase  
1968


Area  
1968

Area  
1968

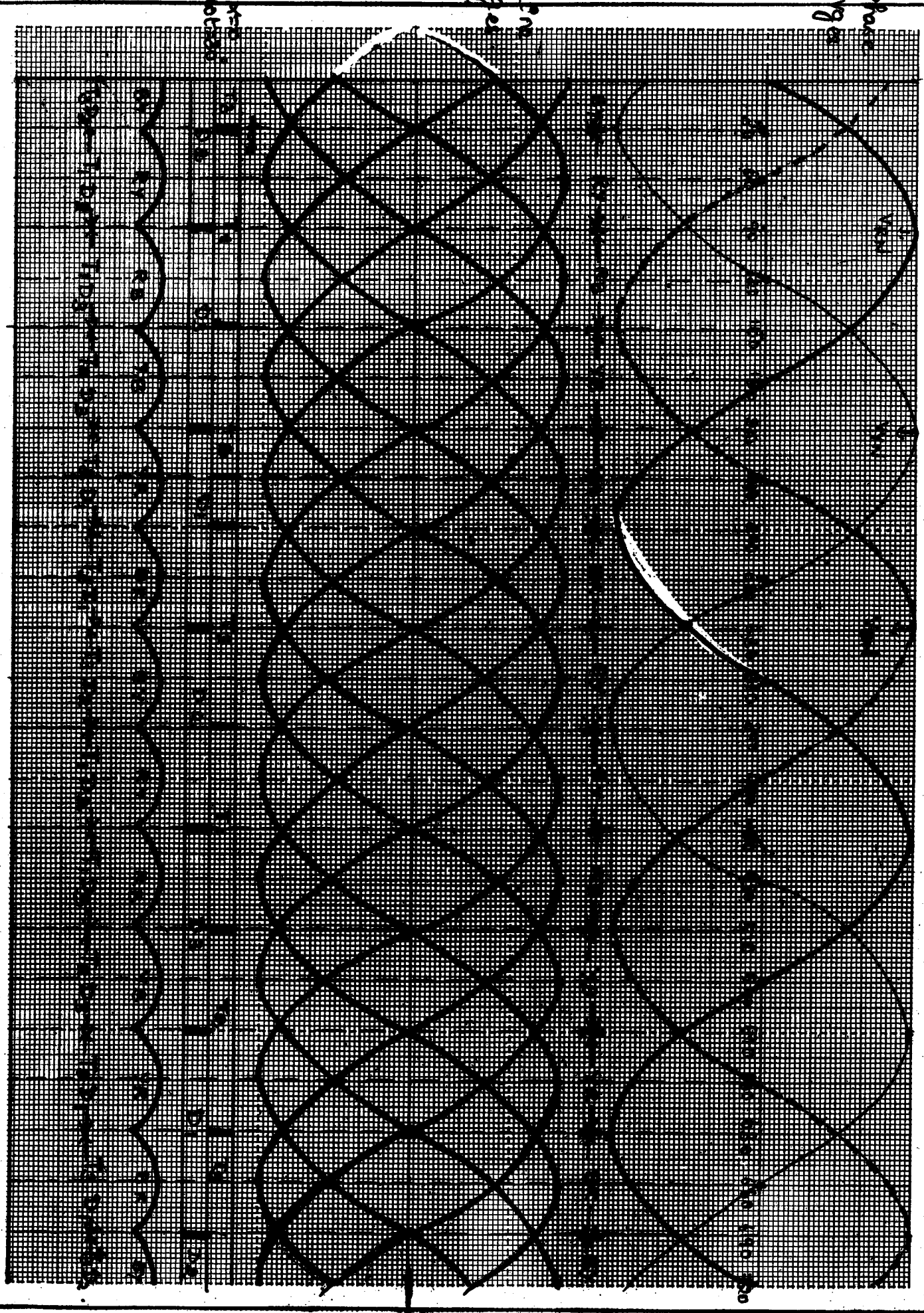


$\alpha = 30^\circ$


$X = 80$   
 $ut = 60$

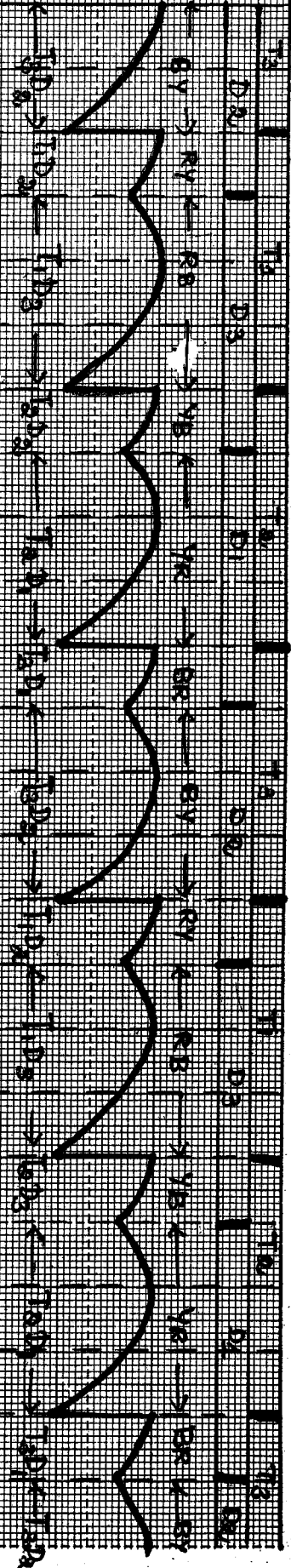

$\alpha = 60$   
 $ut = 60$

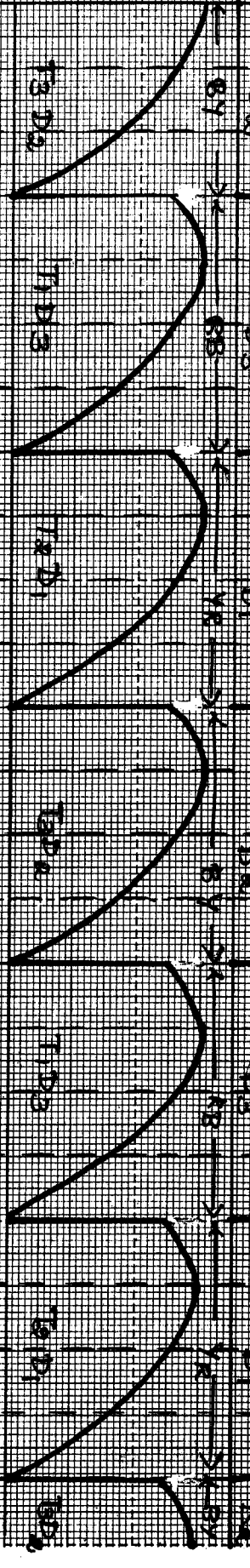


$\alpha = 90$   
 $ut = 120$

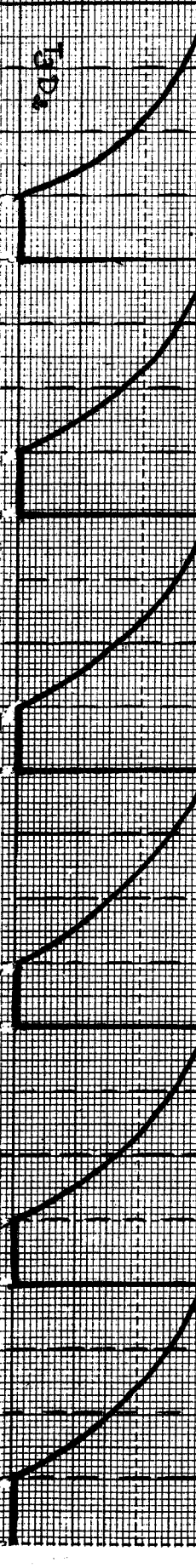

3φ FULL CONVERTER: [with R load]

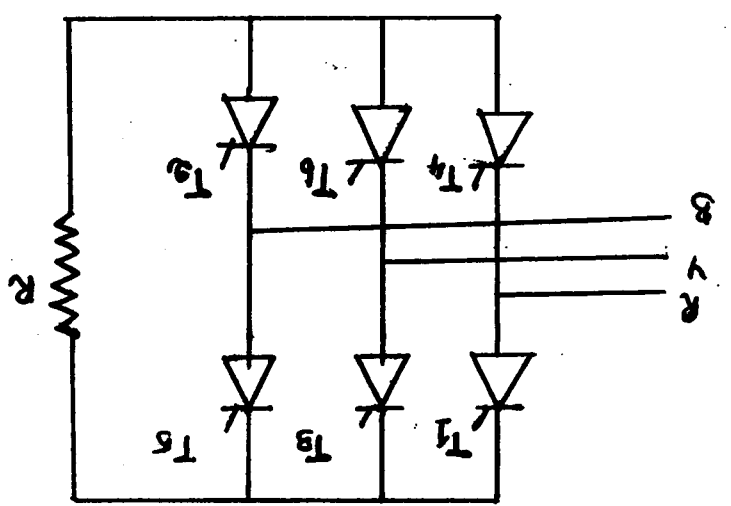
\* Full converter consists of 6 SCRs.  
 \* T<sub>1</sub>, T<sub>8</sub>, T<sub>5</sub> are SCRs of the +ve group.  
 \* T<sub>4</sub>, T<sub>6</sub>, T<sub>2</sub> are SCRs of the -ve group.



\* Only two SCRs conduct in any interval.

- \* Each SCR conducts for 120°.
- \* Every SCR pair conducts for an interval of 60°.
- \* SCRs are triggered in the sequence T<sub>1</sub> → T<sub>2</sub> → T<sub>3</sub> → T<sub>4</sub> → T<sub>5</sub> → T<sub>6</sub>.
- \* Triggering delay between individual SCRs is 60°.
- \* If T<sub>1</sub> is triggered at  $\alpha = 0$ , then T<sub>2</sub> is triggered at  $\alpha = 60^\circ$ , T<sub>3</sub> at  $\alpha = 120^\circ$ ; T<sub>4</sub> at  $\alpha = 180^\circ$ ; T<sub>5</sub> at  $\alpha = 240^\circ$ ; T<sub>6</sub> at  $\alpha = 300^\circ$ .

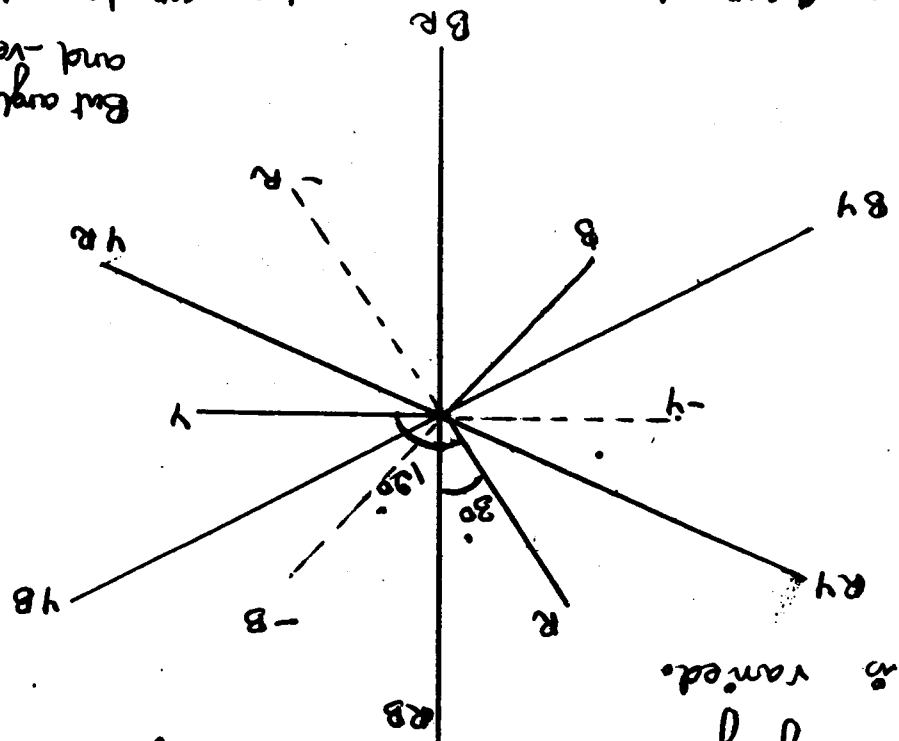\* By varying  $\alpha$  the conduction of SCRs in both the group is varied.



\* Always a SCR from +ve group and one SCR from -ve group will conduct.  
 \* Angle delay b/w SCRs of +ve group on 180° with 120° delay. T<sub>2</sub>, T<sub>4</sub>, T<sub>6</sub> conduct.  
 \* Angle delay b/w SCRs of -ve group on 60° with 120° delay. T<sub>1</sub>, T<sub>3</sub>, T<sub>5</sub> conduct.  
 \* Turn on 60° after T<sub>1</sub> at 30°, T<sub>2</sub> will turn on 60° after T<sub>1</sub> and so on.]  
 \* But angle delay b/w SCR of +ve and -ve group is 60°.

+

For  $\alpha = 0, \omega t = 30$

- \*  $T_1$  is ON at  $\omega t = 30$  ;
- \*  $T_3$  is ON at  $\omega t = 150$  ;
- \*  $T_5$  is ON at  $\omega t = 270$  ;

-ve group

- \*  $T_2$  is ON at  $\omega t = 90$
- \*  $T_4$  is ON at  $\omega t = 210$
- \*  $T_6$  is ON at  $\omega t = 330$ .

From  $\omega t = 30 \rightarrow 90$

- \* R phase is more +ve; Y phase is more -ve.
- \*  $T_1$  is connected to R phase.
- \*  $T_6$  is connected to Y phase.
- \*  $\therefore T_1, T_6$  conducts.
- $V_o = V_{RY}$ .

From  $\omega t = 90$  to  $150$ .

- \* R phase is more +ve; B phase is more -ve.
- \*  $T_1$  is connected to R phase.
- \*  $T_2$  is connected to B phase.
- \*  $T_1, T_2$  conducts
- $V_o = V_{RB}$

From  $\omega t = 150 \rightarrow 210$

- \* Y phase is more +ve; B phase is more -ve.
- \*  $T_3$  is connected to Y phase.
- \*  $T_2$  is connected to B phase.
- \*  $T_3, T_2$  conducts
- $V_o = V_{YB}$

From  $\omega t = 210 \rightarrow 270$ .

\* Y phase is more +ve; R phase is more -ve.

\*  $T_3$  is connected to Y phase.

\*  $T_4$  is connected to R phase.

\*  $T_3 T_4$  conducts

$$V_0 = V_{YR}.$$

From  $\omega t = 270 \rightarrow 330$

\* B phase is more +ve; R phase is more -ve.

\*  $T_5$  is connected to B phase.

\*  $T_4$  is connected to R phase.

\*  $T_5 T_4$  conducts.

$$V_0 = V_{BR}$$

From  $\omega t = 330 \rightarrow 390$

\* B phase is more +ve; Y phase is more -ve.

\*  $T_5$  is connected to B phase.

\*  $T_6$  is connected to Y phase.

\*  $T_5 T_6$  conducts

$$* V_0 = V_{BY}.$$

output vge eqn.

$$\text{For } \alpha \leq 60^\circ \quad V_0(\text{avg}) = \frac{1}{\pi/3} \int_{\frac{\pi}{6} + \alpha}^{\frac{\pi}{2} + \alpha} V_{RY} \, d\omega t = \frac{3}{\pi} \int_{\frac{\pi}{6} + \alpha}^{\frac{\pi}{2} + \alpha} \sqrt{3} V_m \sin(\omega t + \frac{\pi}{6}) \, d\omega t.$$



\* All combinations of SCRs conduct only for 60°

∴ time period = 60° = π/3

$$\begin{aligned} \therefore V_o(\text{avg}) &= \frac{3\sqrt{3} V_m}{\pi} \left[ -\cos(\omega t + \frac{\pi}{6}) \right]_{\frac{\pi}{6} + \alpha}^{\frac{\pi}{2} + \alpha} \\ &= -\frac{3\sqrt{3} V_m}{\pi} \left[ \cos(\frac{\pi}{2} + \alpha + \frac{\pi}{6}) - \cos(\frac{\pi}{6} + \alpha + \frac{\pi}{6}) \right] \\ &= -\frac{3\sqrt{3} V_m}{\pi} \left[ \cos(\frac{2\pi}{3} + \alpha) - \cos(\frac{\pi}{3} + \alpha) \right] \\ &= -\frac{3\sqrt{3} V_m}{\pi} \left[ \cos \frac{2\pi}{3} \cos \alpha - \sin \frac{2\pi}{3} \sin \alpha - \cos \frac{\pi}{3} \cos \alpha + \sin \frac{\pi}{3} \sin \alpha \right] \\ &= -\frac{3\sqrt{3} V_m}{\pi} \left[ -0.5 \cos \alpha - \frac{\sqrt{3}}{2} \sin \alpha - 0.5 \cos \alpha + \frac{\sqrt{3}}{2} \sin \alpha \right] \\ &= -\frac{3\sqrt{3} V_m}{\pi} [-\cos \alpha] = \frac{3\sqrt{3} V_m}{\pi} \cos \alpha \end{aligned}$$

$$\therefore V_o(\text{avg}) = \frac{3\sqrt{3} V_m \cos \alpha}{\pi}$$

for α ≥ 60°

$$\begin{aligned} V_o(\text{avg}) &= \frac{1}{\pi/3} \int_{\frac{\pi}{6} + \alpha}^{\frac{5\pi}{6}} V_m \sin(\omega t) dt \\ &= \frac{3}{\pi} \int_{\frac{\pi}{6} + \alpha}^{\frac{5\pi}{6}} \sqrt{3} V_m \sin(\omega t + \frac{\pi}{6}) dt \\ &= \frac{3\sqrt{3} V_m}{\pi} \left[ -\cos(\omega t + \frac{\pi}{6}) \right]_{\frac{\pi}{6} + \alpha}^{\frac{5\pi}{6}} \end{aligned}$$


$$V_o(\text{avg}) = \frac{3\sqrt{3} V_m}{\pi} \left[ 1 + \cos(\frac{\pi}{3} + \alpha) \right]$$

for α > 90° 3φ full converter behaves like inverter.

Phase  
by  
1942

Area  
by  
1942


Area  
by  
1942

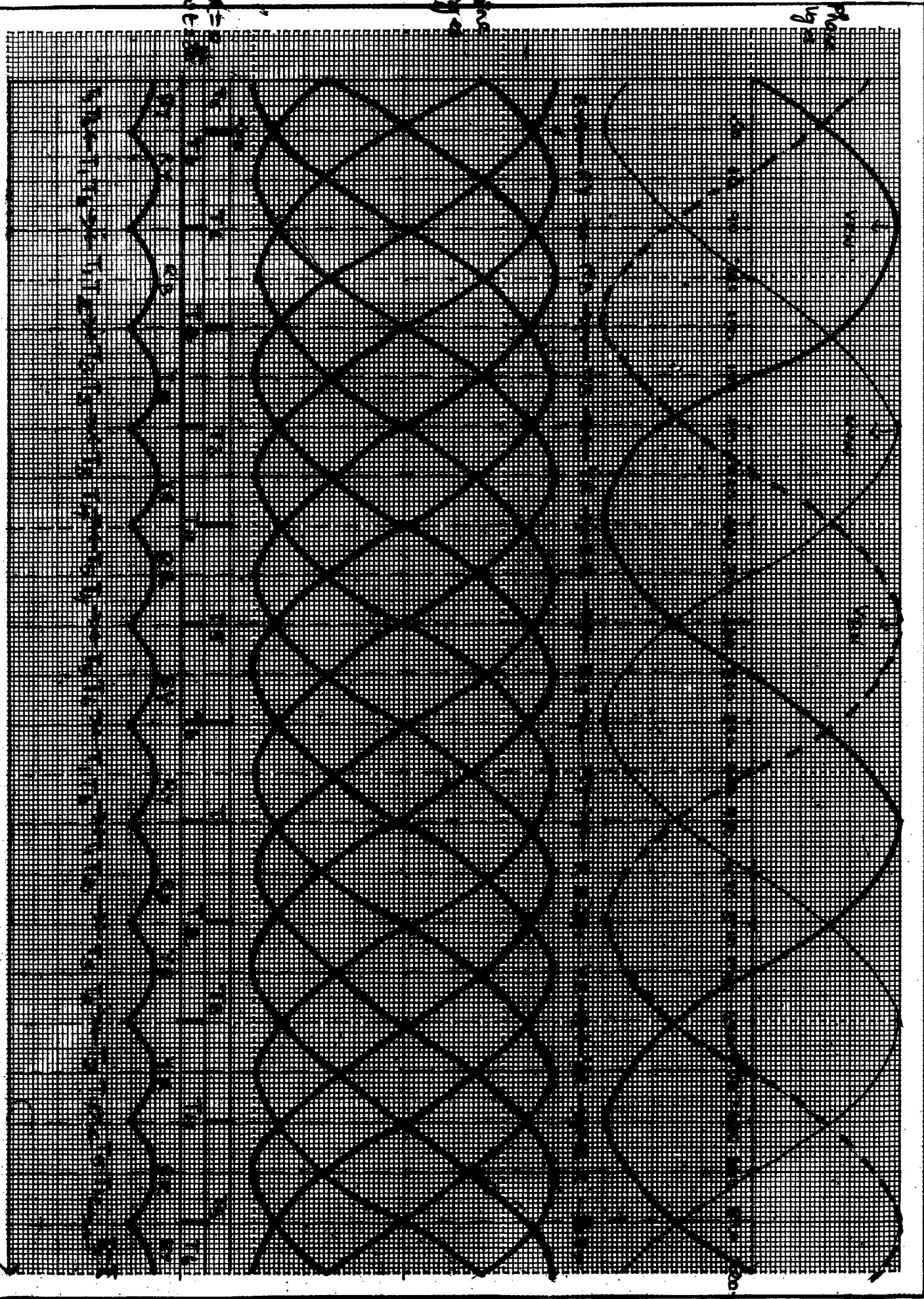


$k = 90$   
 $\delta = 180$

$k = 60$   
 $\delta = 90$


$k = 30$   
 $\delta = 60$

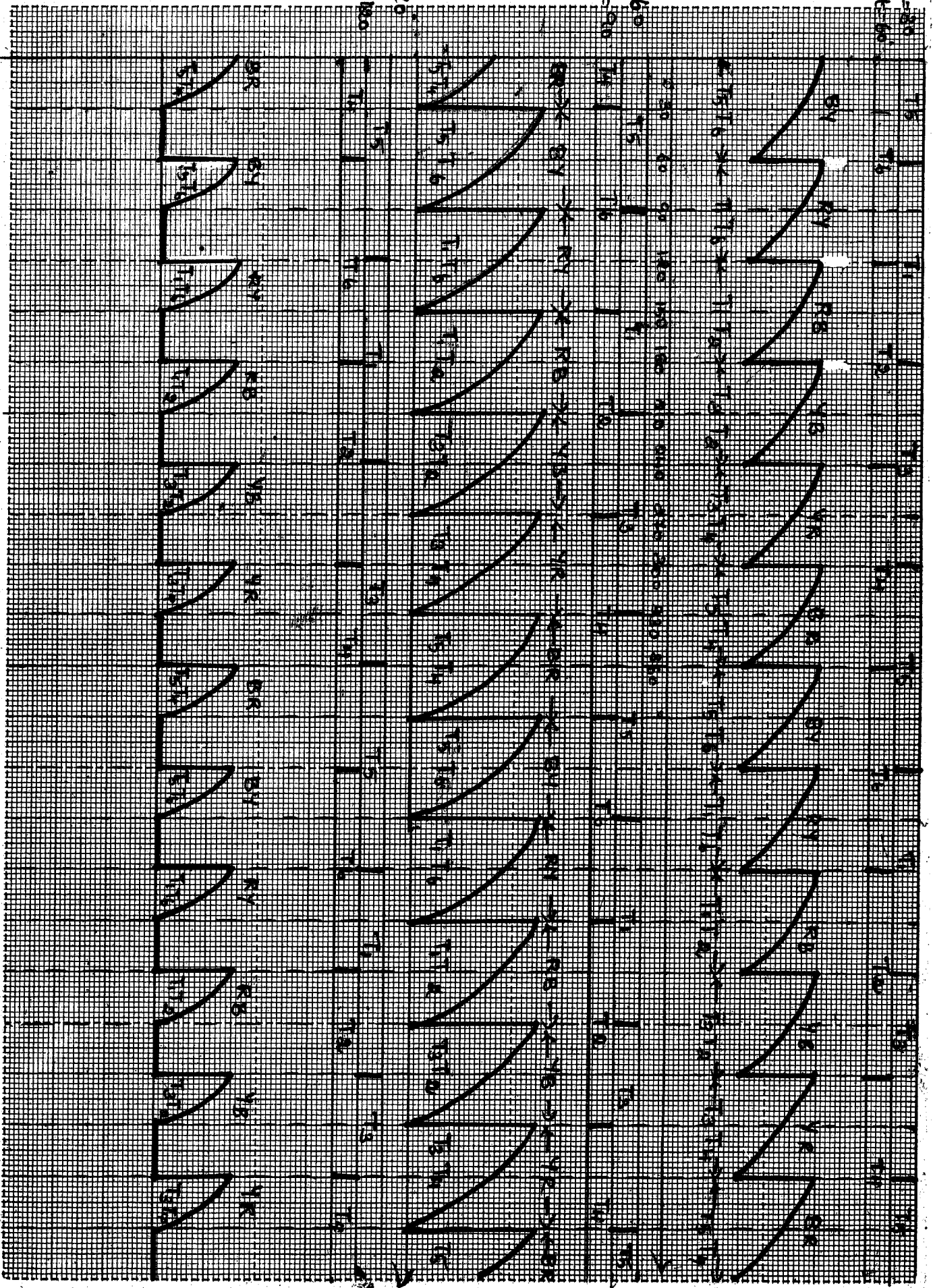

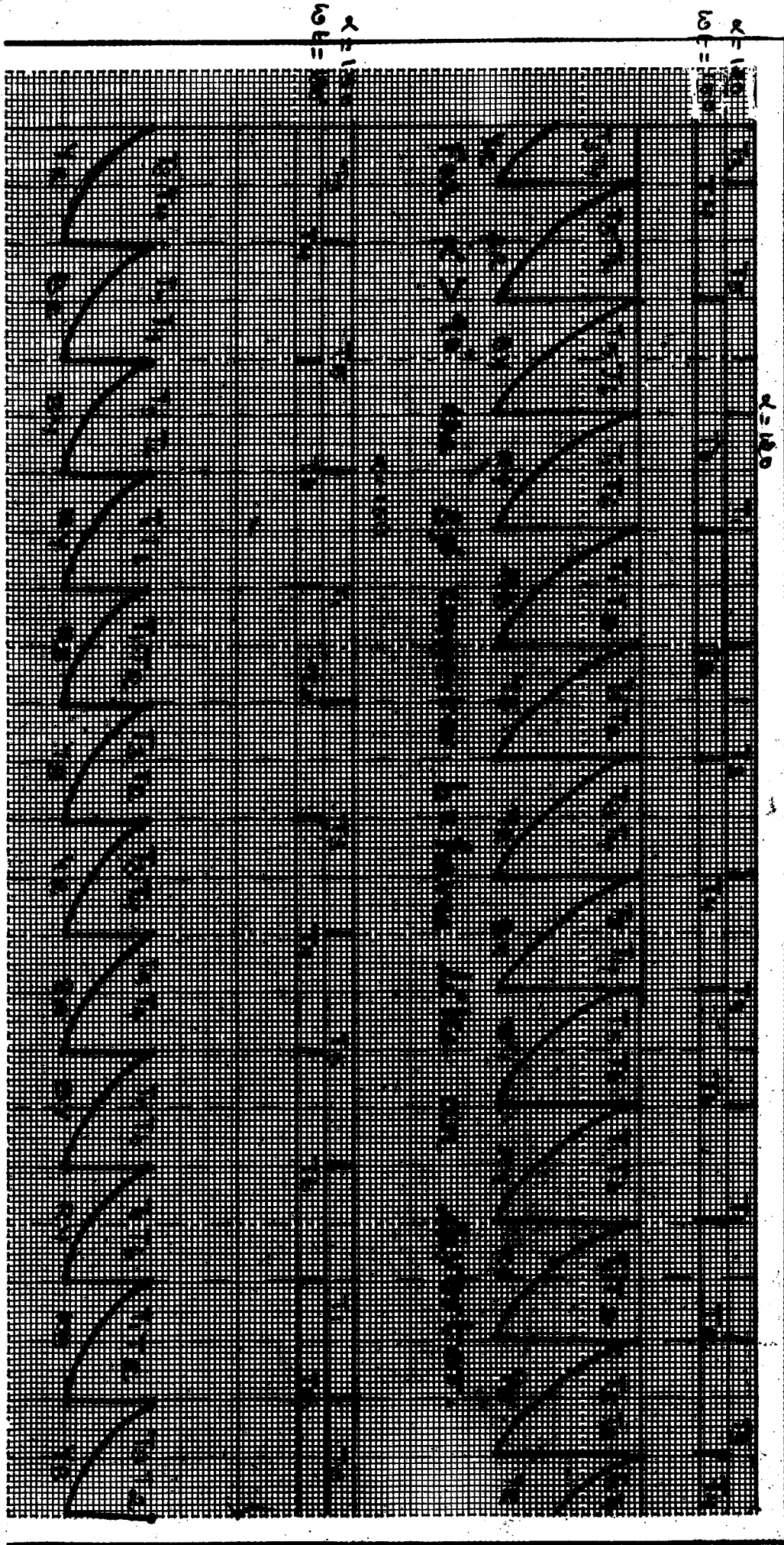

+

### 3φ FULL CONVERTER:- [with R-L load]

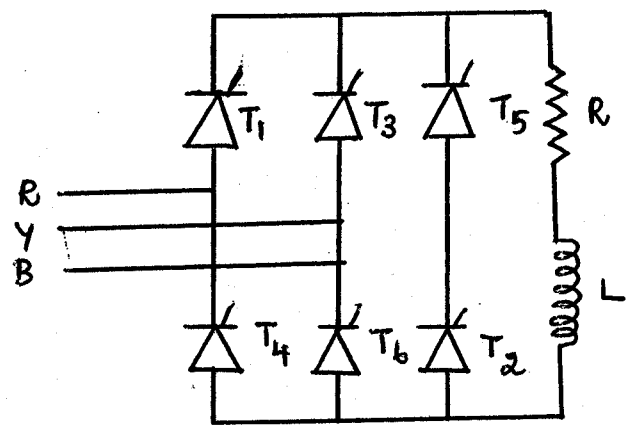

The explanations are same as that of 3φ full converter with R-L load.

- \* Output voltage equation are also same.
- \* The waveforms are also same except for  $\alpha = 90^\circ$ . For  $\alpha = 90^\circ$  the waveforms are as follows.

For  $\alpha \leq 60^\circ$ ;


$$V_o \text{ (avg)} = \frac{1}{\pi/3} \int_{\frac{\pi}{6} + \alpha}^{\frac{\pi}{2} + \alpha} V_{RY} dt = \frac{3}{\pi} \int_{\frac{\pi}{6} + \alpha}^{\frac{\pi}{2} + \alpha} \sqrt{3} V_m \sin(\omega t + \frac{\pi}{6}) dt$$

$$\therefore V_o \text{ (avg)} = \frac{3\sqrt{3} V_m}{\pi} \cos \alpha \quad (\text{already solved})$$

For  $\alpha > 60^\circ$ ;

$$V_o \text{ (avg)} = \frac{1}{\pi/3} \int_{\frac{\pi}{6} + \alpha}^{\frac{5\pi}{6}} V_{RY} dt = \frac{3}{\pi} \int_{\frac{\pi}{6} + \alpha}^{\frac{5\pi}{6}} \sqrt{3} V_m \sin(\omega t + \frac{\pi}{6}) dt$$
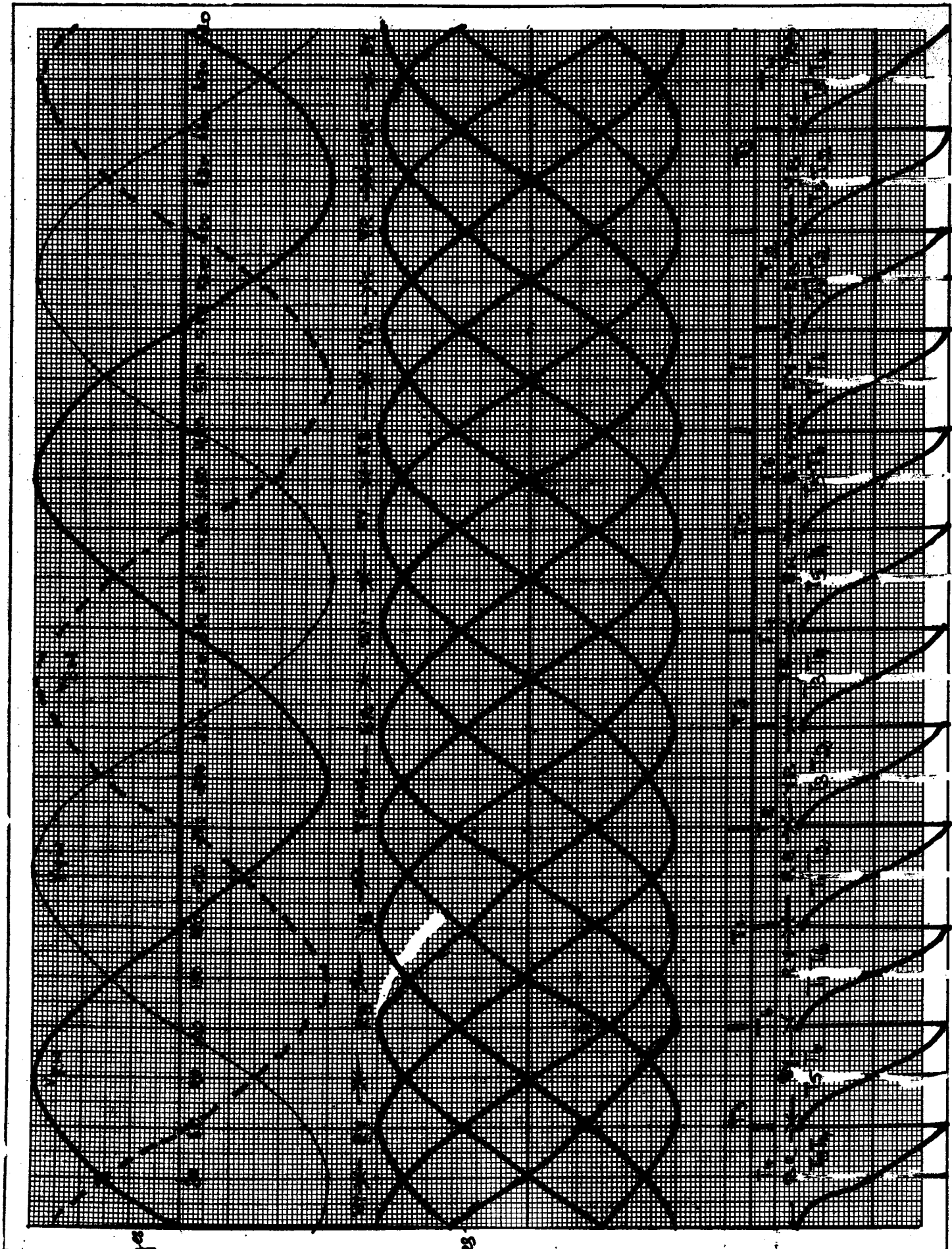
$$V_o \text{ (avg)} = \frac{3\sqrt{3} V_m}{\pi} \left[ 1 + \cos(\frac{\pi}{3} + \alpha) \right]$$



Phase  
Voltages

Line  
Voltages


$\alpha = 90$   
 $wt = 120$

# DUAL CONVERTERS (OR) FOUR QUADRANT CONVERTER:-


\* Two full converters connected in antiparallel (or) back to back with the load in parallel to them is called as a "dual converter".

\* It can be operated in any one of the four quadrants

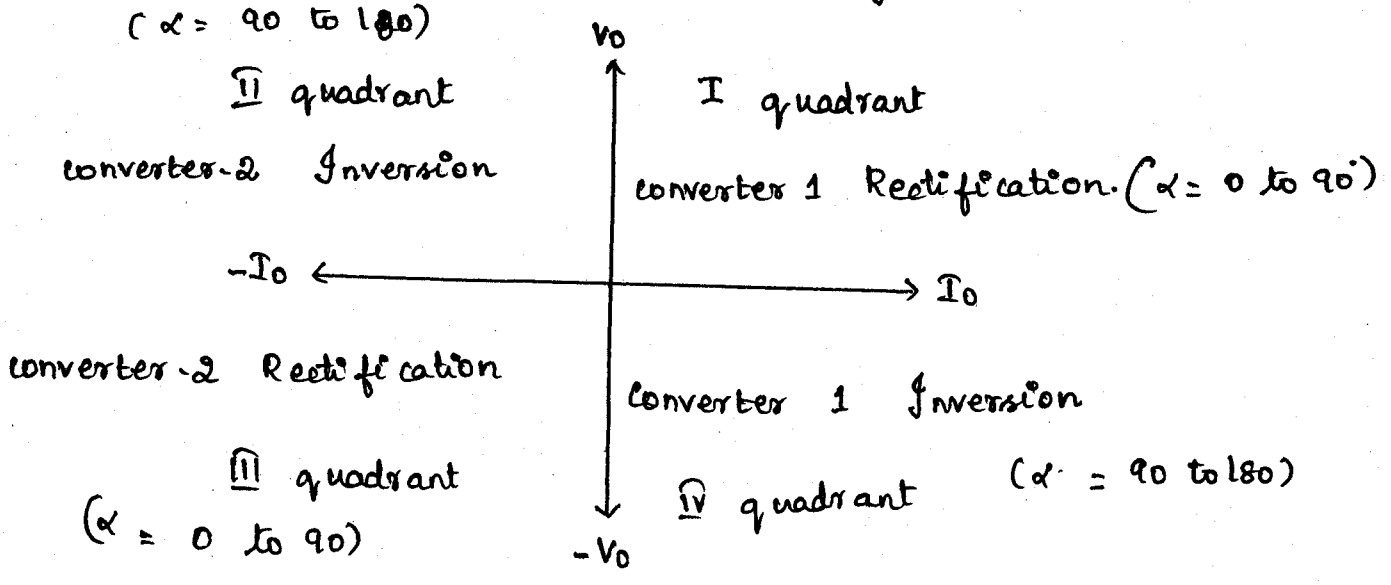\* The average value of output voltage and current can be either positive or negative.


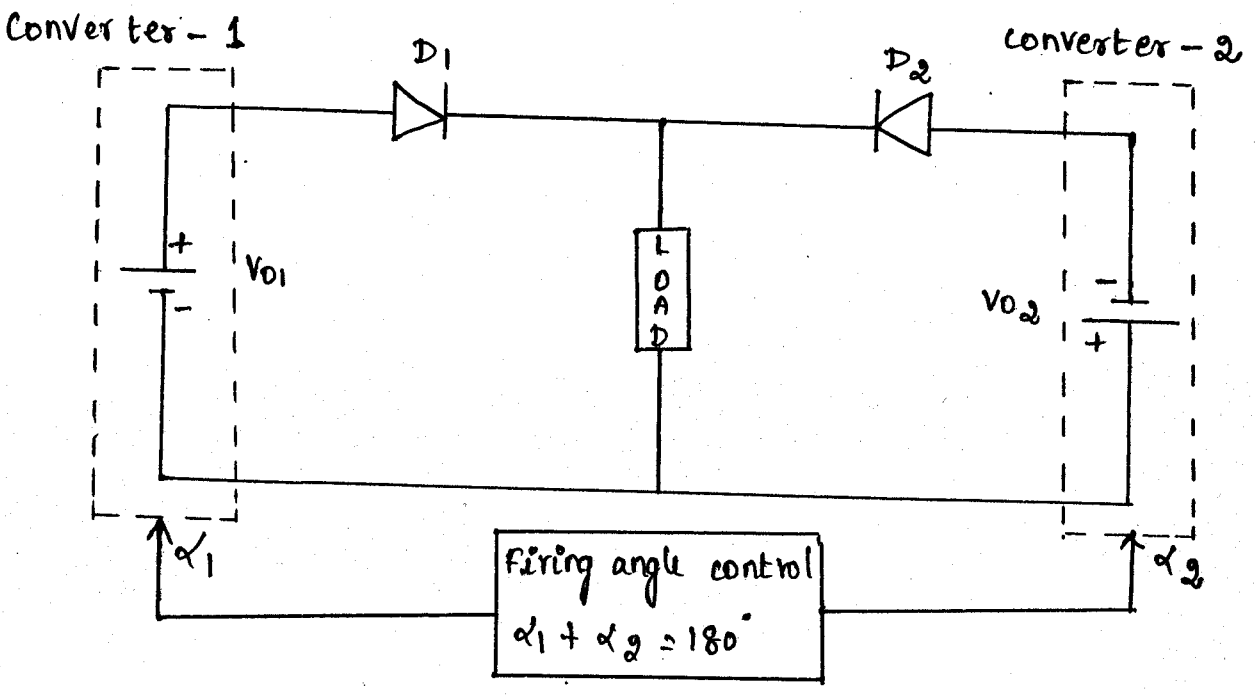
## PRINCIPLE OF DUAL CONVERTER (IDEAL DUAL CONVERTER):-



\* Assume that the dual converter consists of two ideal converters connected in antiparallel.

$$V_{o1} = \text{avg o/p vge of converter 1}$$

$$V_{o2} = \text{avg o/p vge of converter 2}$$

\* Diodes  $D_1$  and  $D_2$  connected in series indicate the unidirectional flow of current from the converters

\* Load current can flow in either direction.

\* Output voltages  $V_{o1}$  and  $V_{o2}$  are equal in magnitude but opposite in polarity

$$\text{i.e. } V_{o1} = -V_{o2}$$

\* So they drive current in opposite directions.

\* when one converter acts as a rectifier the other converter acts as an inverter.

∴ the average output voltages  $\Rightarrow$

$$V_{o1} = V_{max} \cos \alpha_1$$

$$V_{o2} = V_{max} \cos \alpha_2$$

$$\left[ \begin{array}{l} V_{max} = \frac{2V_m}{\pi} \text{ for } 1\phi \\ V_{max} = \frac{3\sqrt{3}V_m}{\pi} \text{ for } 3\phi \end{array} \right.$$

$\alpha_1 =$  firing angle of converter 1;  $\alpha_2 =$  firing angle of converter 2.

For ideal converter

$$V_o = V_{o1} = -V_{o2}$$

$$\text{i.e. } V_{max} \cos \alpha_1 = -V_{max} \cos \alpha_2$$


$$\therefore V_{max} \cos \alpha_1 = V_{max} \cos (180 - \alpha_2)$$

$$\cos \alpha_1 = \cos (180 - \alpha_2)$$

$$\alpha_1 = 180 - \alpha_2$$

$$\text{(or) } \boxed{\alpha_1 + \alpha_2 = 180}$$
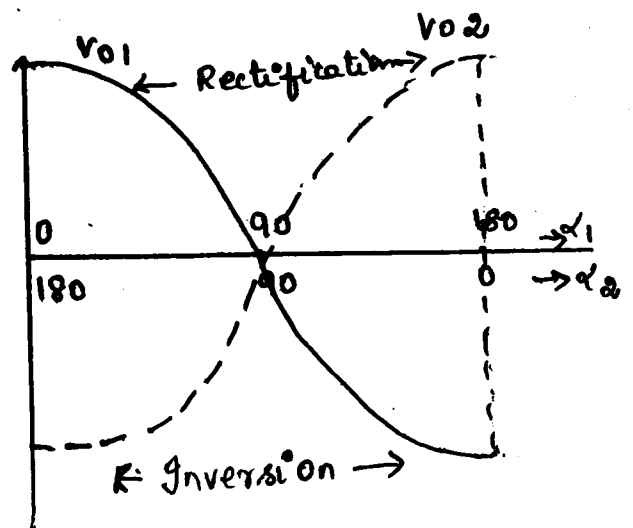
$$\left[ \begin{array}{l} V_{max} \cos \alpha_2 = V_{max} \cos (180 - \alpha_1) \\ -V_{max} \cos \alpha_2 = V_{max} \cos (180 - \alpha_1) \end{array} \right.$$






# PRACTICAL DUAL CONVERTER :-

- \* Firing angle of converters are such that  $\alpha_1 + \alpha_2 = 180$ .
  - \* One converter acts as rectifier with firing angle  $\alpha_1$ .
  - \* Other converter acts as inverter with firing angle  $\alpha_2 = 180 - \alpha_1$ .
  - \* Average value of o/p vges are equal (BUT)
  - \* Instantaneous values of vges are out of phase.
- This results in a voltage difference between the converters.
- \*  $\therefore$  a large circulating current flows between the two converters (but not through the load).
  - \* circulating current can be avoided by suitably triggering the converters.

$\therefore$  a dual converter can be operated in two modes

1. Dual converter without circulating current.
2. Dual converter with circulating current.
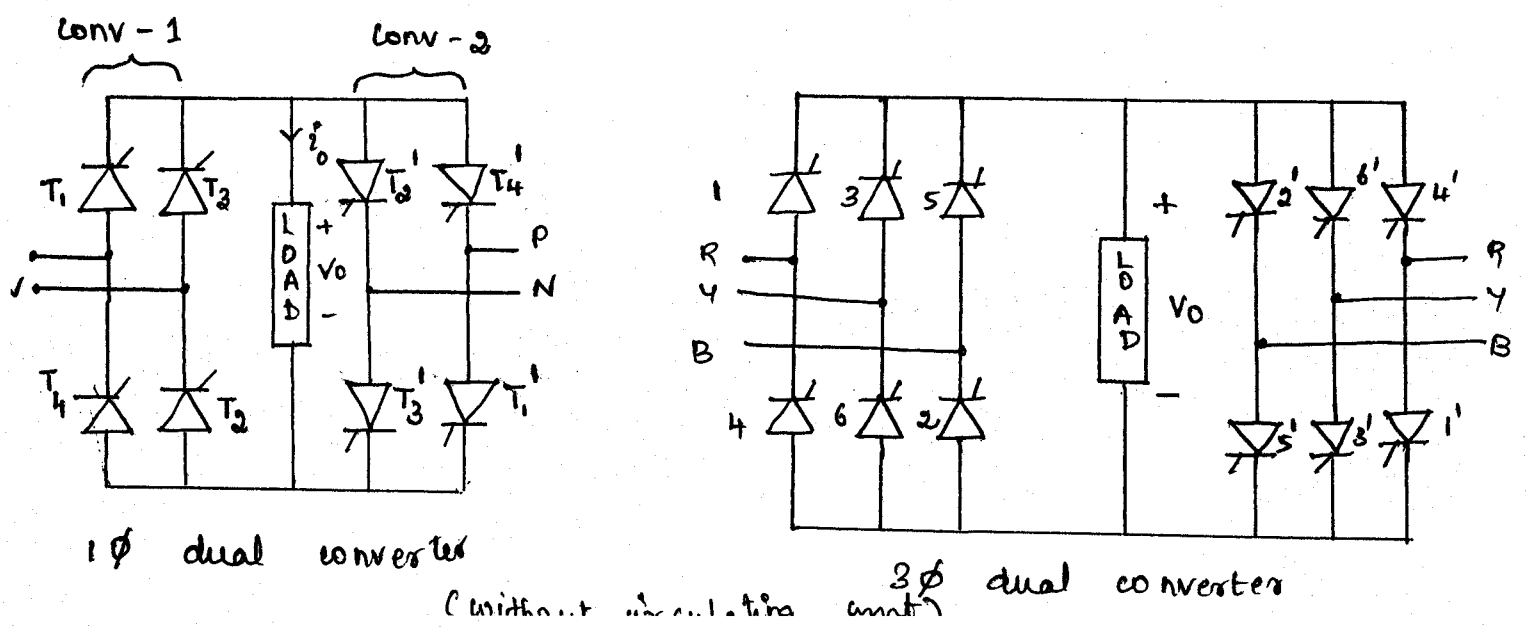
## DUAL CONVERTER WITHOUT CIRCULATING CURRENT :-



In this mode

\* Only one converter operates at a time.

\* Other converter is OFF by blocking gate pulses.

If converter 1 is ON :- For  $\alpha > 90^\circ$  operates in I quadrant  
 $\alpha < 90^\circ$  " " IV quadrant

If converter 2 is ON :- For  $\alpha > 90^\circ$  operates in II quadrant  
 $\alpha < 90^\circ$  " " III quadrant.

To turn ON the second converter,


\* first switch OFF converter 1

\* wait till load current decays to zero


\* Give a delay of 10 to 20 msec and switch conv 2.

(If converter 2 is triggered before converter 1 is OFF then circulating current flows)

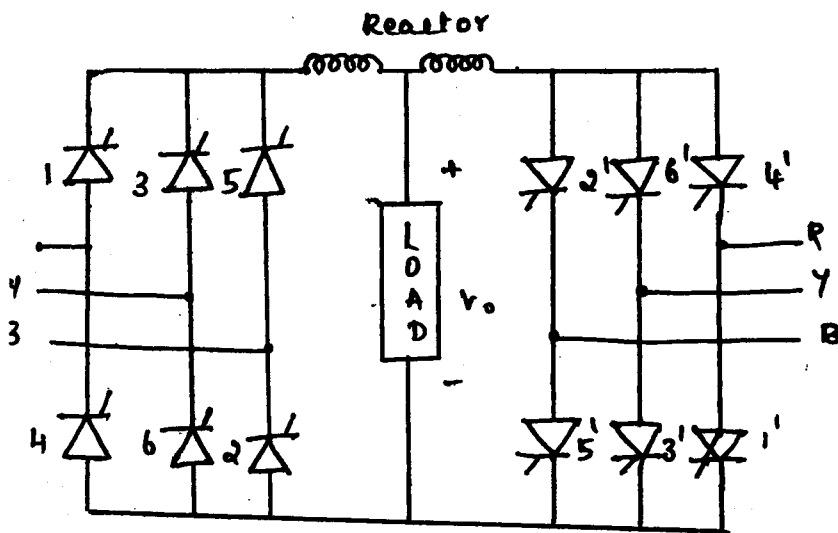1. DUAL CONVERTER WITH CIRCULATING CURRENT:-



3 $\phi$  dual converter

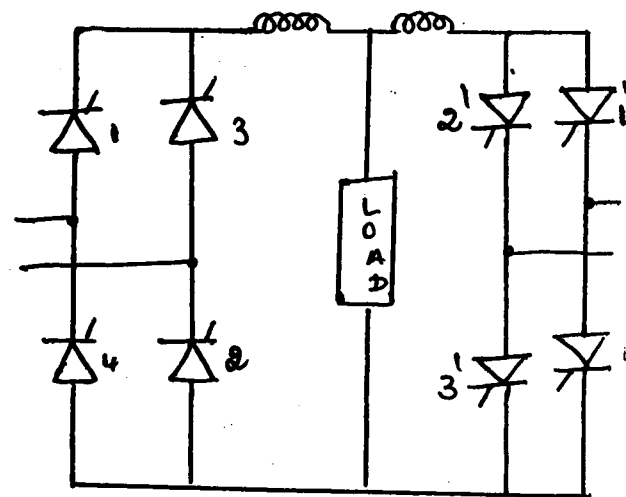

1 $\phi$  dual converter

(with circulating current)

+

In this mode

\* Both converters operate at same time.


\* One converter acts as rectifier while other acts as an inverter.

∴ the instantaneous values of output voltages are different, a circulating current flows. Magnitude of this current is limited by a reactor.

$\alpha_1 + \alpha_2 = 180^\circ$

[ If  $\alpha_1 = 60^\circ$  ;  $\alpha_2 = 180 - \alpha_1 = 180 - 60 = 120^\circ$  ]

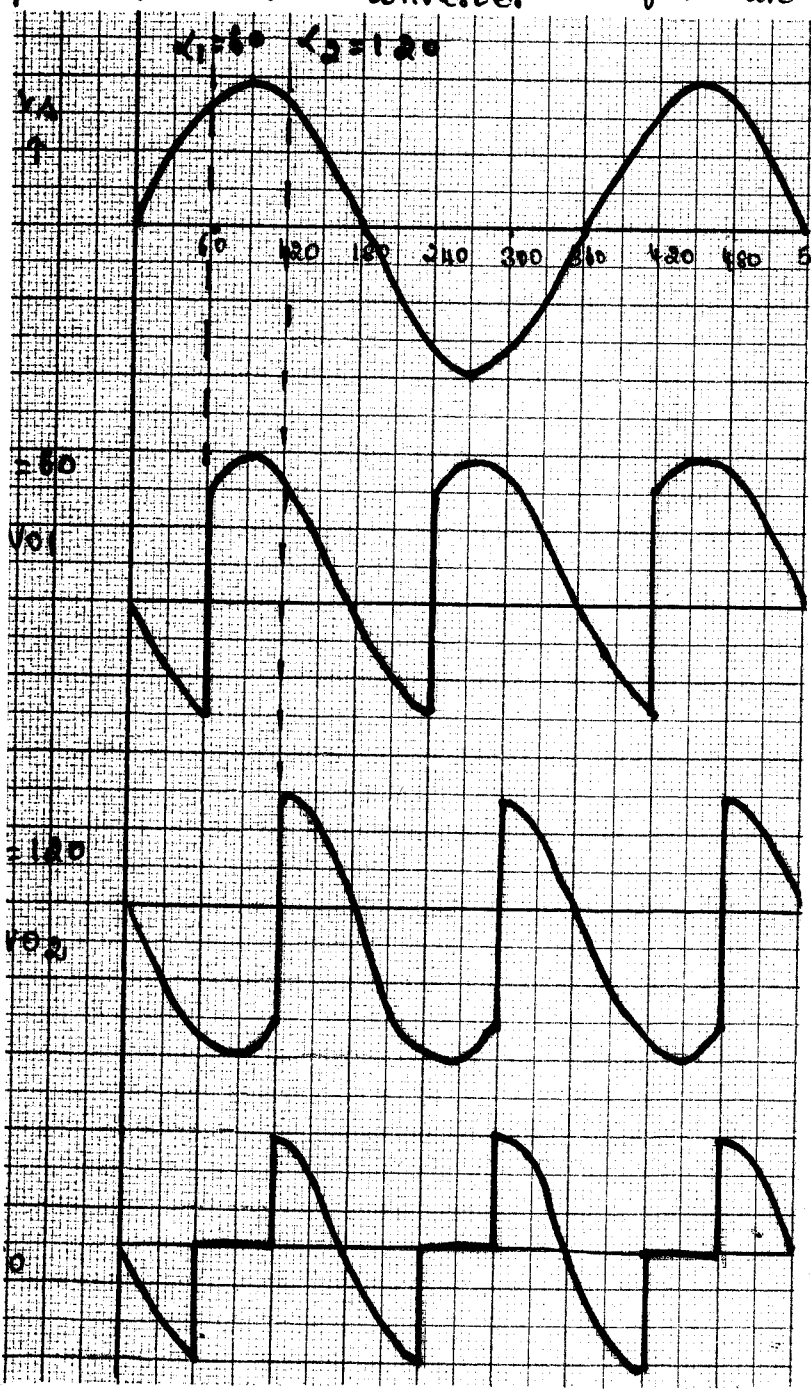for 1 $\phi$  dual converter. waveforms are.



Advantages:-

- \* continuous conduction of both the converters.
- \* Power flow in either direction.
- \* change from one converter to other is faster.

Disadvantages:-

- \* cost and size of reactor is high.
- \* circulating current increases losses and reduces efficiency.
- \* SCRs are required of very high current rating (∴ load current and circulating current flows thro' SCRs)

empty page.

+

# Difference between Half controlled and Fully controlled rectifiers

Half controlled converter	Fully controlled converter
<ul style="list-style-type: none"> <li>• This consists of half number of SCR's and half no of diodes.</li> </ul>	<ul style="list-style-type: none"> <li>• Consists of only SCR's as the controlled devices.</li> </ul>
<ul style="list-style-type: none"> <li>• Operates in only one quadrant</li> </ul>	<ul style="list-style-type: none"> <li>• Operates in two quadrants.</li> </ul>
<ul style="list-style-type: none"> <li>• Output voltage is always +ve</li> </ul>	<ul style="list-style-type: none"> <li>• Output voltage can be -ve in case of inductive load.</li> </ul>
<ul style="list-style-type: none"> <li>• Internal freewheeling action is present</li> </ul>	<ul style="list-style-type: none"> <li>• External freewheeling diode has to be connected.</li> </ul>
<ul style="list-style-type: none"> <li>• Power factor is better</li> </ul>	<ul style="list-style-type: none"> <li>• power factor is poor than half converter.</li> </ul>
<ul style="list-style-type: none"> <li>• Inversion is not possible</li> </ul>	<ul style="list-style-type: none"> <li>• Inversion is possible.</li> </ul>
<ul style="list-style-type: none"> <li>• Used for battery chargers, lighting and heater control</li> </ul>	<ul style="list-style-type: none"> <li>• Used for dc motor drives.</li> </ul>

# Comparison between 3 $\phi$ and 1 $\phi$ converters.

No	Parameter	1 $\phi$ Converter	3 $\phi$ Converter
1.	Ripple content in Output	More	Less
2.	Output power	Less upto 5kw	More than 5kw
3.	Ripple frequency	100 Hz	150 Hz and 300 Hz
4.	Control	Easy control	Complex control.
5.	circuit Implementation	Less complex	complex implementation
6.	Maximum supply power factor	0.9	0.955
7.	Supply and load derating	Higher	Less.

— X — X — X — X — X —