



17510

21415

3 Hours/100 Marks

Seat No.

--	--	--	--	--	--	--	--	--

-
- Instructions :** (1) Answer **each** next main question on a **new page**.
(2) Illustrate your answers with **neat sketches wherever necessary**.
(3) Figures to the **right** indicate **full marks**.
(4) Assume **suitable data**, if necessary.
(5) **Use of Non-programmable Electronic Pocket Calculator is permissible**.
-

MARKS

1. A) Attempt **any three** of the following : **12**
- a) Draw a single-line diagram of modern power system indicating essential components.
 - b) State the expression for Complex power, Real power and Reactive power at sending end of transmission line.
 - c) State the difference between 'A-C. resistance' and 'D.C. resistance' of a conductor.
 - d) For a generalised two port π (pi) network. Prove that $AD - BC = 1$ where A, B, C, D are GCC.
- B) Attempt **any one** of the following : **6**
- a) Explain the procedure to measure GCC of a erected to line.
 - b) Define 'self GMD' and 'Mutual GMD' with an example.
2. Attempt **any two** of the following : **16**
- a) i) List out the advantages of generalised circuit representation in power system analysis.
 - ii) Write expression for co-ordinates of centre and radius for sending end and receiving end circle diagram.

P.T.O.



- b) A three phase line with equilateral spacing of 3 mt. is to be rebuilt with horizontal spacing such that $D_{13} = 2D_{12} = 2D_{23}$. The line conductors are fully transposed. Determine the spacing between adjacent conductors so that the new tr. line has the same inductance as the original line.
- c) In a three phase line with 132 kV at receiving end has $A = D = 0.98 \angle 3^\circ$, $B = 110 \angle 75^\circ \Omega$. Find the sending end power if load of 200 MW at 0.8 p.f. lagging p.f. is being delivered at receiving end. Calculate the max. power demand for $V_R = V_S = 275$ kV.

3. Attempt **any four** of the following :

16

- a) Draw reactance diagram for given power system as shown in Fig. 1. considering generator rating as common base values.

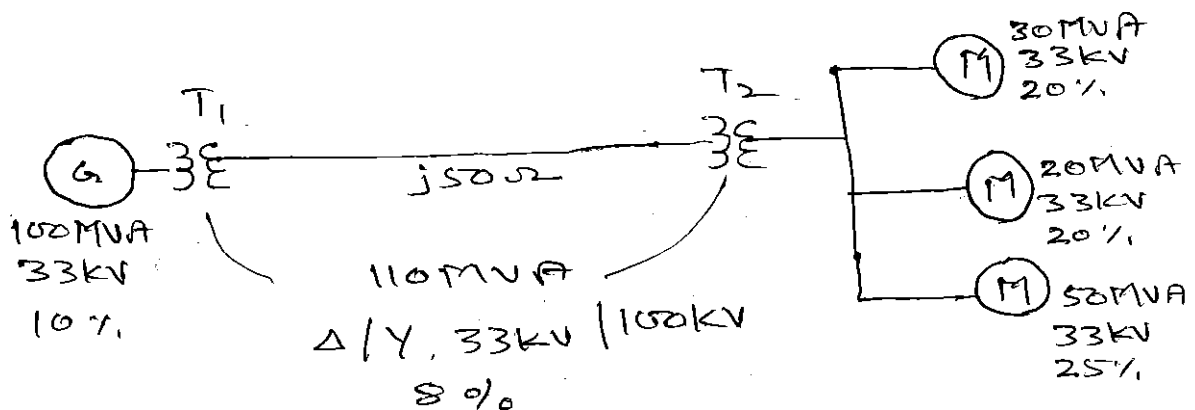


Fig. 1.

- b) Explain the stepwise procedure to draw sending end circle diagram.
- c) Determine the loop inductance of single phase tr. line comprised of solid conductors of diameter 1.5 cm. and spacing between two conductors as 7 mt.
- d) A 200 kV tr. line base GCC $A = 0.86 \angle 7^\circ$ $B = 300 \angle 75^\circ \Omega$. Determine real power at unity p.f. that can be received if voltage at both end are maintained at 200 kV.
- e) Derive an expression for capacitance of single phase tr. line comprised of solid conductors.



4. A) Attempt **any three** of the following : 12

- i) Define skin effect. State the factors on which skin effect depends ?
- ii) A 50 Hz, 3 ϕ , 27 kV line has following GCD $A = 0.896 \angle 0.7^\circ$,
 $B = 138.7 \angle 84.2^\circ$. If line is supplied at 275 kV determine the MVA rating of shunt reactor that would be required to maintain 275 kV at receiving end when line is delivering no load.
- iii) State advantages of p.v. system in power system analysis.
- iv) State the necessity of reactive power compensation. Explain any one method of the reactive power compensation.

B) Attempt **any one** of the following : 6

- a) A 3 ϕ , 50 Hz line has resistance of 20 Ω , inductance 0.2 H and capacitance 1 μ F. All parameters are per km. Length of line is 150 km and delivers a load of 50 MW at 132 kV, 0.8 lag. p.f. Determine ABCD constants of the line (considering π model).
- b) Determine the self G.M.D. of conductors shown in Fig. 2.
Assume $r = 0.1$ cm :



Fig. 2.

5. Attempt **any two** of the following : 16

- a) Two transmission line networks are connected in series. Determine A, B, C, D constants of overall network.
- b) A 3 ϕ , 132 kV tr. line delivers 40 MVA at 0.8 p.f. lagging. Determine sending end voltage with the help of circle diagram. Given that $A = 0.98 \angle 3^\circ$
 $B = 110 \angle 72^\circ \Omega$. Also find max. power delivered at receiving end.



- c) Determine inductive reactance of 1ϕ tr. line with the arrangement as shown in fig. 3. The diameter of each conductor is 1 cm. and current is equally shared by two parallel conductors.

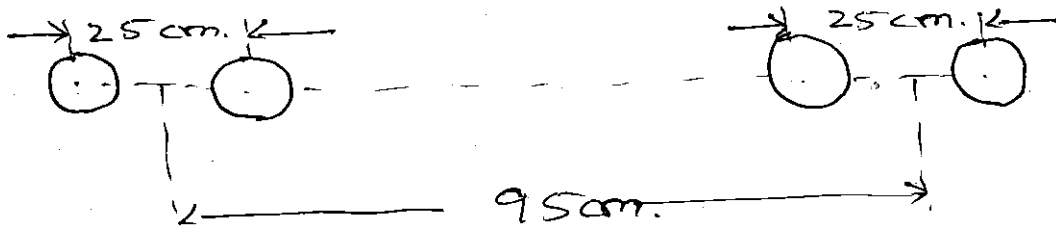


Fig. 3.

6. Attempt **any four** :

16

- Derive the expression for complex power at receiving end of the line with generalised circuit.
- Prove that p.u. reactance of transformer remains same refer to both side of the transformer.
- Give significance of inductance, resistance and capacitance parameters of tr. line.
- State the field of applications of following reactive power compensators :
 - Shunt capacitor bank
 - Series inductor bank
 - Synchronous condenser
 - Auto transformer.
- A 3 phase, 50 Hz, line is 250 km long. It has series impedance $35 + j 40 \Omega$ and shunt admittance $930 \times 10^{-4} \bar{U}$. It delivers 40 MW at 220 kV with 0.9 lag. p.f. Determine ABCD constant considering medium line having nominal T circuit.