

17547

14115

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--	--	--

- Instructions –*
- (1) All Questions are *Compulsory*.
 - (2) Answer each next main Question on a new page.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Assume suitable data, if necessary.

	Marks
1. a) Attempt any <u>THREE</u> of the following:	12
(i) State necessity of adder and subtractor circuit in PAL-D decoder.	
(ii) Draw block diagram of sync. separator and describe its working.	
(iii) Justify the use of microcontroller in TV receiver.	
(iv) Draw construction of SAW filter. Why pre-amplifier is needed before the SAW filter.	
b) Attempt any <u>ONE</u> of the following:	6
(i) Draw ckt. diagram of ident and colour killer ckt. and describe its operations.	
(ii) Draw construction of trinitron picture tube and describe its working.	

- 2.** **Attempt any FOUR of the following:** **16**
- a) Draw block diagram of SMPS. State the functions of each block.
 - b) Draw ckt. diagram of ACC amplifier and describe its working.
 - c) Illustrate the operation of forward SMPS with neat circuit diagram.
 - d) State the purpose of remote control system in TV. State its advantages and disadvantages (any two of each).
 - e) State the features of plasma TV (any four).
 - f) Draw the block diagram of remote control transmitter and receiver.
- 3.** **Attempt any FOUR of the following:** **16**
- a) Draw block diagram of push-pull SMPS and state the function of each block.
 - b) Draw block diagram of microcontroller based TV.
 - c) Draw block diagram of VIF stage in colour TV receiver and draw its response curve.
 - d) Draw ckt. diagram of reference oscillator and state its need in PAL-D decoder.
 - e) Compare plasma and LCD display technology (any four points).
- 4.** a) **Attempt any THREE of the following:** **12**
- (i) Explain with the suitable diagram how an LCD display works.
 - (ii) State the need of AGC and AFT in colour TV receiver.
 - (iii) Explain the working principle of plasma screen.
 - (iv) Draw ckt. diagram of vertical output amplifier and describe its working.
- b) **Attempt any ONE of the following:** **6**
- (i) Draw schematic diagram of VIF IC and state the function of each block.
 - (ii) Draw ckt. diagram of luminance signal processing and describe its working.

5. Attempt any TWO of the following: **16**

- a) Draw block diagram of colour TV receiver. State the function of each block.
- b) Draw schematic diagram of IC 7609 and state the function of each block.
- c) Draw block diagram of PAL-D decoder and state the function of each block.

6. Attempt any FOUR of the following: **16**

- a) Draw block schematic of AFT and state the function of each block.
 - b) List any eight major controls available in plasma TV. State the function of any two controls.
 - c) Explain with diagram working of freqⁿ synthesizer tuning.
 - d) What is 3D TV technology? Why it is necessary to use special glasses for watching 3D programmes?
 - e) Draw construction of chroma delay line and describe its working.
-