



17547

11718

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All questions are **compulsory**.
 - (2) Answer **each** next main question on a **new** page.
 - (3) Illustrate your answers with neat sketches **wherever** necessary.
 - (4) Figures to the **right** indicate **full** marks.
 - (5) Assume suitable data, if **necessary**.
 - (6) Use of Non-programmable Electronic Pocket Calculator is **permissible**.
 - (7) Mobile Phone, Pager and any other Electronic Communication devices are **not** permissible in Examination Hall.
 - (8) Use of Steam tables, logarithmic, Mollier's chart is **permitted**.

Marks

1. A) Attempt **any three** : **(4×3=12)**
- a) Describe generation of U and V signals in TV Receiver.
 - b) State necessity of adder and subtractor circuit in PAL-D decoder.
 - c) Why micro controller is used in TV Receiver ?
 - d) With neat block diagram explain working of AFT in colour TV.
- B) Attempt **any one** : **(6×1=6)**
- a) What is meant by auto stereoscope method of 3D TV ? Write its one advantages. Name the different methods and describe any one.
 - b) Draw construction of trinitron picture tube and describe its working.
2. Attempt **any four** of the following : **(4×4=16)**
- a) Draw block diagram of SMPS. State the function of each block.
 - b) Draw ckt. diagram of ACC amplifier and describe its working.
 - c) State purpose of remote control system in TV. Write its advantages and disadvantages (any two of each).
 - d) List any eight major controls available in plasma TV. State function of any two controls.
 - e) Describe orientation of liquid crystal to form matrix of picture pixels in TV.
 - f) Draw diode split technique for generation of EHT.

P.T.O.

**3. Attempt any four :**

- a) Draw and describe basic structure of SAW filter.
- b) Draw schematic diagram of IC-CA-7607 and state its function.
- c) Draw schematic diagram of Colour Killer Circuit and state its function.
- d) Compare plasma and LCD display technology (any 4 points).
- e) Draw ckt diagram of reference oscillator and state its need in PAL-D decoder.

4. A) Attempt any three of the following :

(4×3=12)

- a) State need of AGC in Colour TV Receiver.
- b) Draw ckt diagram of vertical output amplifier and describe its working.
- c) Draw the block diagram of sweep section and elaborate the function of any two blocks.
- d) Draw Luminance signal processing ckt diagram and describe its working.

B) Attempt any one of the following :

(6×1=6)

- a) Illustrate with suitable ckt diagram how the IDENT and Killer o/p's are obtained from the burst phase discriminator output.
- b) Draw neat diagram of PAL decoder and state function of each block.

5. Attempt any two :

(8×2=16)

- a) Draw neat block diagram of Colour TV receiver and state function of each block.
- b) Draw neat circuit diagram of horizontal output amplifier and describe its operation.
- c) Draw schematic diagram of IC 7609 and state the function of each block.

6. Attempt any four of the following :

(4×4=16)

- a) Draw construction of chroma delay line and describe its working.
 - b) What is 3D TV Technology ? Why it is necessary to use special glasses for watching 3D programmes ?
 - c) Illustrate with diagram working of frequency synthesizer tuning.
 - d) Draw neat block diagram of sound section of TV and explain it.
 - e) Draw block diagram of hyper band tuner state different types of tuning.
-