

17320

11718

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions* –
- (1) All Questions are *Compulsory*.
 - (2) Answer each next main Question on a new page.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

1. a) Attempt any SIX of the following: 12
- (i) Draw symbol of EXOR gate and also write its truth table.
 - (ii) Identify the function of IC 0800 and IC 0809.
 - (iii) Convert the following binary number to gray code:
 - 1) 1101001
 - 2) 11111
 - (iv) What is the role of Preset and clear terminal of flip-flop?
 - (v) Compare TTL and CMOS Logic families. (2 points)
 - (vi) What is Tristate buffer? Draw its symbol.
 - (vii) Define modulus of counter? How many flip flops are required for mod 5 counter?
 - (viii) State the necessity of multiplexer.

P.T.O.

b) **Attempt any TWO of the following:****8**

- (i) Convert the following into Binary and Add them
 $(A96)_{16} + (28B)_{16}$
- (ii) Differentiate between Synchronous and Asynchronous counter.
- (iii) Draw circuit diagram of 1:4 Demux using logic gate.
Write its truth table.

2. **Attempt any FOUR of the following:****16**

- a) Compare EPROM and flash memory.
- b) Describe operation of full adder with proper truth table and logical diagram.
- c) Convert the following number into Binary:
 - (i) $(736.6)_8$
 - (ii) $(2F9.25)_{16}$
- d) State and prove De Morgan's Theorems.
- e) Draw the diagram of 3-bit twisted ring counter using JK F/F.
Also write its truth table. Draw waveforms.
- f) Draw the block diagram of successive approximation type ADC and explain its working.

3. Attempt any FOUR of the following:**16**

- a) Convert the following expression into their standard SOP form $Y = A + BC + ABC + B$
- b) What is Race around condition and how it is eliminated?
- c) Solve the following using 1^s and 2^s complement method.
 - (i) $(42)_{10} - (63)_{10}$
 - (ii) $(11010)_2 - (11100)_2$
- d) What is priority encoder? Draw the truth and symbol table of decimal to BCD encoder.
- e) Draw 4 bit weighted resistor DAC and give expression for output voltage.
- f) Reduce the following Boolean expression using Boolean laws.

$$Y = A\bar{B} + \bar{A}B + AB + \bar{A}\bar{B}$$

$$Y = A\bar{B}C + \bar{A}BC + ABC$$

4. Attempt any FOUR of the following:**16**

- a) Draw the internal diagram of IC 7490. Design mod 8 counter using IC 7490.
- b) Explain with circuit diagram, the principle of TTL gate (NAND) with totem pole.
- c) Calculate analog output of 4 bit DAC and digital input is 1011. Assume $V_{fs} = 5V$
- d) Compare sequential and combinational logic circuit. (Four points)
- e) Implement OR gate and AND gate using NAND gate.
- f) Compare single slope and dual slope ADC.

5. Attempt any FOUR of the following:**16**

- a) Compare R-2R and binary weighted register.
- b) Define memory? Write down types of memory.
- c) Draw PIPO shift register. State applications of shift register.
- d) Design 16:1 MUX using 8:1 MUX
- e) Give any four characteristics of CMOS and ECL logic families.
- f) Convert the following decimal numbers into excess-3 code
 - (i) $(5)_{10}$
 - (ii) $(25)_{10}$
 - (iii) $(46)_{10}$
 - (iv) $(144.4)_{10}$

6. Attempt any FOUR of the following:**16**

- a) Draw block diagram and explain working of dual slope ADC.
 - b) Describe working of SR latch using NAND gates with proper truth table.
 - c) Draw the block diagram of ALU IC 74181 and also write its operation.
 - d) Mention any eight Boolean laws.
 - e) Draw 3 bit synchronous counter with truth table and explain working.
 - f) Draw and explain static RAM cell (TTL).
-