

17524

11718

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Illustrate your answers with neat sketches wherever necessary.
 - (3) Figures to the right indicate full marks.
 - (4) Assume suitable data, if necessary.
 - (5) Use of Non-programmable Electronic Pocket Calculator is permissible.
 - (6) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

1. (A) Attempt any **THREE** of the following :

12

- (a) State the various types of D.C. Motor. Give atleast two applications of D.C. Motor.
- (b) (i) Define intrinsic and extrinsic semiconductor.
(ii) Draw symbol of Diode and Zener diode.
- (c) Draw the wiring diagram of 'Turn Indicator'.
- (d) Define : (i) Frequency (ii) Cycle
(iii) Time period (iv) Amplitude

(B) Attempt any **ONE** of the following :

1 × 6 = 6

- (a) Describe construction and working of single phase transformer.
- (b) Define wiring Harness. State the importance of colour coding in automobile electrical wiring.

[1 of 4]

P.T.O.

2. Attempt any FOUR of the following :**16**

- (a) Describe working of ultrasonic flow meter.
- (b) State any four difference between self induction and mutual inductance.
- (c) Draw any four electrical symbols.
- (d) Describe working of resistance split phase induction motor with help of diagram.
- (e) Draw symbols of LED, SCR, photodiode and N–P–N transistor.
- (f) Define the terms :
 - (i) Dynamic error
 - (ii) Sensitivity
 - (iii) Accuracy
 - (iv) Speed of response

3. Attempt any FOUR of the following :**16**

- (a) Draw a labelled diagram of LVDT and describe its function as gauge for displacement measurement.
- (b) Describe working of P-N junction diode. Draw characteristics also.
- (c) Describe the working of seven segment LED display.
- (d) A 200 kVA, 3300/240 V, 50 Hz single phase transformer has 80 turns on secondary winding. Calculate :
 - (i) Primary and secondary current
 - (ii) Maximum value of flux
 - (iii) Number of primary winding turns
- (e) Compare the mechanical instruments and electrical instruments.

4. (A) Attempt any THREE of the following :

12

- (a) Define the following terms :
 - (i) Current
 - (ii) Resistance
 - (iii) Magnetic flux
 - (iv) Reluctance
- (b) Compare insulated and earthed return system.
- (c) Draw the block diagram of 'General Measurement System'.
- (d) Compare between core type transformer with shell type transformer.
(4 points)

(B) Attempt any ONE of the following :

6

- (a) Describe with circuit diagram the working of centre tapped full wave rectifier. Draw the wave form of input and output.
- (b) Define the terms multiplexer and de-multiplexer. Draw Schematic diagram of 1 : 4 de-multiplexer.

5. Attempt any FOUR of the following :

16

- (a) Describe construction and working of RJD.
- (b) State the types of stepper motor and describe any one.
- (c) Compare between PNP transistor and NPN transistor.
- (d) What is positive return system and negative return system ?

P.T.O.

- (e) Three resistance $10\ \Omega$, $15\ \Omega$ and $25\ \Omega$ are connected in series and the potential difference across them is 250 V. Find
- (i) Equivalent Resistance of circuit.
 - (ii) Total current of the circuit.
 - (iii) Voltage drop across each resistance
- (f) Draw the symbols and truth table for NOR and NAND.

6. Attempt any FOUR of the following :

16

- (a) Draw the symbols and truth table of R-S and D-flip-flop.
 - (b) State Faraday's Law of electromagnetic induction.
 - (c) Draw & explain V-I characteristics of SCR. Define latching current and holding current.
 - (d) Draw a neat sketch of stroboscope and describe working to measure speed of induction motor.
 - (e) Describe the working of strain gauge load cell.
-