

Scheme - I

Sample Question Paper

Program Name : Electrical Engineering Program Group
Program Code : EE/EP/EU
Semester : Fifth
Course Title : Elements of Industrial Automation (Elective)
Max. Marks : 70

22526

Time: 3 Hrs.

Instructions:

- (1) All questions are compulsory.
- (2) Illustrate your answers with neat sketches wherever necessary.
- (3) Figures to the right indicate full marks.
- (4) Sub-questions in a main question carry equal marks.
- (5) Assume suitable data if necessary.
- (6) Preferably, write the answers in sequential order.

Q.1 Attempt any Five of the following.

10 Marks

- a) Draw the symbols of following components used in industrial control circuits.
 - i) Fuse
 - ii) Over load relay
 - iii) Earthing
 - iv) 3 Φ Induction Motor
- b) State the functions of PID controller module and communication module.
- c) List any two input and output devices used in conjunction with PLC
- d) Draw the symbols of following relay type instructions. i) IF-OPEN ii) IF -CLOSE
- e) State any two uses of HMI.
- f) State the function of seal in circuit w.r.t. PLC.
- g) Draw the ladder program for verifying the XOR logic.

Q.2 Attempt any Three of the following.

12 Marks


- a) Develop the control circuit for star-delta starter used for starting a 3 Φ Induction Motor.
- b) State the functions of following components in PLC i) Input module ii) CPU
- c) Draw a ladder diagram for 3 motor operation for following condition:
 - i) Start push button starts motor M_1 . After 15 seconds M_2 and M_3 starts
 - ii) Stop push button stops M_3 and after 15 seconds motor M_2 and M_1
- d) Develop the ladder diagram for ON/OFF temperature controller.

Q.3) Attempt any Three of the following.

12 Marks

- a) Explain the instruction T_{ON} and T_{OFF} .
- b) Explain block diagram of SCADA .Identify different components of it.
- c) Develop the ladder program for Forward – Reverse control of a 3 Φ Induction Motor.

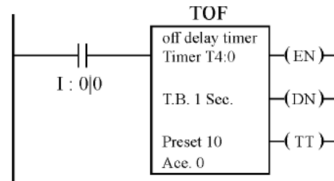- d) Draw the timing diagram for following timer instruction bit.
- I:0/0
 - EN
 - DN
 - TT



Q.4) Attempt any Three of the following.

12 Marks

- Develop a ladder and wiring diagram of DOL starter with OLR.
- Identify the criterion for comparing the given PLCs for particular application.
- Explain with block diagram the working of soft starter.
- Explain the working of FWD-STOP-REV control circuit of an Induction motor.
- Draw the block diagram of digital input module of PLC. State function of its blocks.

Q.5) Attempt any Two of the following.

12 Marks

- Develop a generalized DCS architecture for control of a plant.
- Explain the working of PLC based Traffic light control with the help of ladder diagram.
- Develop a control and power circuit for conveyer.

Q.6) Attempt any Two of the following.

12 Marks

- Develop the ladder program for bottle filling application.
- Explain the block diagram and function of each part in PID controller module.
- Develop a ladder program explaining the use of Latching Relay.
 - Explain the ladder program of water level controller

Scheme - I

Sample Test Paper - I

Program Name : Electrical Engineering Program Group
Program Code : EE/EP/EU
Semester : Fifth
Course Title : Elements of Industrial Automation (Elective)
Max. Marks : 20

22526

Time: 1 Hour

Instructions:

- (1) All questions are compulsory.
- (2) Illustrate your answers with neat sketches wherever necessary.
- (3) Figures to the right indicate full marks.
- (4) Sub-questions in a main question carry equal marks.
- (5) Assume suitable data if necessary.
- (6) Preferably, write the answers in sequential order.

Q.1 Attempt any FOUR.

08 Marks

- a. State the need of Automation.
- b. State the functions of proximity switch and pressure switch.
- c. State the function of soft starter.
- d. Draw the symbol of MCB and DC motor.
- e. Differentiate between modular and fixed PLC.
- f. State the function of stepper motor module in PLC.

Q.2 Attempt any THREE.

12 Marks

- a. Develop control and power circuit for lifting magnet.
- b. Develop control and power circuit for mill extruder.
- c. Compare micro and mini PLCs based on CPU type, no. of I/Os, speed and memory.
- d. Identify the components of Analog output module. State the functions of any four of them.
- e. Explain the functions of various components of the block diagram of PLC

Scheme - I

Sample Test Paper - II

Program Name : Electrical Engineering Program Group
Program Code : EE/EP/EU
Semester : Fifth
Course Title : Elements of Industrial Automation (Elective)
Max. Marks : 20

22526

Time: 1 Hour

Instructions:

- (1) All questions are compulsory.
- (2) Illustrate your answers with neat sketches wherever necessary.
- (3) Figures to the right indicate full marks.
- (4) Sub-questions in a main question carry equal marks.
- (5) Assume suitable data if necessary.
- (6) Preferably, write the answers in sequential order.

Q.1 Attempt any FOUR.

08 Marks

- a. State the components of Ladder diagram.
- b. Draw a PLC wiring diagram for control of a lamp from 2 switches.
- c. State the I/O list for bottle filling application.
- d. State the function of RTU and MTU w.r.t. SCADA.
- e. State any four features of DCS.
- f. Draw the off delay timer instruction with waveforms.

Q.2 Attempt any THREE.

12 Marks

- a. Develop forward reverse control of 3 Φ IM using PLC.
- b. With reference to Ladder logic, draw the symbols of following instructions:
 - (i) NO
 - (ii) OSR
 - (iii) Output coil
 - (iv) NC.
- c. List arithmetic instructions of PLC. Explain any one instruction with example.
- d. Draw ladder diagram for given truth tables

A	B	y
0	0	1
0	1	0
1	0	0
1	1	0

A	B	y
0	0	1
0	1	0
1	0	0
1	1	1

- e. Explain CTD instruction with waveforms.