

22526

11920

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Answer each next main Question on a new page.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

1. Attempt any FIVE of the following :

10

- (a) State the need of automation.
- (b) Draw the symbol of following :
 - (i) push button
 - (ii) limit switch
 - (iii) proximity switch
 - (iv) pressure switch
- (c) Draw the block diagram of PLC.
- (d) Draw and explain ladder diagram for AND operation.
- (e) List types of timers.
- (f) State the function of seal in circuit w.r.t. PLC.
- (g) Give the full form of SCADA & HMI.

- 2. Attempt any THREE of the following : 12**
- (a) Develop the control circuit for star-delta starter used for starting a 3 ϕ induction motor.
 - (b) State the functions of PLC memory w.r.t. types, speed of execution.
 - (c) Develop the ladder diagram for stepper motor control.
 - (d) Write the ladder program for 24 hour clock.
- 3. Attempt any THREE of the following : 12**
- (a) Explain count up (CTU) instruction with timing diagram.
 - (b) Develop the ladder diagram for forward-reverse control of a 3 ϕ induction motor.
 - (c) Explain instructions :
 - (i) If-closed
 - (ii) If-open
 - (d) Explain block diagram of SCADA. Identify different components of it.
- 4. Attempt any THREE of the following : 12**
- (a) Explain with block diagram, the working of soft starter.
 - (b) Explain the working of FWD – STOP – REV control circuit of an induction motor.
 - (c) Draw the block diagram of analog input module of PLC. State the function of each block.
 - (d) Explain the function of
 - (i) Communication module
 - (ii) PID controller module
 - (e) Develop ladder and wiring diagram of DOL starter with OLR.

5. Attempt any TWO of the following : 12

- (a) Develop control and power circuit diagram of hoist control and mill.
- (b) Develop a generalised DCS architecture for control of a plant.
- (c) Explain the working of PLC based bottle filling system with the help of ladder diagram.

6. Attempt any TWO of the following : 12

- (a) Develop a ladder diagram for ON/OFF temperature control.
 - (b) Explain the instruction T_{on} and T_{off} with timing diagram.
 - (c) Draw the block diagram of digital output module of PLC and explain the function of each block.
-

