

22225

11819

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
  - (2) Illustrate your answers with neat sketches wherever necessary.
  - (3) Figures to the right indicate full marks.
  - (4) Assume suitable data, if necessary.

- |   | <b>Marks</b> |
|---|--------------|
| <b>1. Attempt any FIVE of the following :</b>   | <b>10</b>    |
| (a) Draw the symbol of inductor and capacitor. State the unit of inductor and capacitor.  |              |
| (b) State the need of filters. Define filter.   |              |
| (c) Define $\alpha$ and $\beta$ of transistor.  |              |
| (d) Define amplification factor and trans-conductance of JFET.  |              |
| (e) State the two advantages and disadvantages of integrated circuits.  |              |
| (f) Define transducer and name two passive transducers.   |              |
| (g) State seebeck and Peltier effect.   |              |
| <br>  |              |
| <b>2. Attempt any THREE :</b>   | <b>12</b>    |
| (a) Determine the value of capacitance with the following colour code.<br>(i) Orange, Orange, Blue<br>(ii) Yellow, Violet, Yellow |              |
| (b) Draw the neat sketch of center tap full wave rectifier. Draw i/p and o/p waveforms.   |              |
| (c) Draw and explain zener diode as a voltage regulator.  |              |
| (d) Describe the working principle of npn transistor with the help of diagram.  |              |

**3. Attempt any THREE :****12**

- (a) Sketch the construction of n-channel JFET and explain its working principle.
- (b) Differentiate active and passive transducer on the basis of any four points.
- (c) State the different types of resistors. State any four specifications of resistors.
- (d) Explain the working of two stage RC coupled amplifier with neat circuit diagram.


**4. Attempt any THREE :****12**

- (a) Explain any four selection criteria of transducers for temperature measurement.
- (b) Differentiate between P-N junction diode and zener diode.
- (c) Draw DC load line of transistor. Explain working of transistor as a switch.
- (d) Draw the Drain characteristics of JFET showing different operating regions. If drain current is 5 mA,  $I_{DSS} = 10 \text{ mA}$  &  $V_{as (off)} = -6V$ . Find the value of  $V_{as}$ .
- (e) Draw the block diagram of regulated power supply and explain the working of each block.

**5. Attempt any TWO :****12**

- (a) Solve the following :

- (i) In the waveform shown in fig. (1). State it's amplitude, frequency, phase and wavelength.

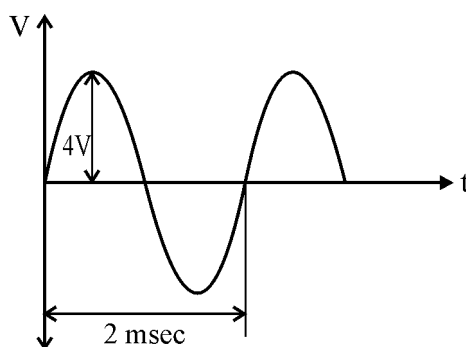**Fig. 1**

- (ii) Define : amplitude and frequency

- (b) (i) In Circuit shown in fig. (2), a silicon transistor with  $\beta = 50$  is used. Take  $V_{BE} = 0.7$  V. Find Q point value.

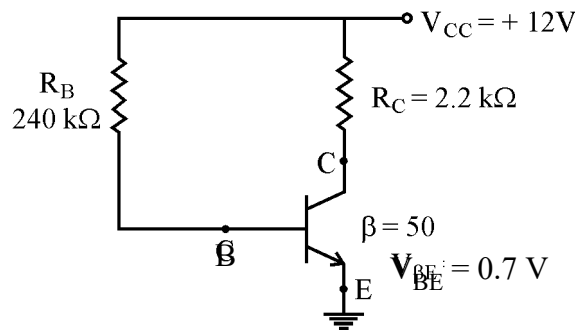


Fig. 2

- (ii) Define operating point of the transistor.
- (c) In full wave bridge rectifier  $V_m = 10$  V,  $R_L = 10$  K $\Omega$   
find out  $V_{DC}$ ,  $I_{DC}$ , ripple factor and PIV.

6. Attempt any TWO :

12

- (a) Explain working principle of N-Channel depletion type MOSFET with construction diagram. Compare depletion type MOSFET & enhancement type MOSFET.
- (b) Differentiate CE, CB, CC w.r.t. to
- (i) Input resistance
  - (ii) Output resistance
  - (iii) Current gain
  - (iv) Voltage gain
  - (v) Phase shift between input and output
  - (vi) Applications
- (c) List four types of electrical pressure transducers and describe one application of each one.

